





JOINT INSTITUTE

交大密西根学院


FET Single Stage Amplifier

Ve311 Electronic Circuits (Fall 2020)

Dr. Chang-Ching Tu

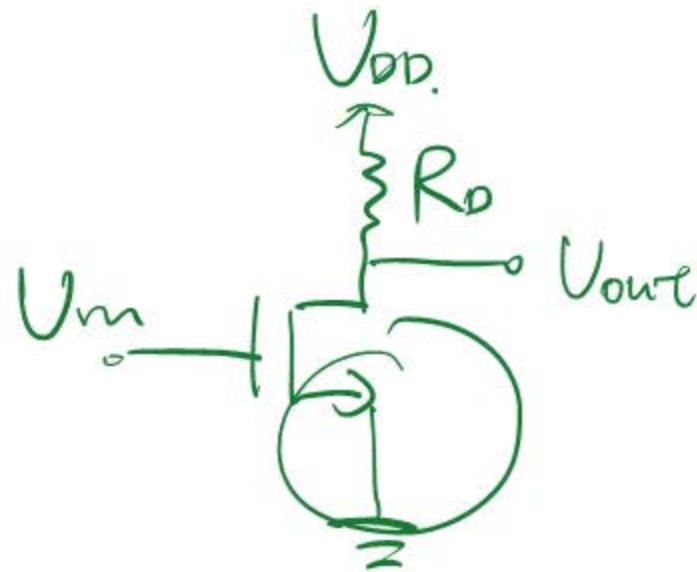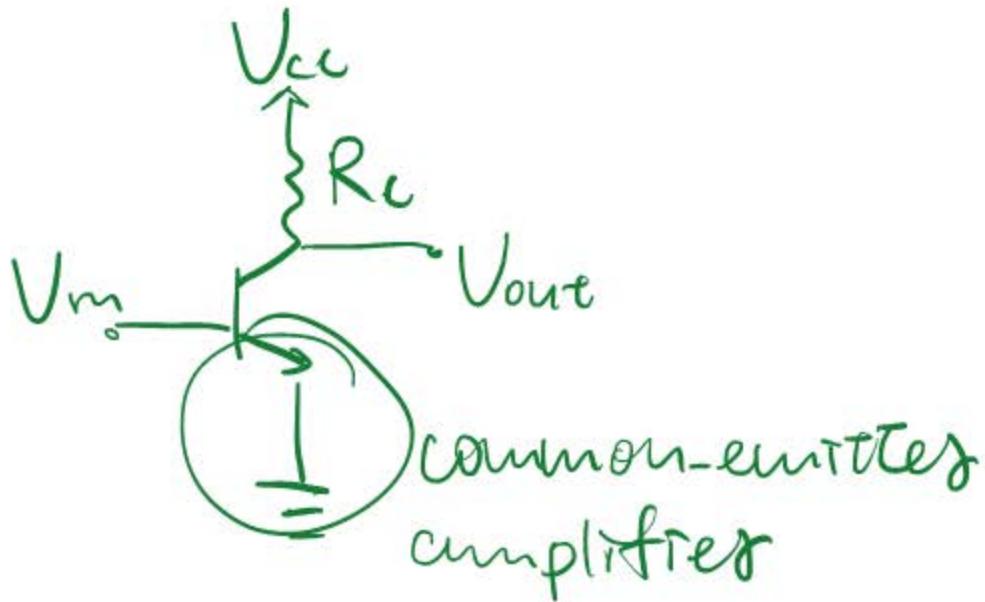

Common-Source with Resistive Load

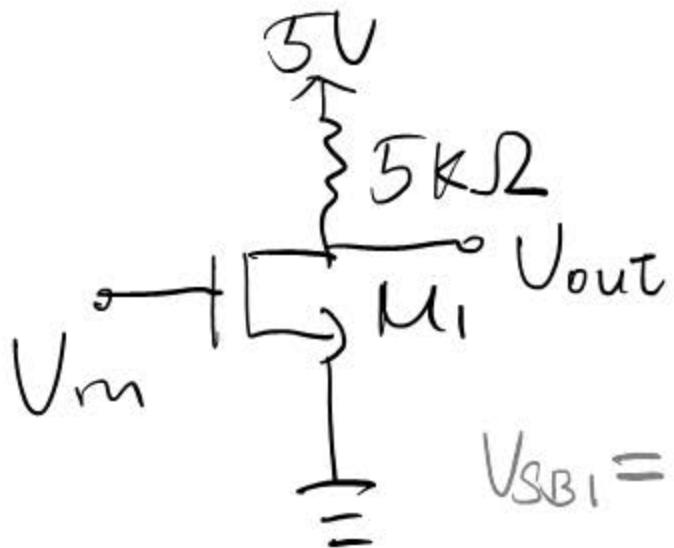

M₁ has size $\frac{10 \mu m}{2 \mu m} = \frac{\text{W drawn}}{\text{W drawn}}$

$\lambda \neq 0, \gamma \neq 0$

$$Vm = 0.8 + 0.0018m(2\pi f_0 t)$$

$$V_{out} = V_{outT} + V_{outC} = ?$$

1° Find out $V_{outT} = ?$
then confirm whether

$$V_{DS} \geq V_{GS} - V_{TH}$$


$$V_{outT} \geq V_{IN} - (V_{TH}) = 0.1$$

$0.8 \quad 0.7$

$$V_{outT} = 5 - (5k) \cdot I_{D1}$$


$$I_{D1} = \frac{1}{2} \mu n C_{ox} \left(\frac{10 \mu m}{2 \mu m + 2L_D} \right)$$

$$(0.8 - 0.7)^2 (1 + \lambda V_{out})$$

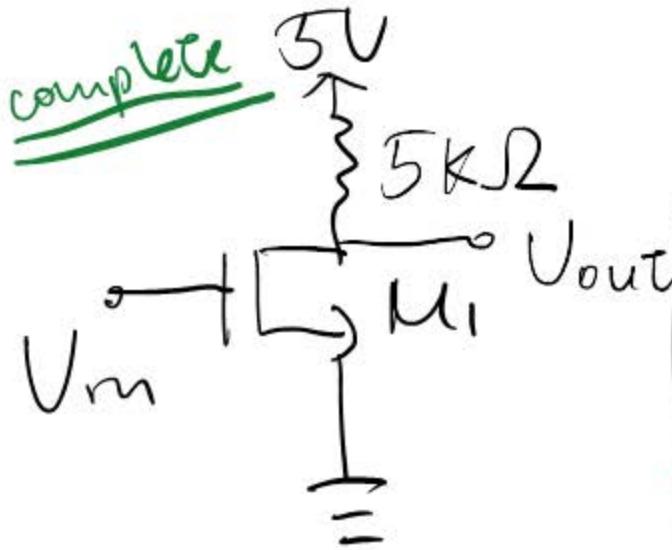

2° Find out $U_{out} = ?$


If using Pspice, do DC sweep.

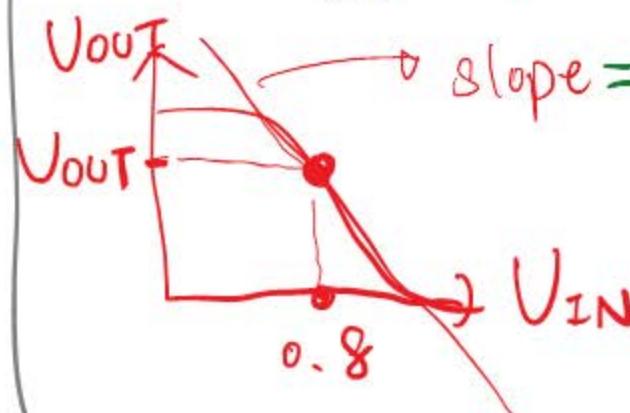


$$Av = \left. \frac{dU_{out}}{dU_{IN}} \right|_{U_{IN}=0.8}$$

$$U_{out} = 0.001 Av \sin(\omega t)$$

Small-signal

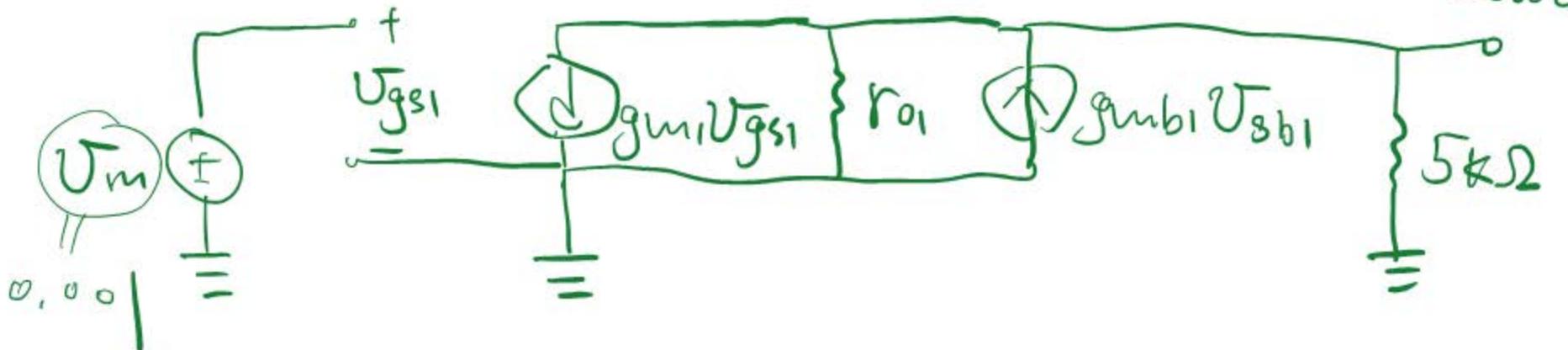

Small-signal

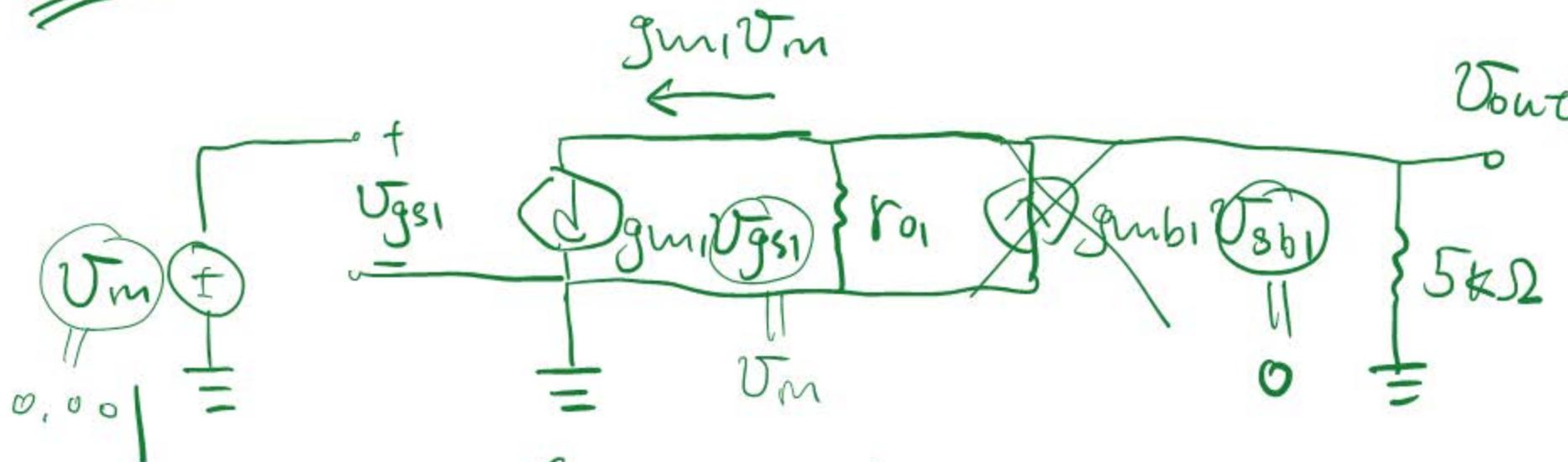

$$V_{out} = - (g_{m1} V_m) (r_{o1} \parallel 5k\Omega)$$

$$\{ g_{m1} = I_{D1} \text{Cox} \left(\frac{W}{L_{eff}} \right) (0.1)^2 (+\Delta V_{out})$$

$$r_{o1} \approx \frac{1}{I_{D1} \gamma}$$



$$\boxed{A_v = \frac{V_{out}}{V_m}} = -g_{m1} (r_{o1} \parallel 5k\Omega)$$

Common-Source with Resistive Load

DC Analysis

$$\lambda = 0$$

$$\gamma = 0$$

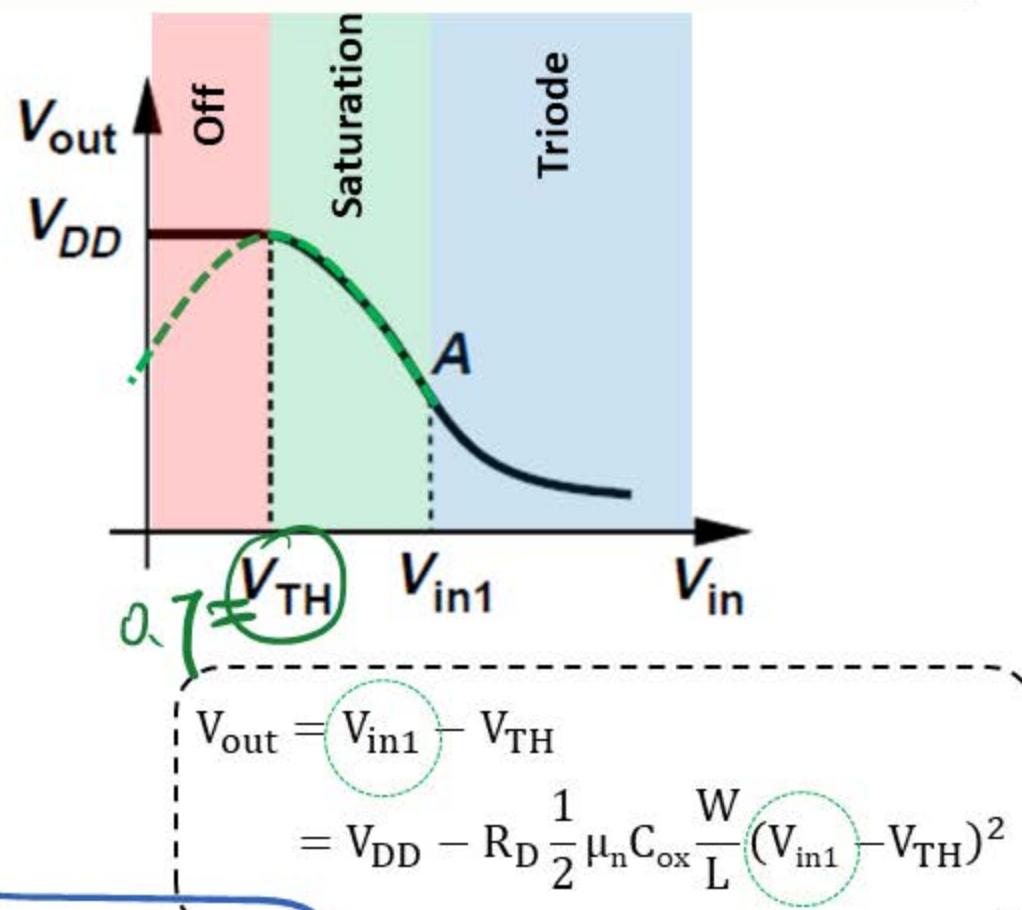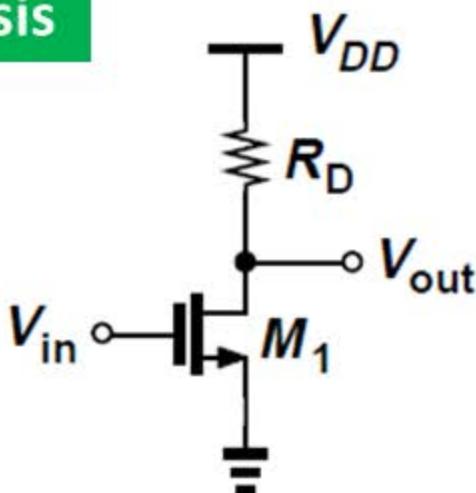

- $V_{in} < V_{TH} \rightarrow M_1 \text{ Off}$

$$V_{out} = V_{DD}$$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1 \text{ in Saturation}$

$$V_{out} = V_{DD} - R_D \left[\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \right] = I_{D1}$$

- $V_{in} > V_{in1} \rightarrow M_1 \text{ in Triode}$



$$V_{out} = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} \left[(V_{in} - V_{TH}) V_{out} - \frac{1}{2} V_{out}^2 \right] = I_{D1}$$

Common-Source with Resistive Load

DC Analysis

$$\lambda = 0$$

$$\gamma = 0$$

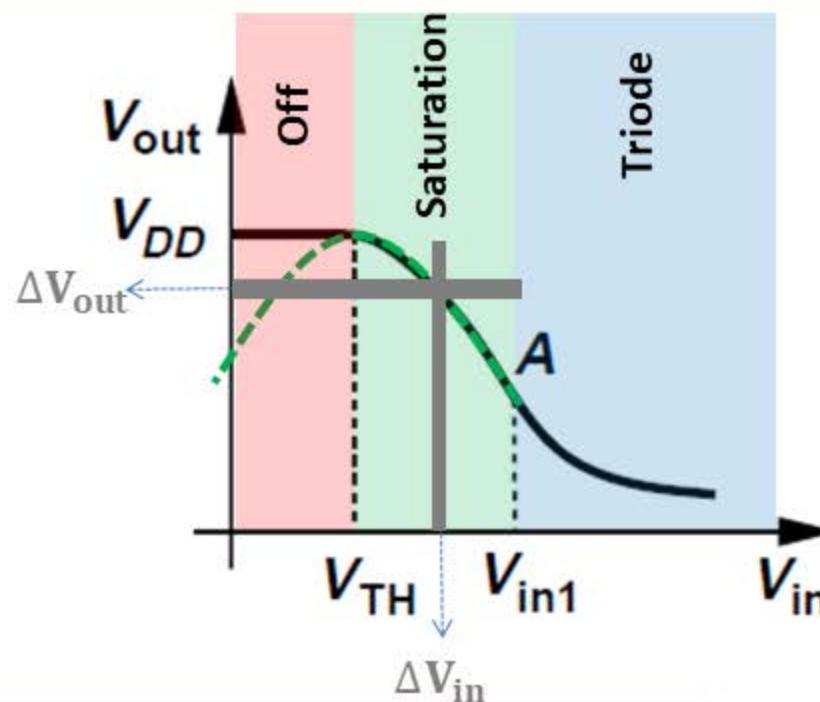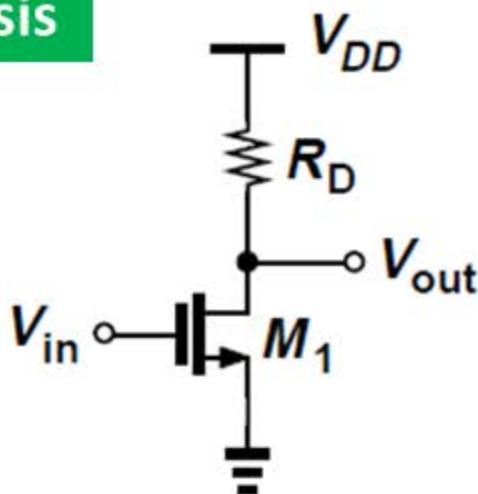

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH}) \\ = -gm \cdot R_D$$


- V_{gs} increases by $\Delta V_{in} \rightarrow I_d$ increases by $\Delta V_{in} \cdot gm \rightarrow V_{out}$ decreases by $\Delta V_{in} \cdot (gm \cdot R_D)$

Common-Source with Resistive Load

Small-signal Analysis

$$\lambda = 0$$

$$\gamma = 0$$

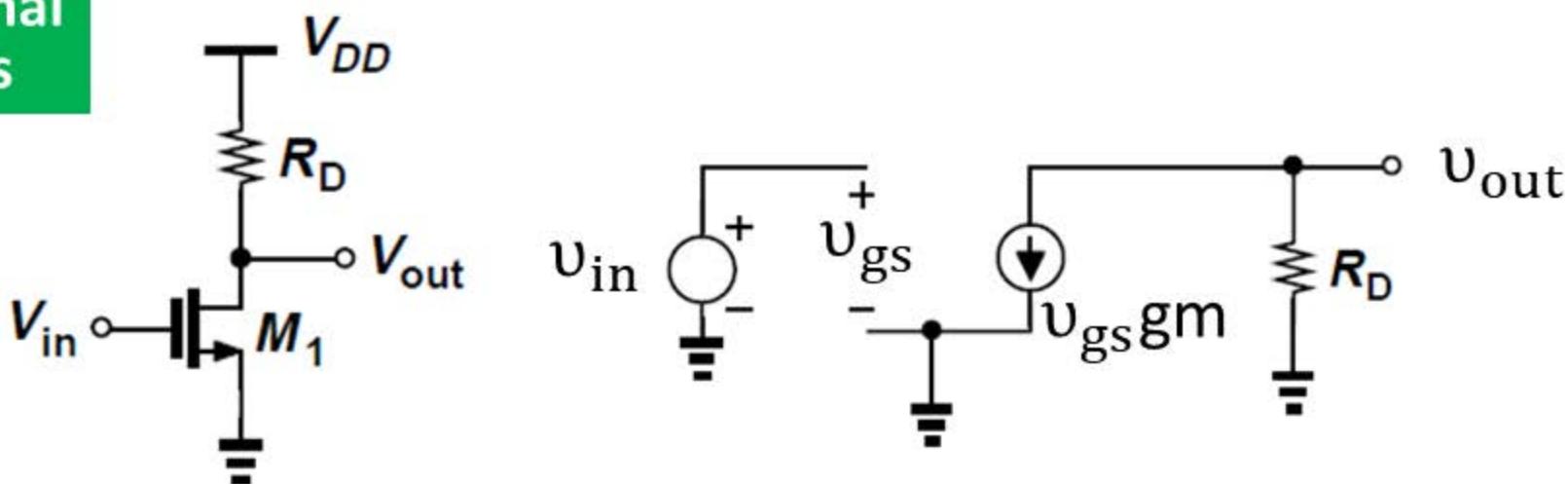

$$A_v = \frac{v_{out}}{v_{in}} = -gm \cdot R_D$$



- Small-signal analysis leads to the same result as DC analysis.

Common-Source with Resistive Load

DC Analysis

$$\lambda \neq 0$$

$$\gamma \neq 0$$

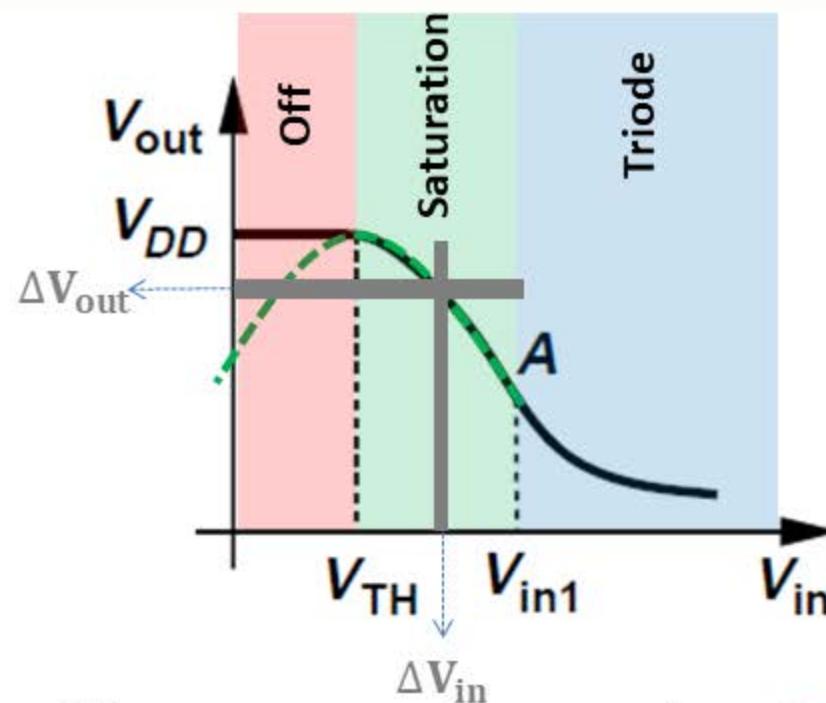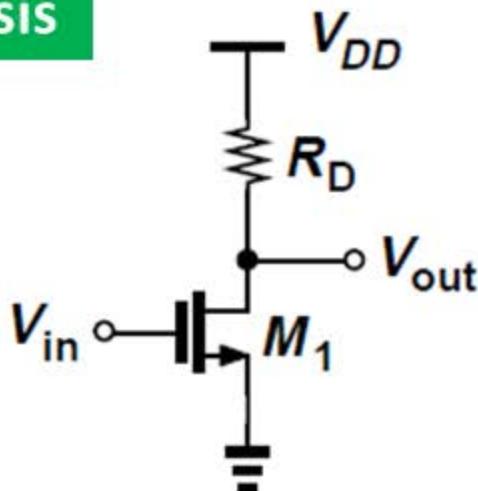

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = \frac{\partial \left[V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{out}) \right]}{\partial V_{in}}$$

$$= -R_D \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})(1 + \lambda V_{out}) - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \lambda \frac{\partial V_{out}}{\partial V_{in}}$$

$$= gm \quad \approx I_D \quad = A_v$$


$$A_v = \frac{-gmR_D}{1 + R_D \frac{I_D}{r_o} \lambda} = -gm \frac{1}{R_D + r_o} = -gm(R_D \parallel r_o)$$

$$= 1/r_o$$

Common-Source with Resistive Load

Small-signal Analysis


$\lambda \neq 0$
 $\gamma \neq 0$

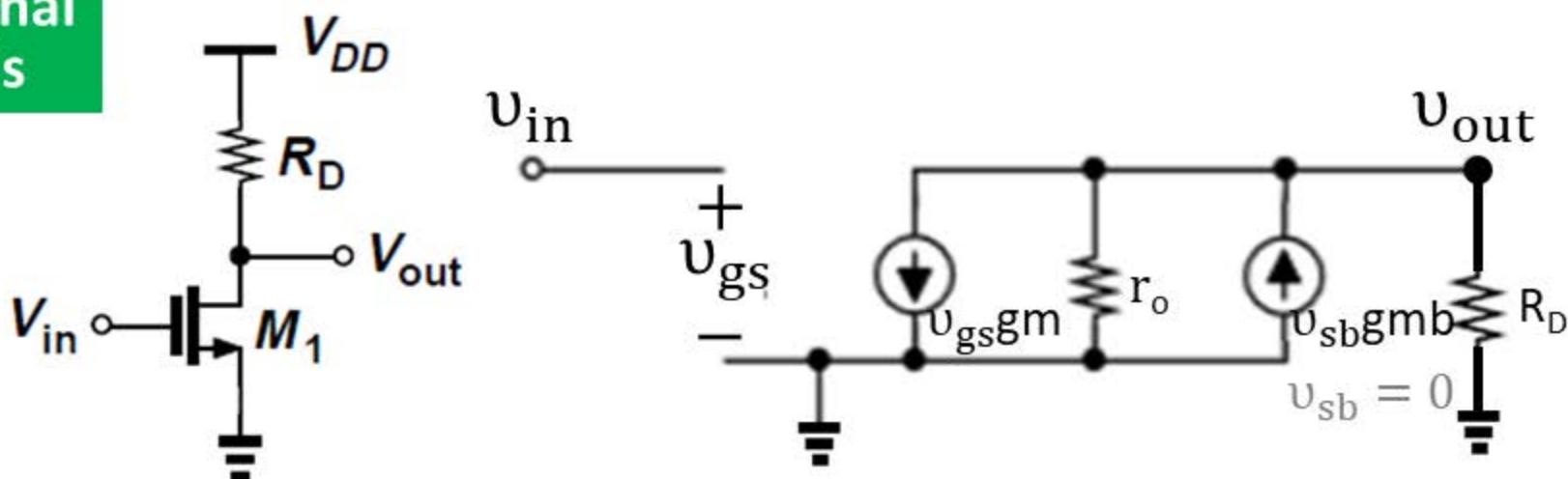

$$A_v = \frac{v_{out}}{v_{in}} = -gm \cdot (R_D \parallel r_o)$$

- Small-signal analysis leads to the same result as DC analysis.
- gm is a function of V_{GS} and V_{DS} , while r_o is a function of I_D . → **Nonlinearity**

(A)

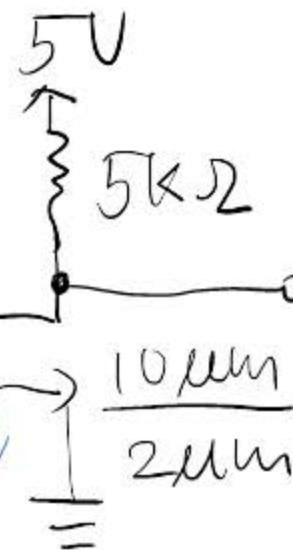

$r = 0, \lambda \neq 0$

(B)

$$V_{out} = ?$$

$$\begin{aligned} 0.8 & \rightarrow \\ +0.0018mwt & \rightarrow \frac{10\mu m}{2\mu m} \end{aligned}$$

$$\boxed{V_{SB} = 0}$$

$$\boxed{U_{SB} = 0}$$

$$V_{TH} = V_{TH0} = 0.7$$




$$\begin{aligned} 0.9 & \rightarrow \\ +0.0018mwt & \rightarrow \frac{10\mu m}{2\mu m} \end{aligned}$$



$$V_{out} = ?$$

$$\boxed{V_{SB} = 0.1}$$

$$\boxed{U_{SB} = 0}$$


$$V_{TH} > V_{TH0} = 0.7$$

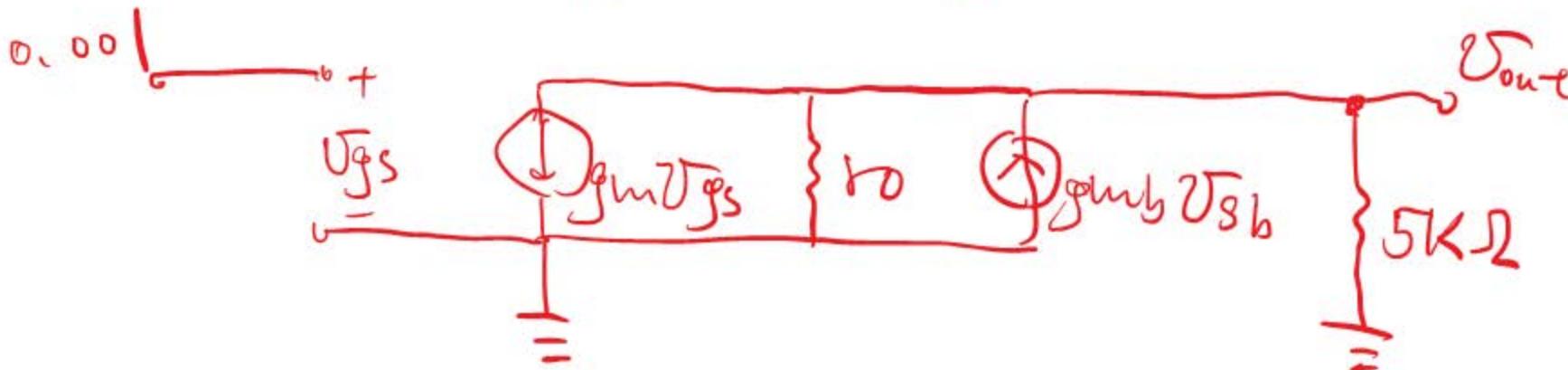

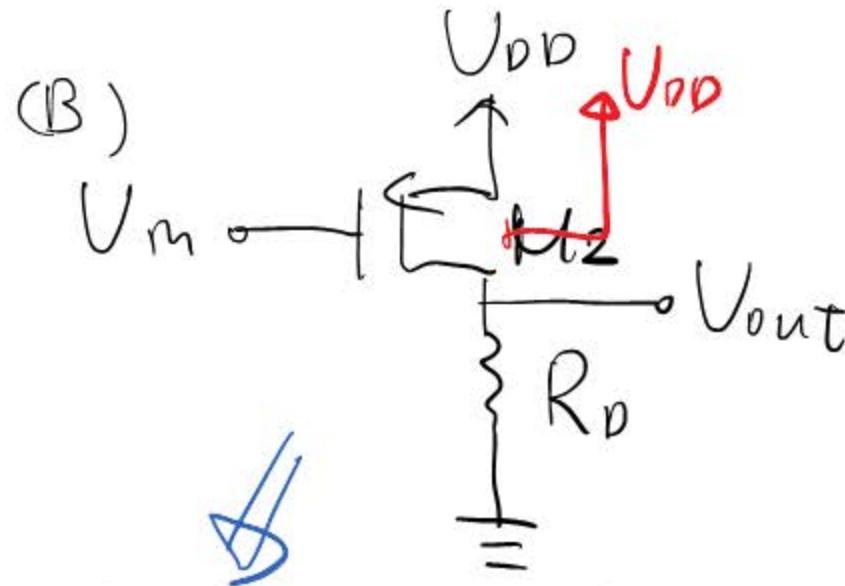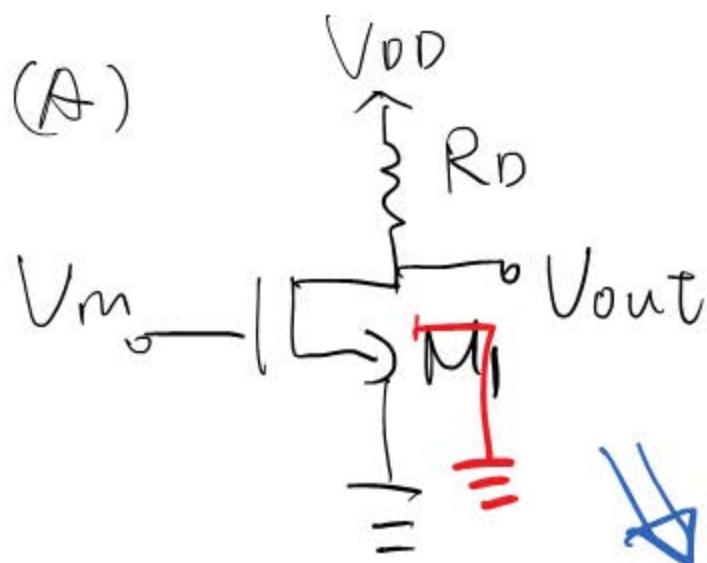


what are the analytical expressions for A_V ?
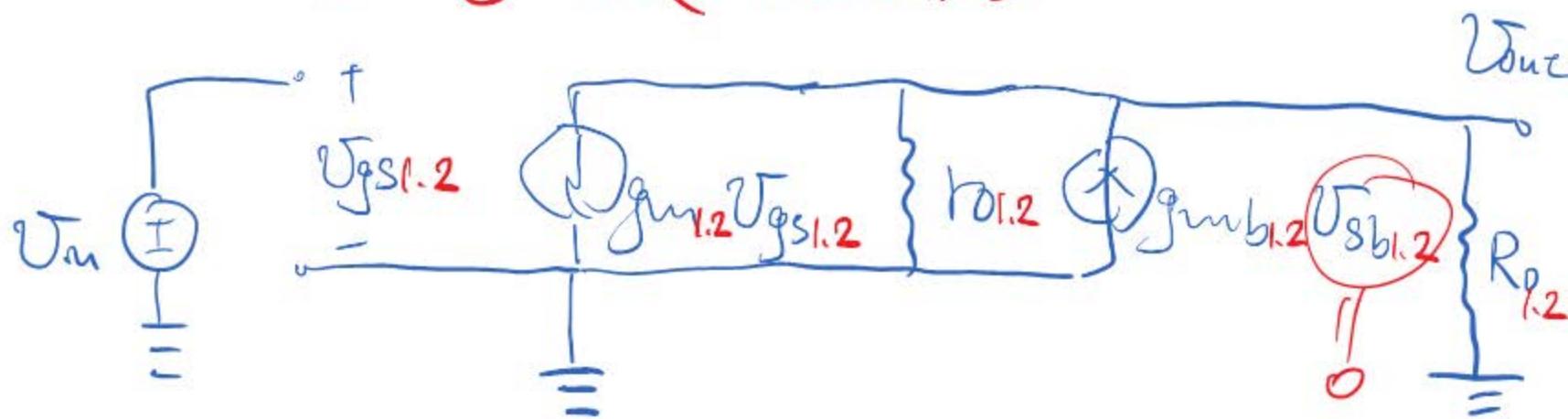
$$A_V = -g_{m1,2} (f_{D1,2} / R_{D1,2})$$




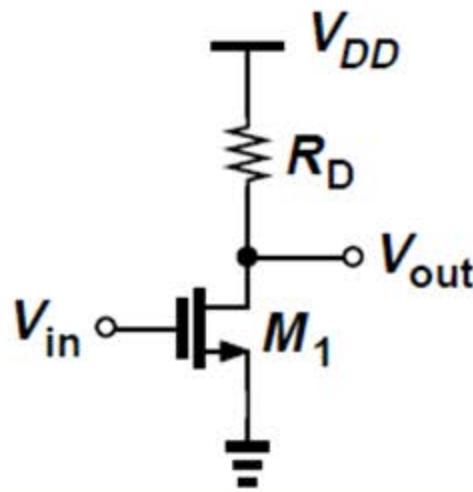Example


Sketch the drain current and transconductance of M_1 as a function of input voltage. Assume $\lambda = \gamma = 0$.



Solution:


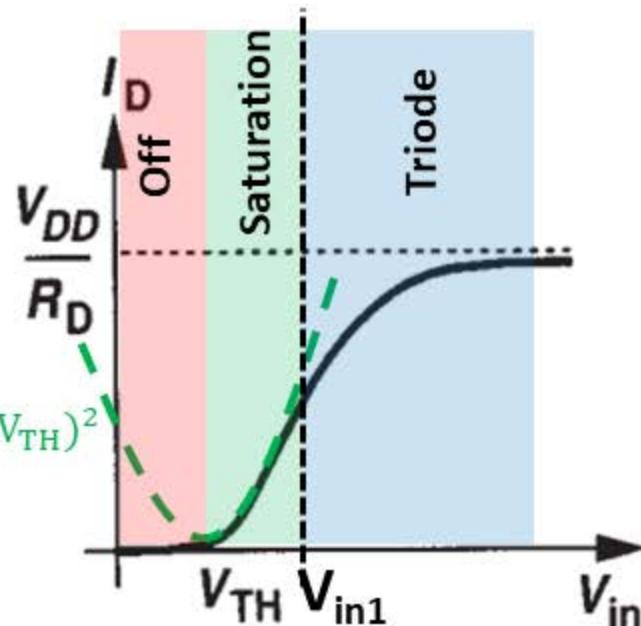

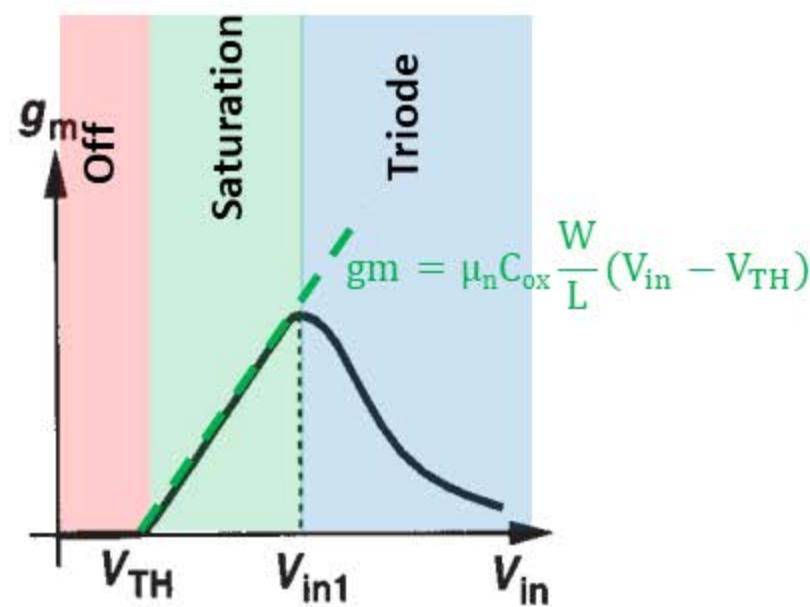
$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2$$



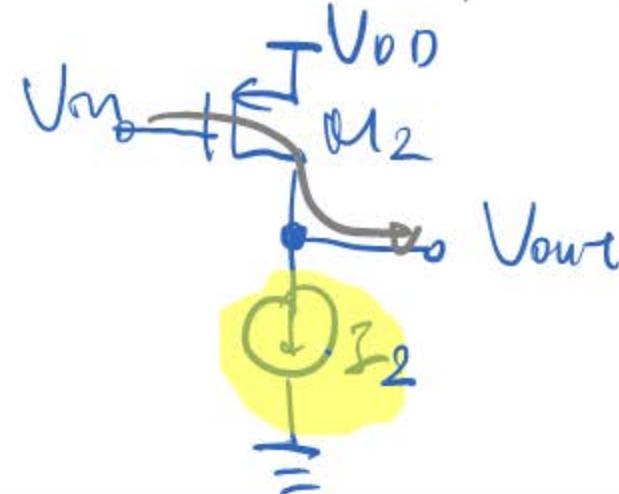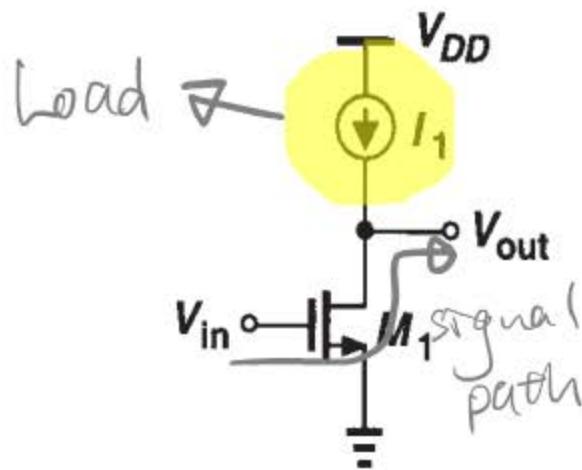Example

Assuming M_1 in saturation, calculate its small-signal gain. (analytical form)



Solution:

- Small-signal Analysis:

$$A_v = \frac{V_{out}}{V_{in}} = -gm_1 r_{o1} \approx \frac{1}{n I_{D1}}$$



- DC Analysis:

$$I_1 = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 (1 + \lambda V_{DS})$$

$r_o \neq 0$
 $\gamma \neq 0$

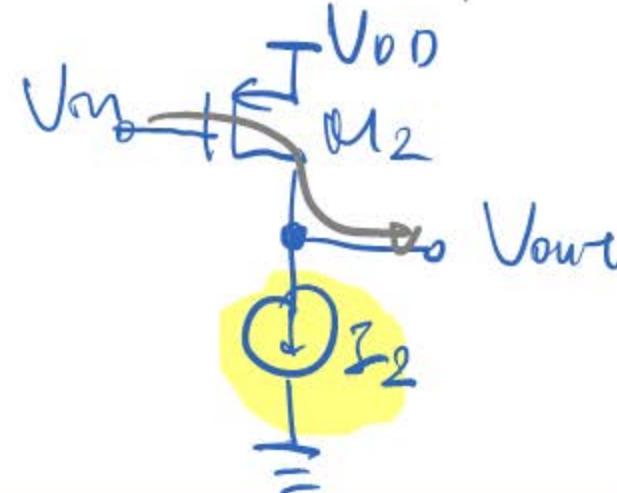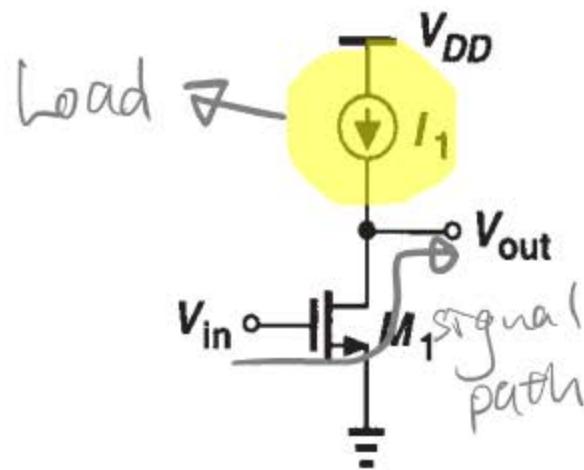Example

Assuming M_1 in saturation, calculate its small-signal gain. (analytical form)



Solution:

- Small-signal Analysis:

$$A_v = \frac{V_{out}}{V_{in}} = -gm_1 r_{o1} \rightarrow \infty$$



- DC Analysis:

$$I_1 \neq \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{TH})^2 \rightarrow V_{out} \text{ undefined. (floating)}$$


Example

Assuming M_1 in saturation, calculate its small-signal gain.


入キ〇
トキ〇

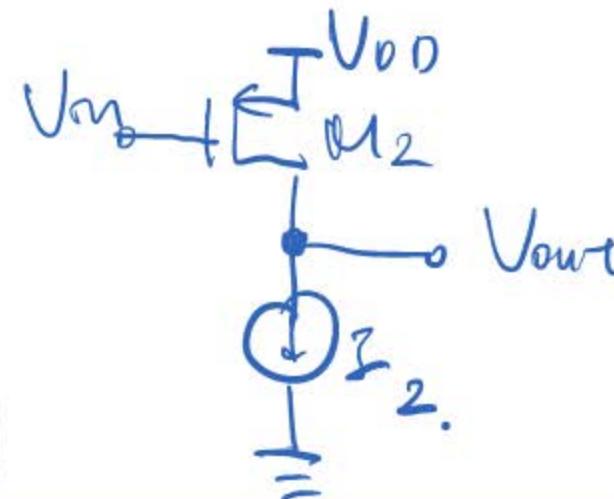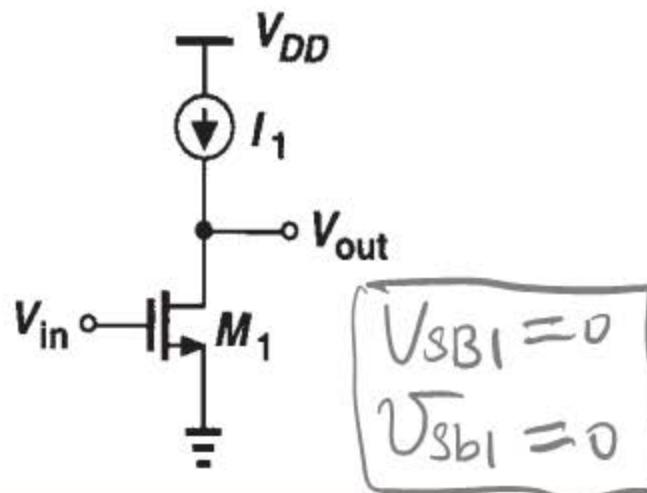

Solution:

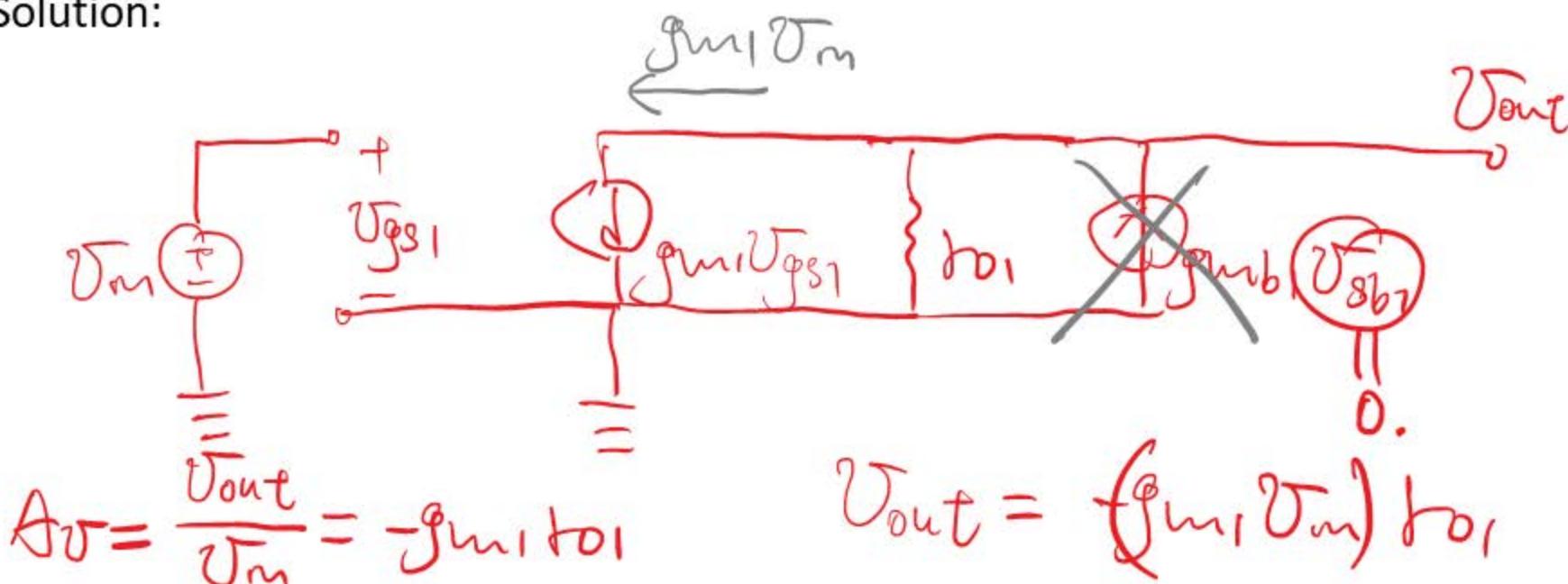

$\tau \neq 0$
 $r \neq 0$

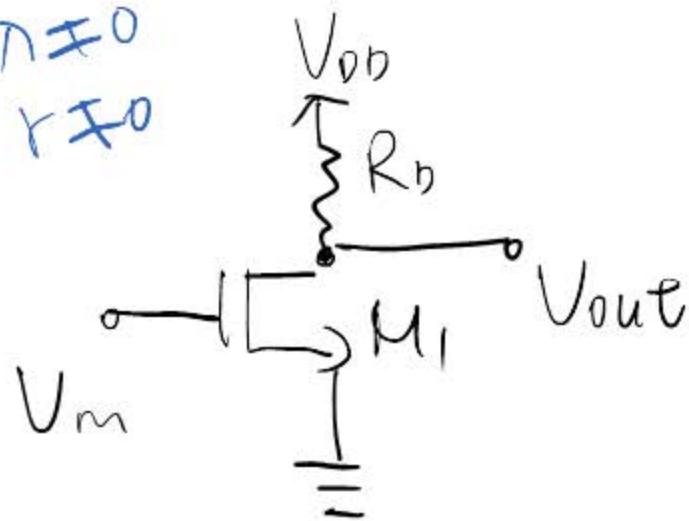


Find out the analytical
expressions for A_V , R_m
and R_{out} ?

$$A_V = -g_m (R_D \parallel R_D)$$

2° $R_{out} = ?$


- a. In small-signal circuit, turn V_m off.
- b. Put a test small-signal (V_t) at the output.
- c. Calculate small-signal current (δI) flowing into output.
- d. $R_{out} = V_t / \delta I$

$\tau \neq 0$
 $r \neq 0$

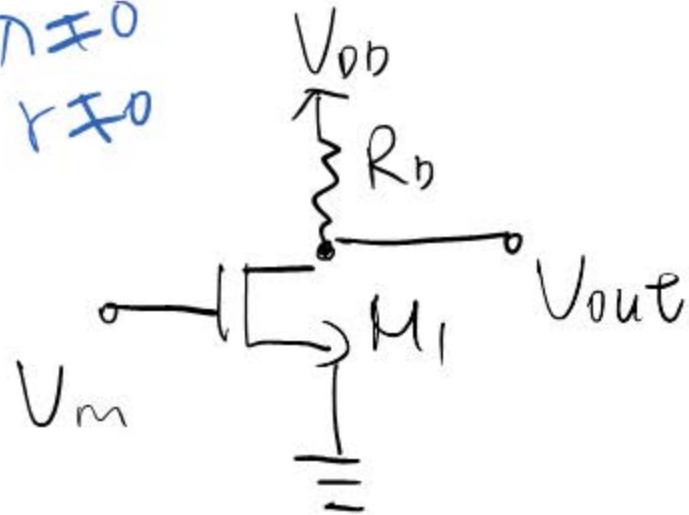


Find out the analytical
expressions for A_v , R_m
and R_{out} ?

$$2^{\circ} R_{out} = r_{o1} // R_D$$

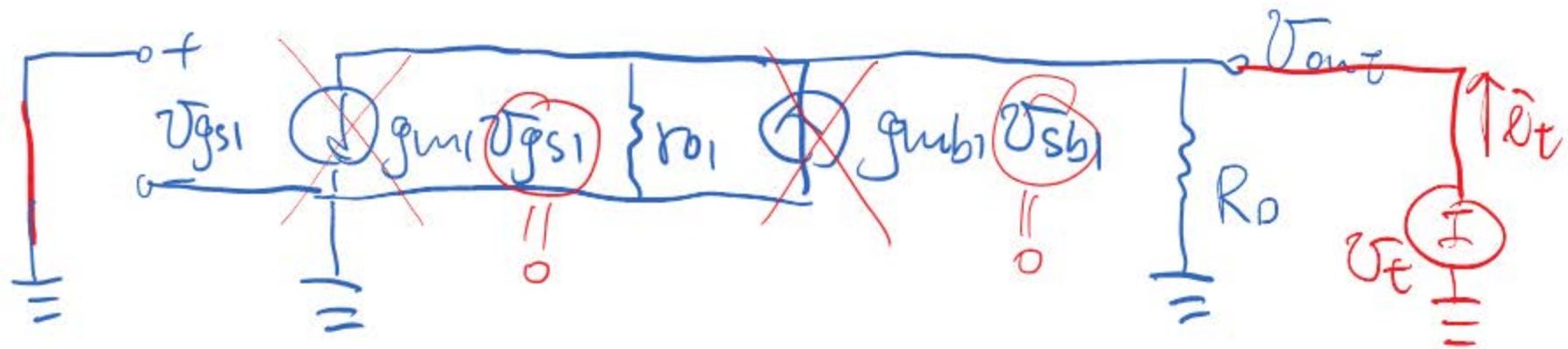


$\gamma \neq 0$
 $r \neq 0$

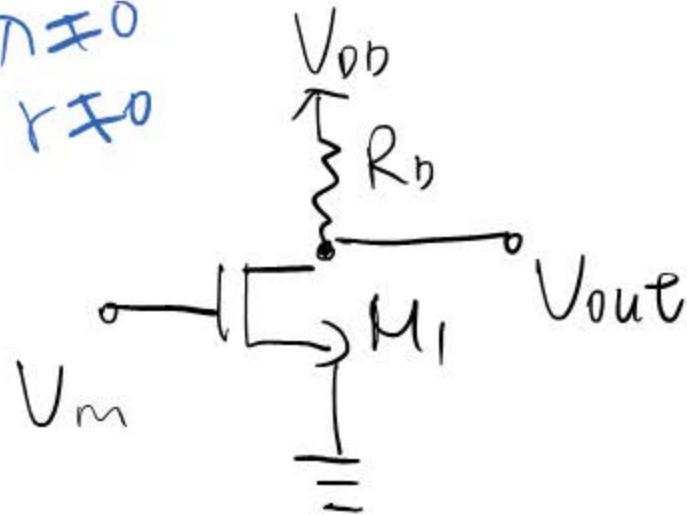


Find out the analytical
expressions for A_V , R_m
and R_{out} ?
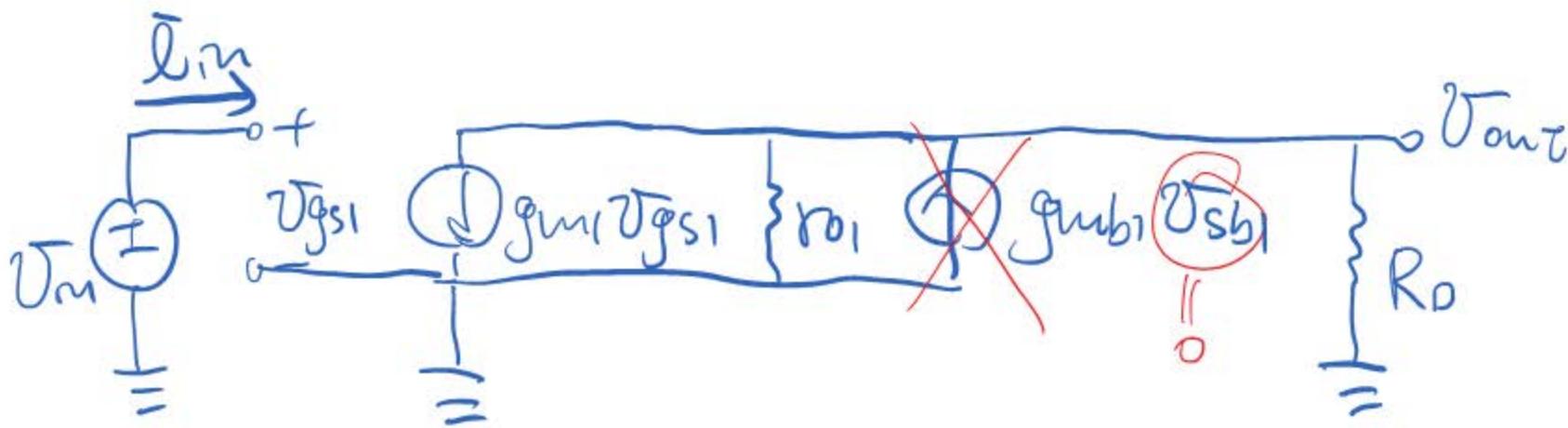
$$3^{\circ} R_m = \frac{V_m}{\delta m} = \infty$$




$$\gamma \neq 0$$

$$r \neq 0$$

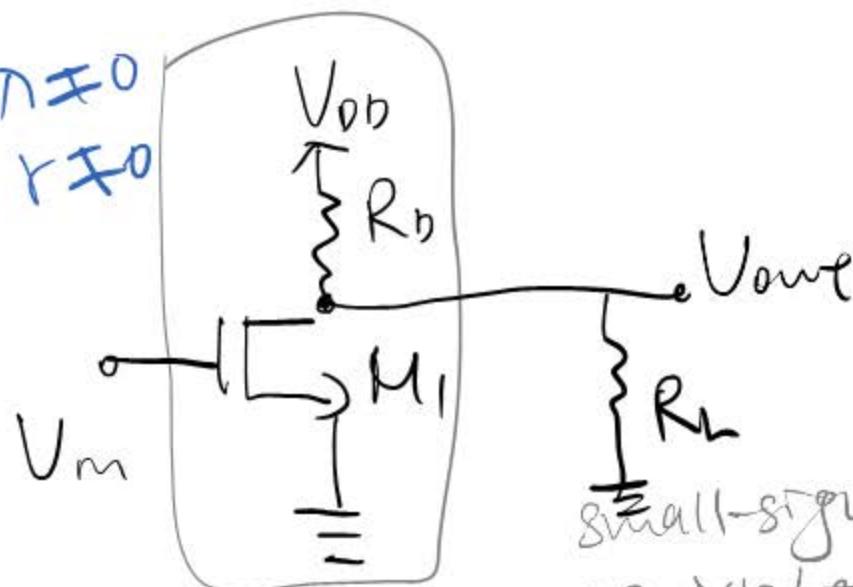


$$V_{out} = V_m A_v \frac{R_L}{R_{out} + R_L}$$



small-signal equivalent circuit.

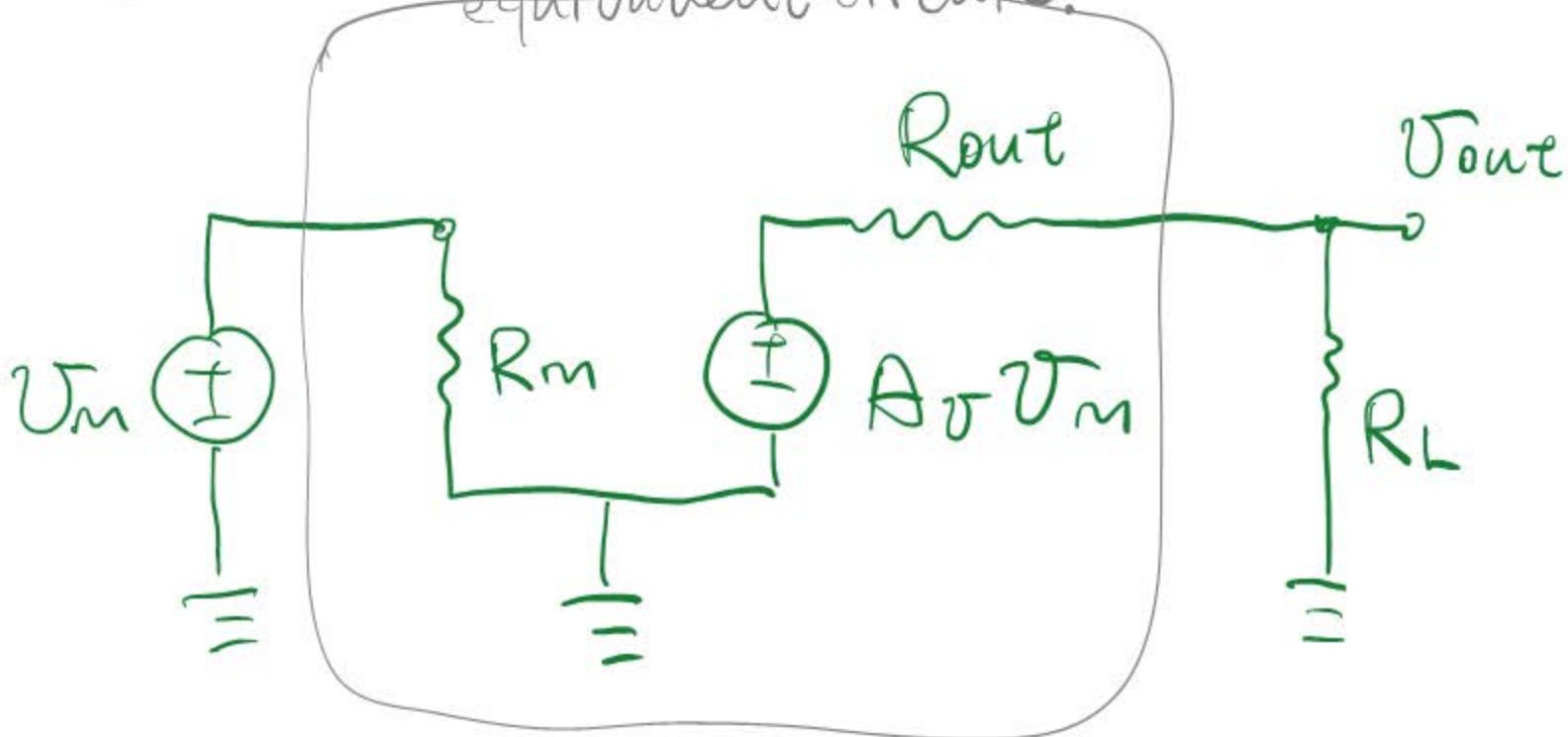


Common-Source with Diode-Connected Load

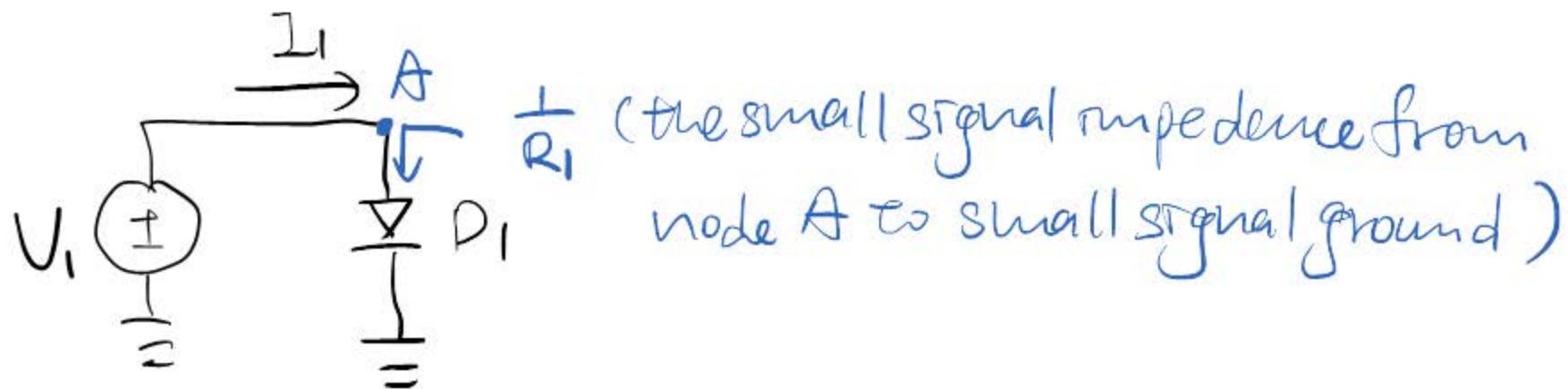

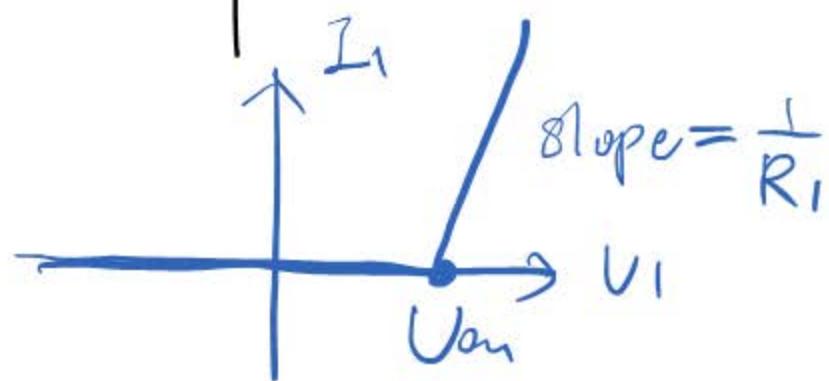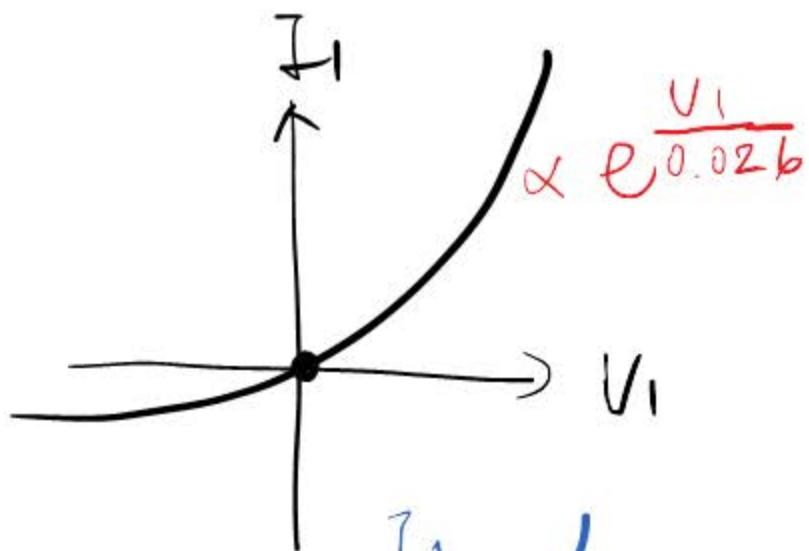
(the small signal impedance from node A to small signal ground)



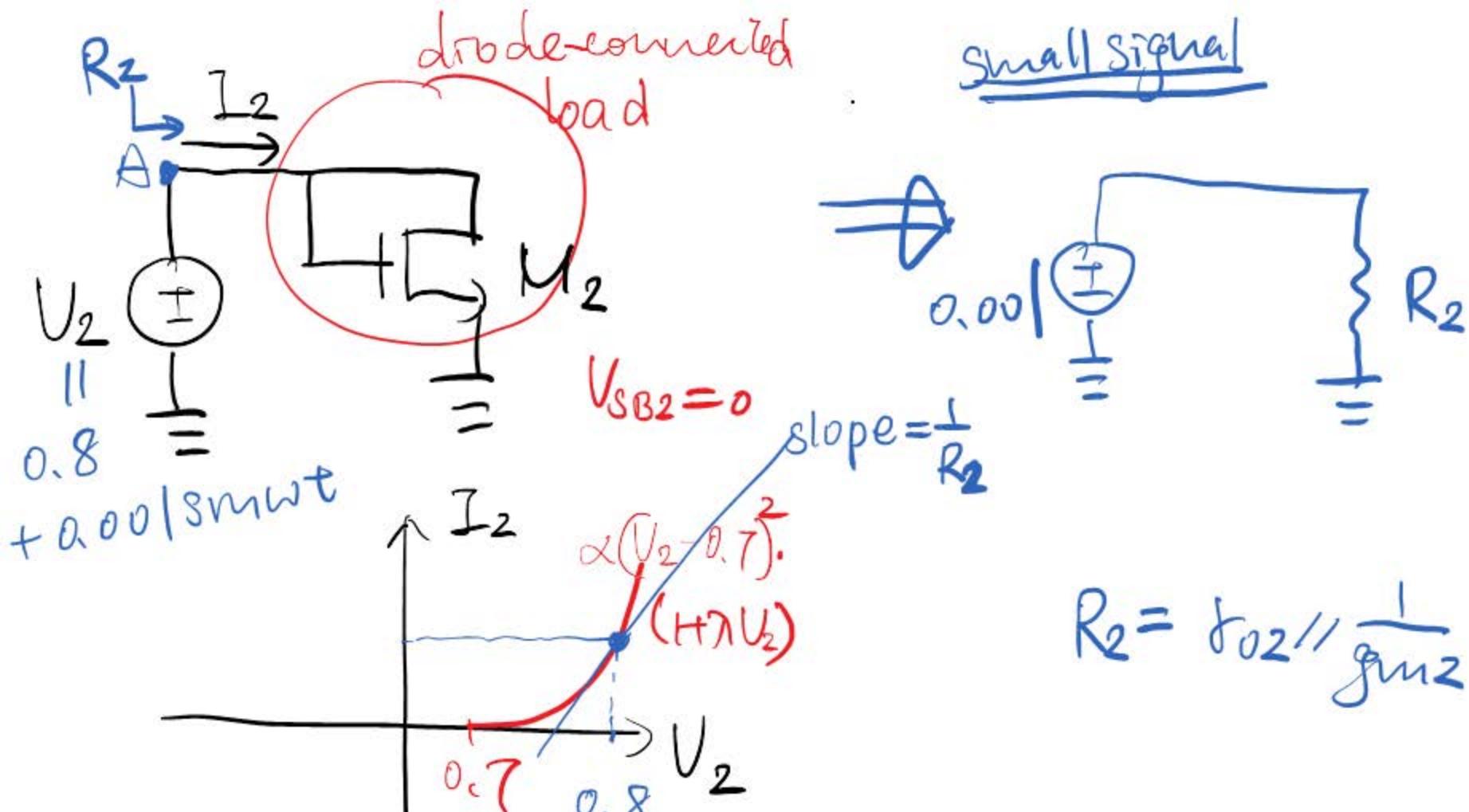

M_2 always in sat.

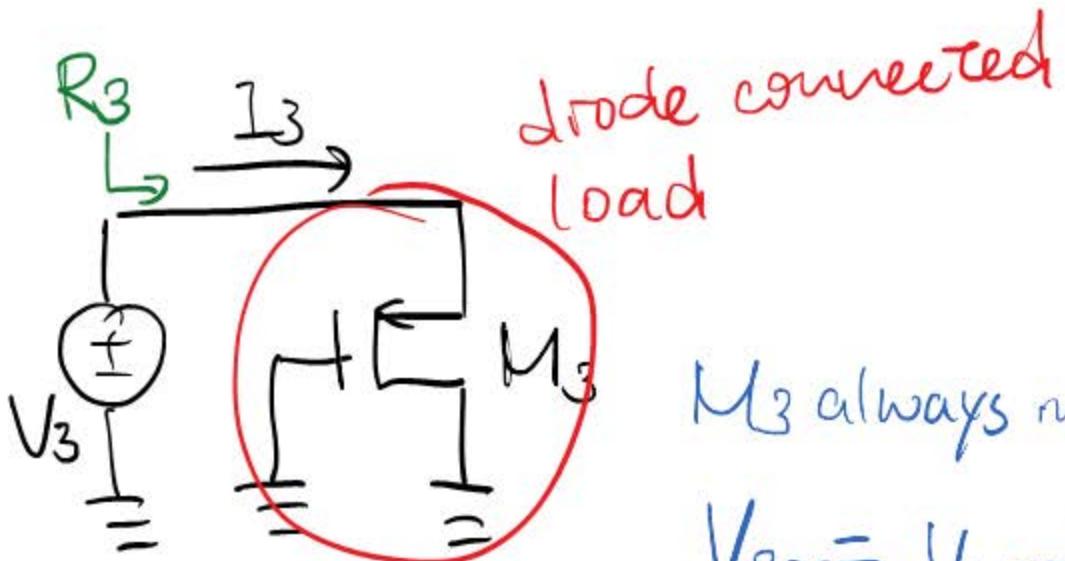
$$I_2 = \frac{1}{2} \mu_n C_o x \frac{\omega}{L_{eff}} (U_2 - 0.7)^2 (H\pi U_2)$$



$$R_3 = r_{o3} \parallel \left(\frac{1}{\mu_{n3} + \mu_{mb3}} \right)$$


M_3 always in Sat.

$$V_{BS3} = V_{DD} - V_3 > 0, |V_{TH3}| > 0.8$$

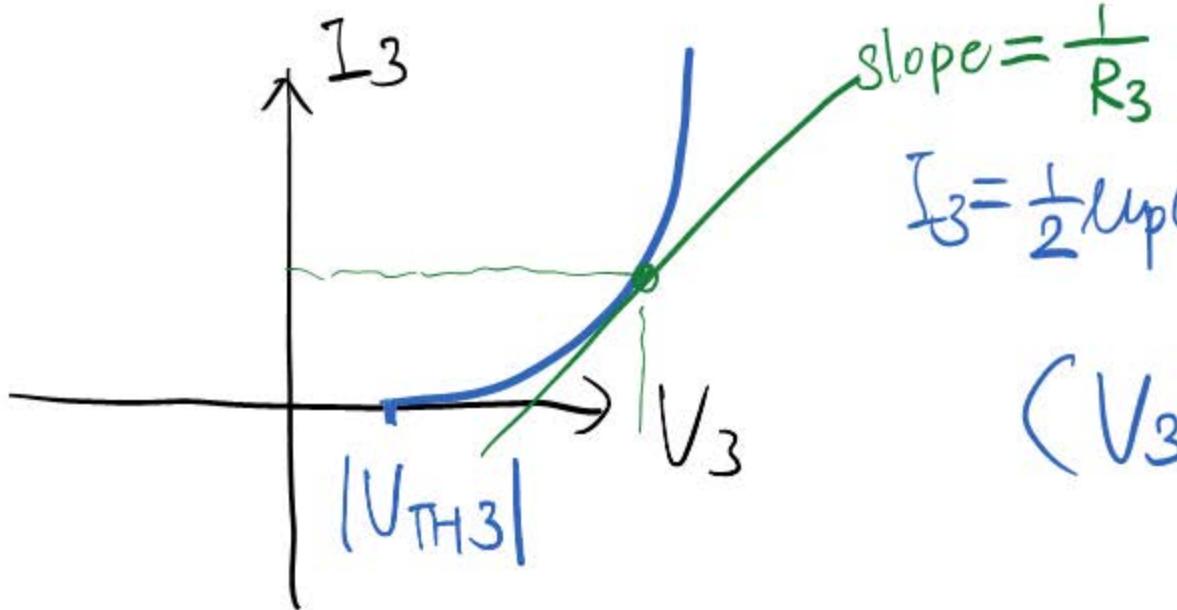



$$I_3 = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right)_3 \cdot$$

$$(V_3 - |V_{TH3}|)^2 (1 + \gamma V_3)$$

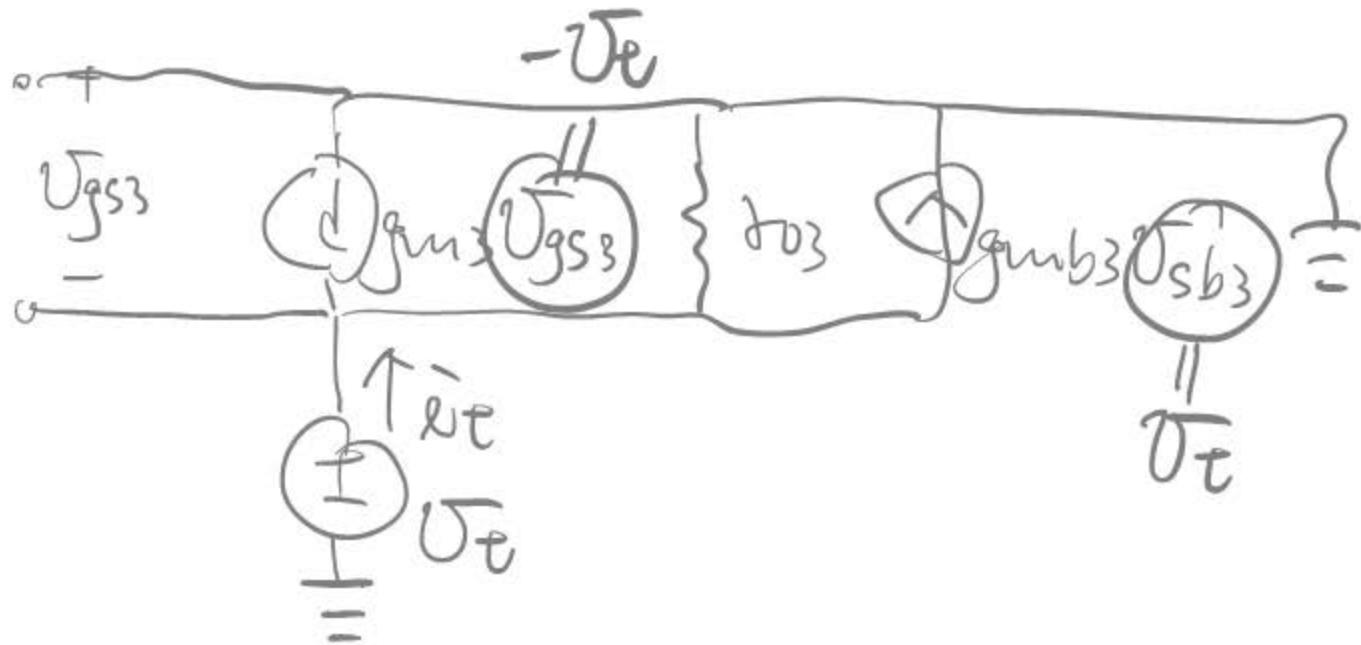



$$\dot{e}_t = (g_{m3} + g_{mb3})U_t + \frac{U_e}{r_{o3}}$$
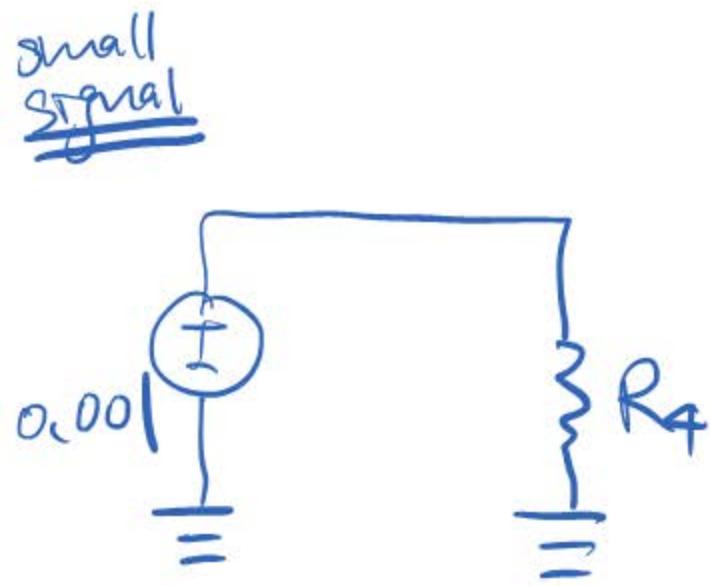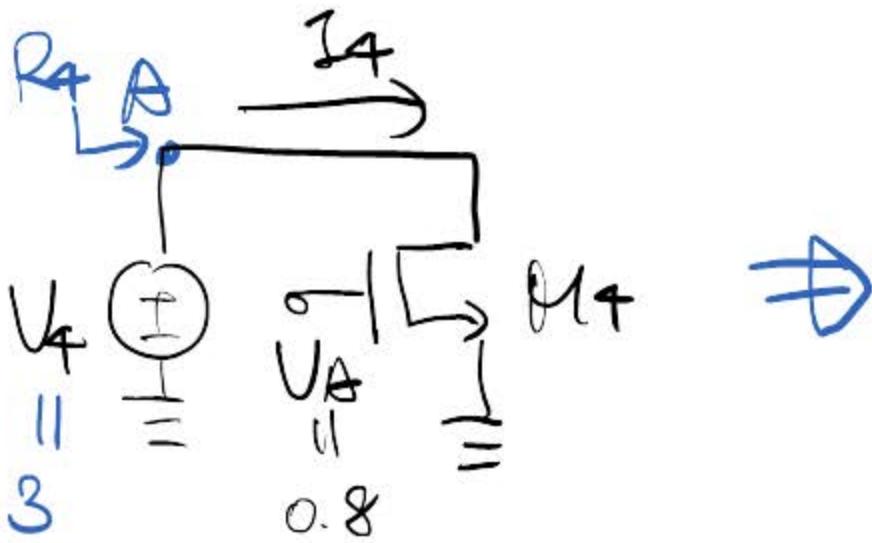
$$R_3 = U_e / \dot{e}_t = r_{o3} \parallel \left(\frac{1}{g_{m3} + g_{mb3}} \right)$$




+0.001smwt

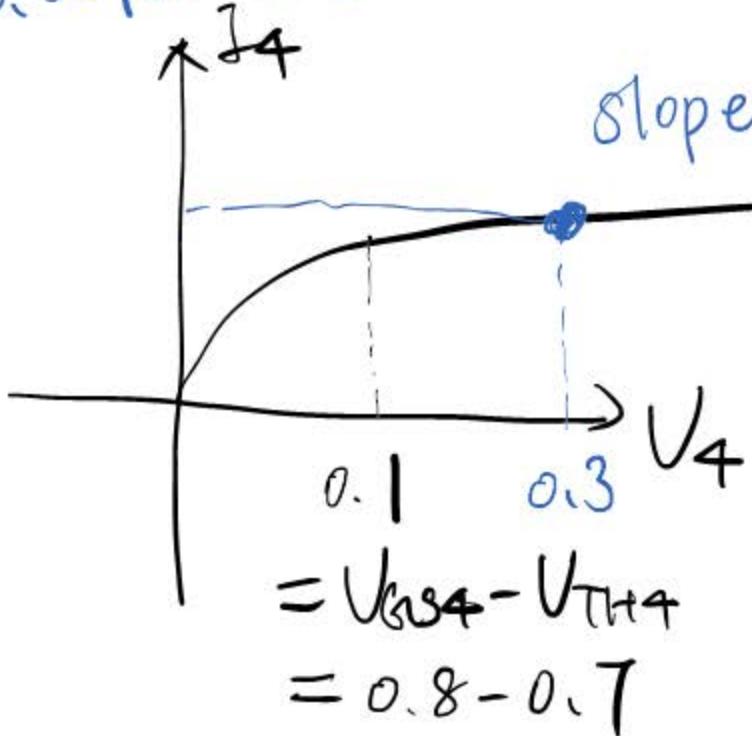


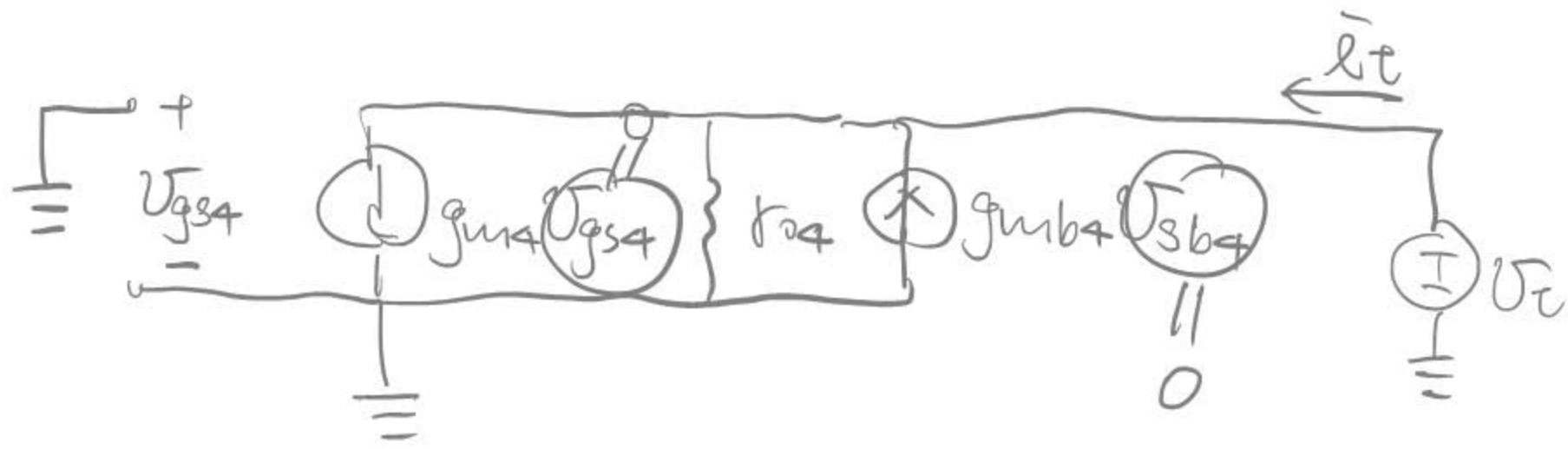


$$R_4 = \frac{U_e}{\bar{E}_e} = r_{o4}$$

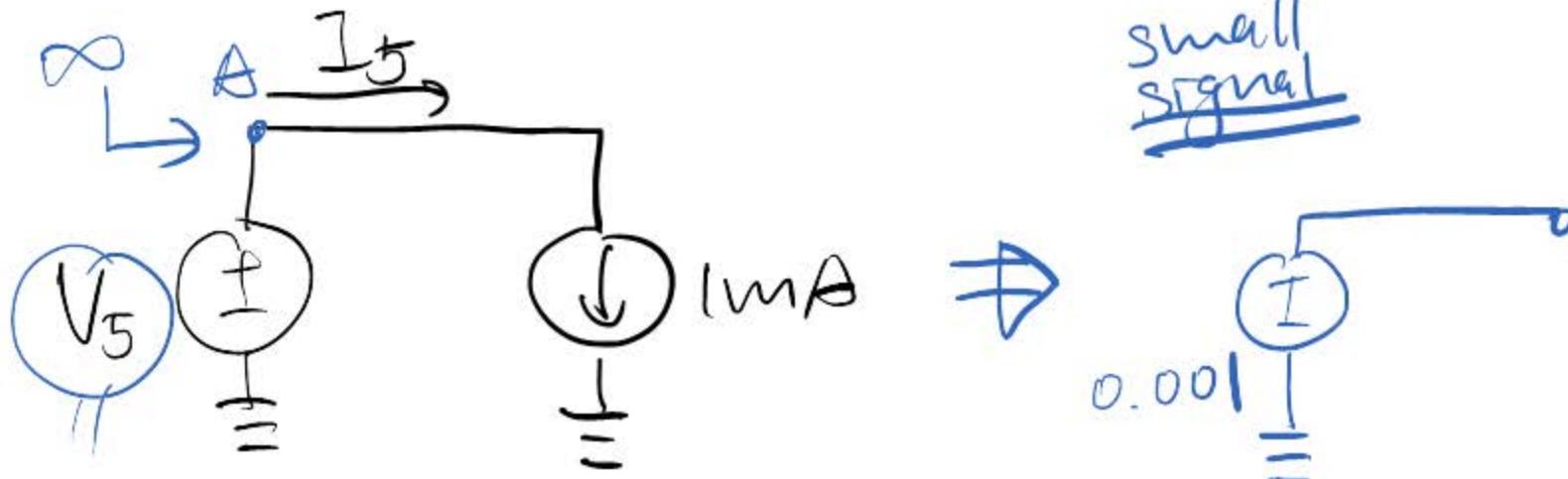


$$3 + 0.001 \text{SM} \omega t$$

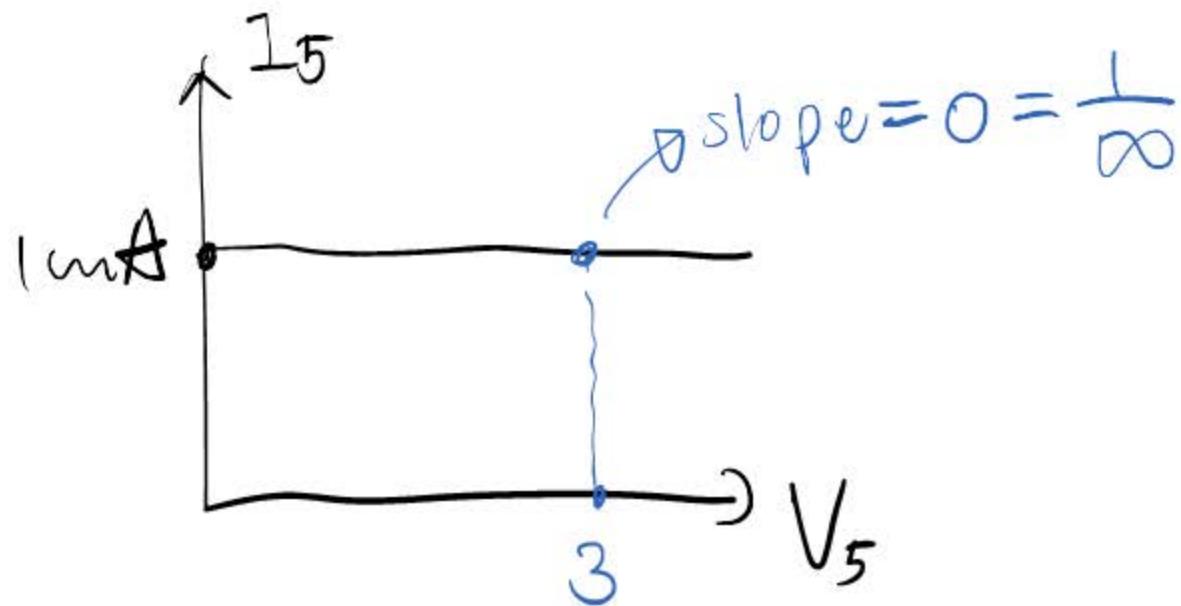

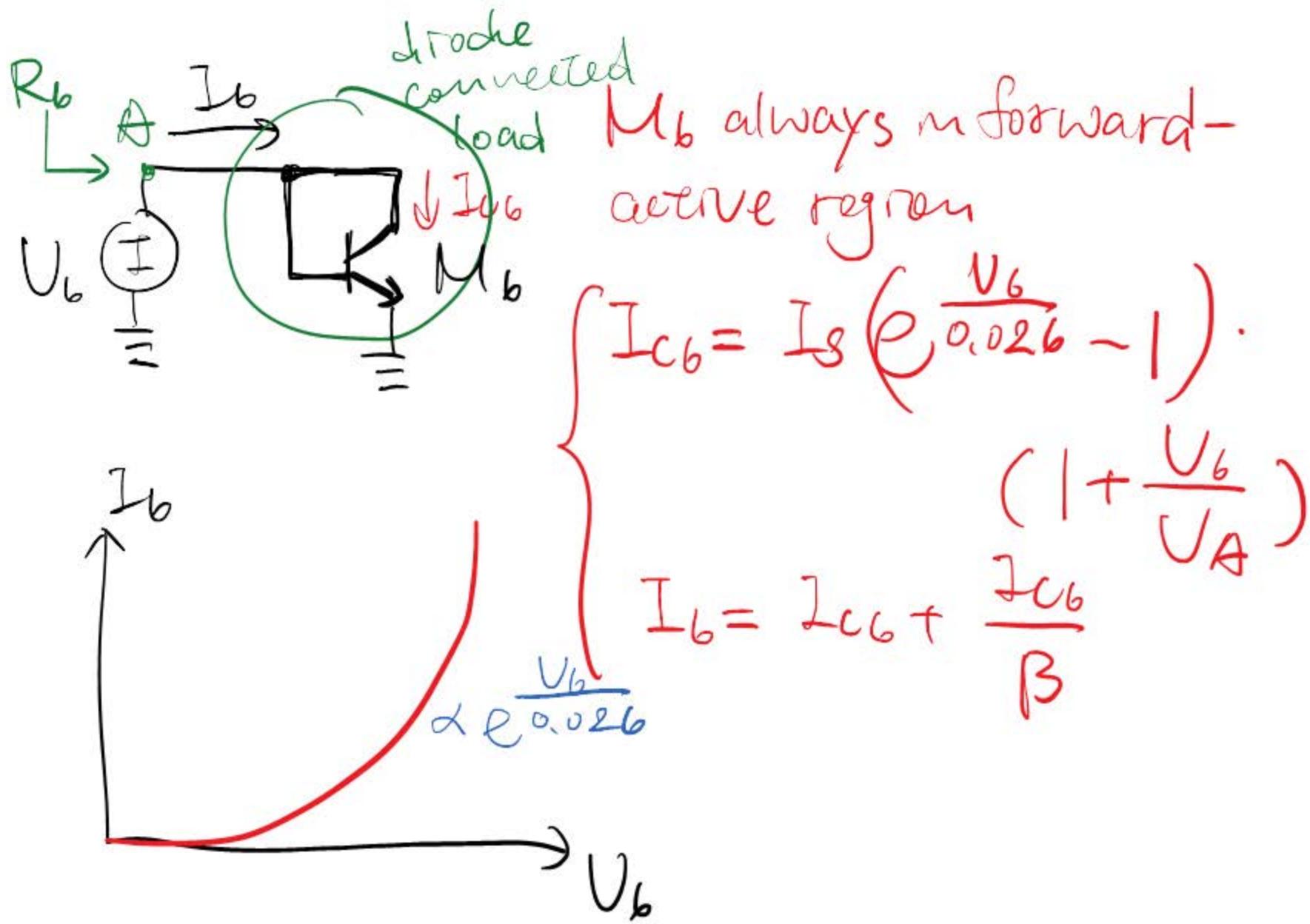



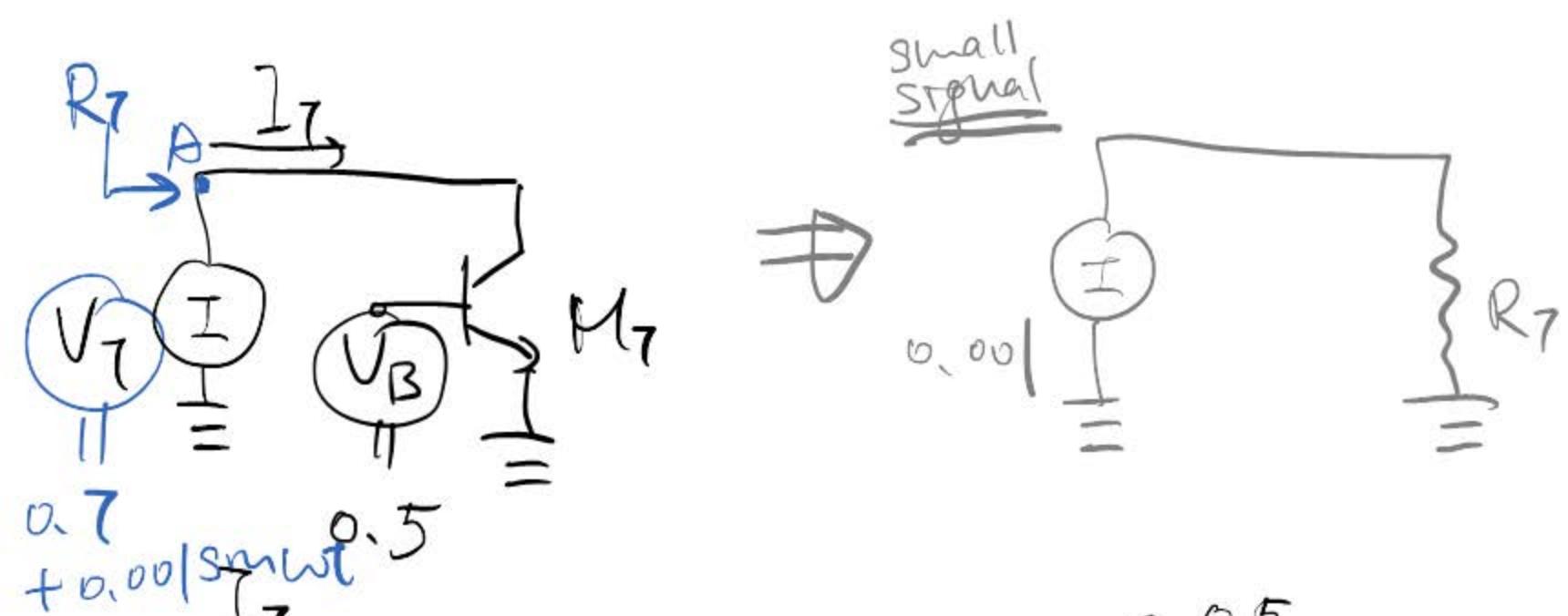
$$R_6 = \frac{U_e}{\partial t} = r_{T6} \parallel r_{o6} \parallel \frac{1}{g_{m6}}$$



$$0.7 + 0.001 \sin \omega t$$

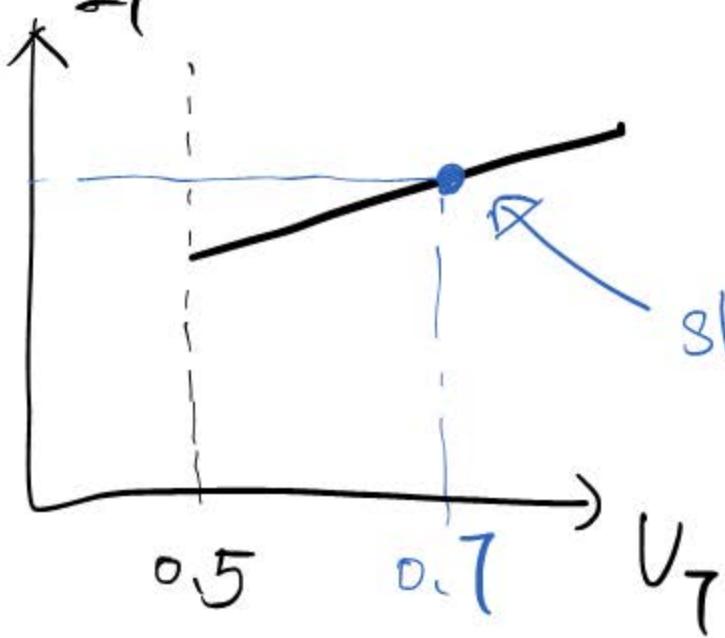


$$I_T = I_S \left(e^{\frac{V_T}{0.026}} - 1 \right) \left(1 + \frac{V_T}{U_A} \right)$$

$$\text{slope} = \frac{1}{R_T} = \frac{1}{r_{07}}$$




$$R_L = \frac{U_e}{\vec{I}_C} = R_o$$

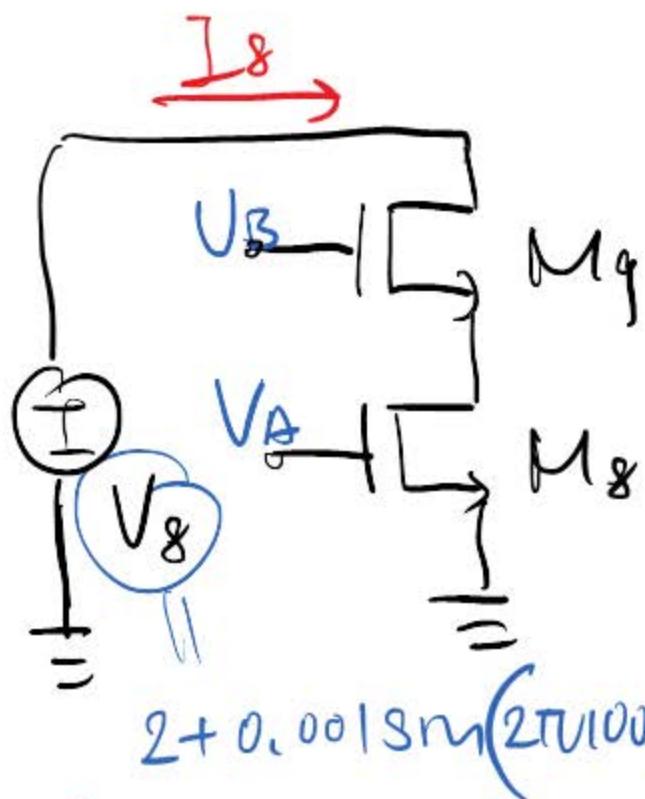


V_B and V_A are DC voltages properly chosen so that M_8, q are in the sat.

$$2 + 0.001 \sin(2\pi 100t)$$

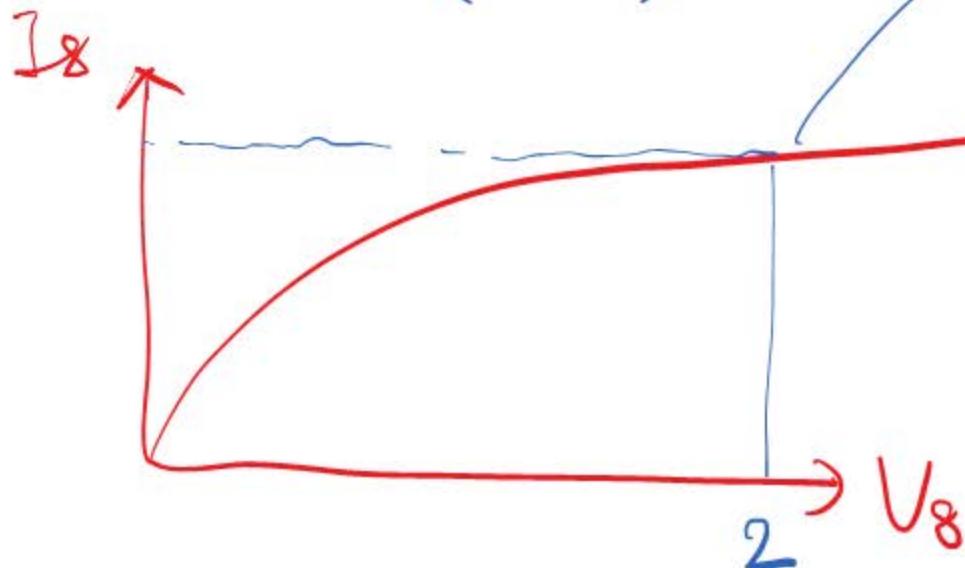

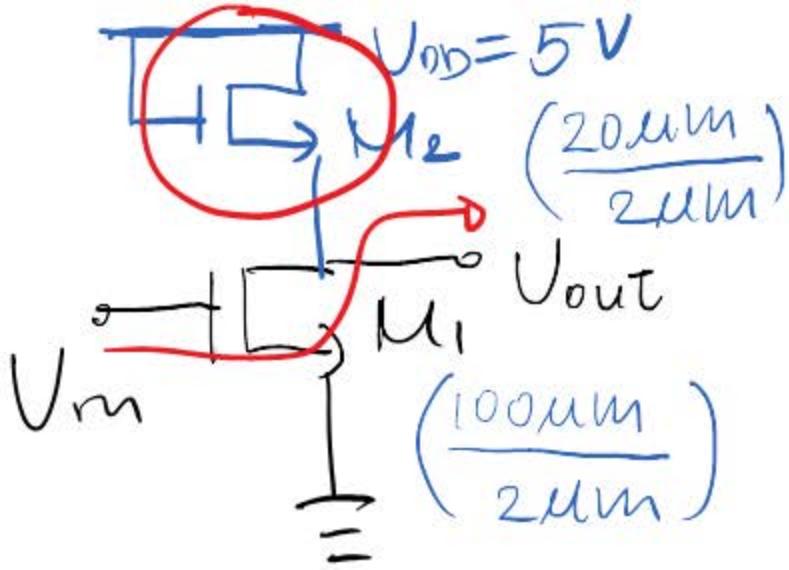slope = $\frac{1}{R_{08} + R_{0q} + (g_{m8} + g_{mbq})R_{0q} T_{08}}$



1° Find out $V_{OUT} = ?$

Then we make sure
 M_1 and M_2 in sat.

$$\frac{1}{2} \mu n C_o x \left(\frac{100\mu m}{2\mu m - 2LD} \right) (0.8 - 0.7)^2 \cdot (1 + \gamma V_{OUT})$$

$$\gamma \neq 0, \beta \neq 0$$

$$V_m = 0.8 + 0.0018m(2\pi f_{OFT})$$

$$V_{out} = V_{OUT} + V_{out} = ?$$





$$= \frac{1}{2} \mu n C_o x \left(\frac{20\mu m}{2\mu m - 2LD} \right) \cdot$$


$$(5 - V_{OUT} - V_{TH1})^2$$

$$[1 + \gamma(5 - V_{OUT})]$$

$$V_{SB1} = 0 \Rightarrow V_{TH1} = 0.7$$
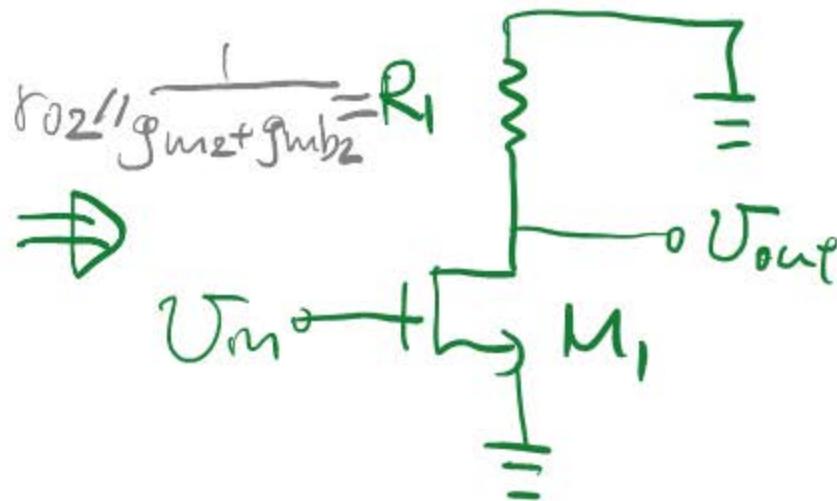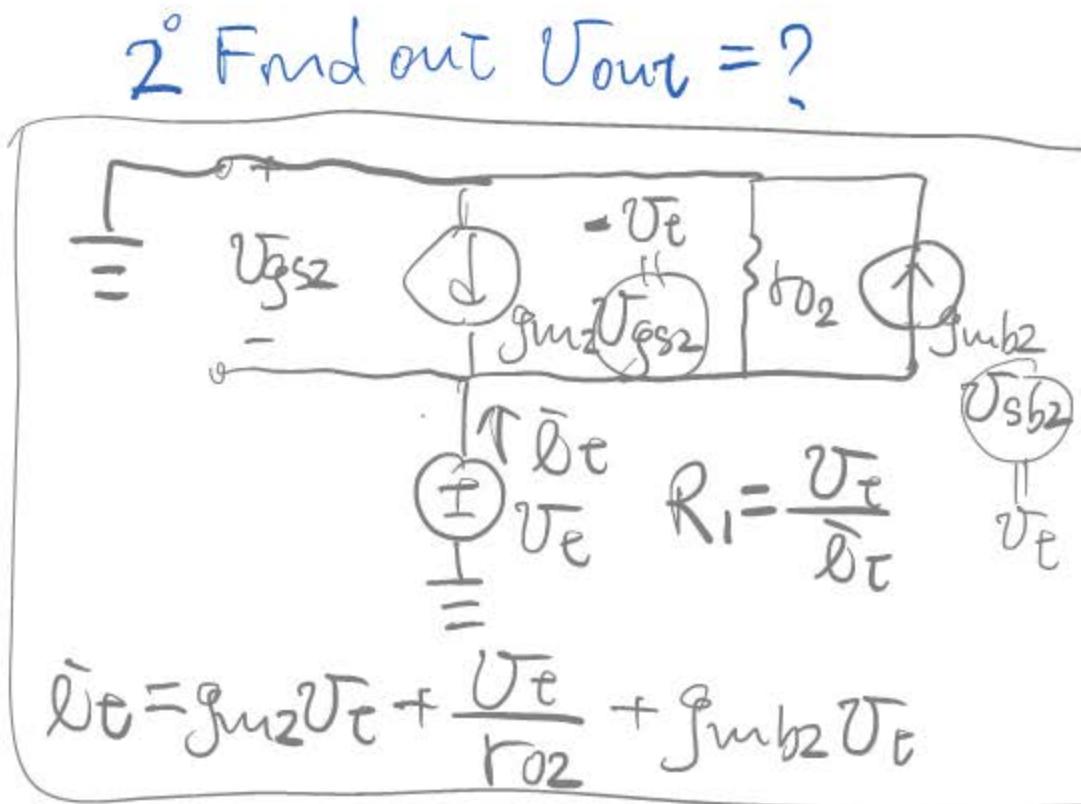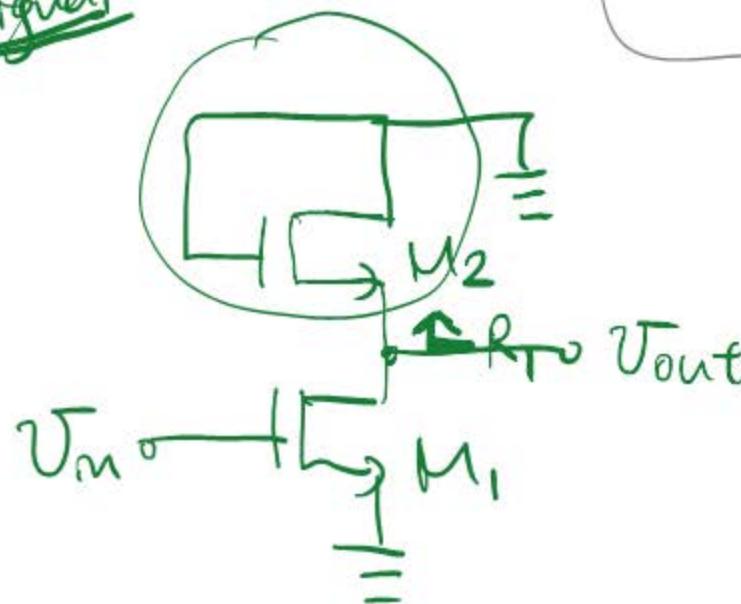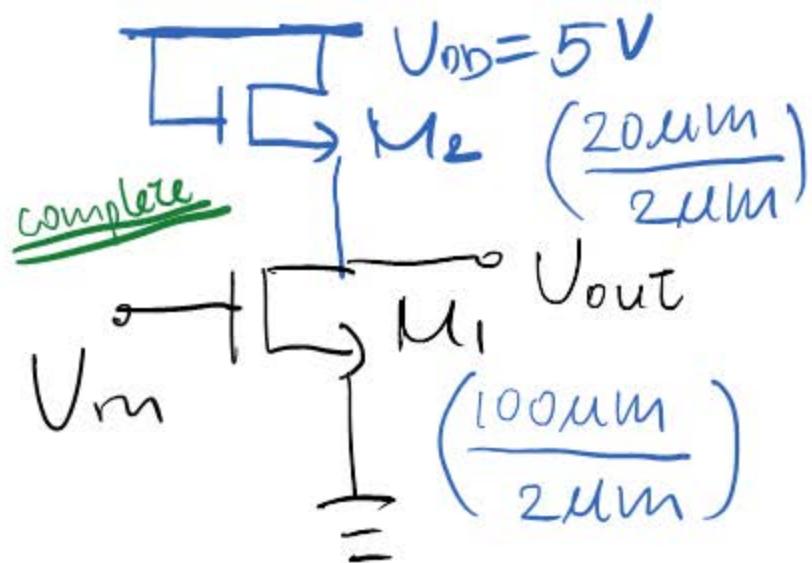
$$V_{SB2} = V_{OUT} \Rightarrow V_{TH2} > 0.7$$



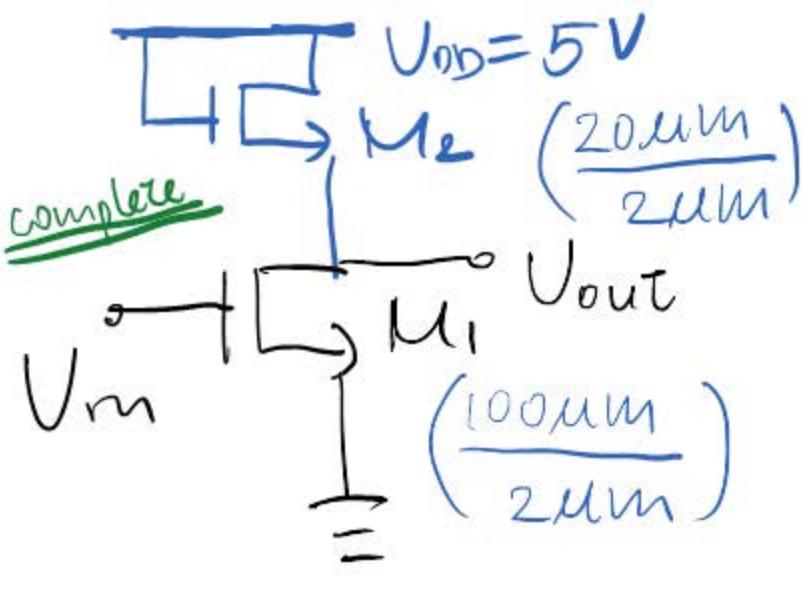



2^o Find out $V_{out} = ?$


$$V_{out} = -g_{m1} V_{in} (r_{o1} // R_1)$$

$$= -g_{m1} V_{in} \left(r_{o1} // r_{o2} // \frac{1}{g_{m2} + g_{mb2}} \right)$$

$$\cong -g_{m1} V_{in} \frac{1}{g_{m2} + g_{mb2}} \stackrel{\text{P}}{\cong} -V_{in} \frac{g_{m1}}{g_{m2}}$$

small-signal

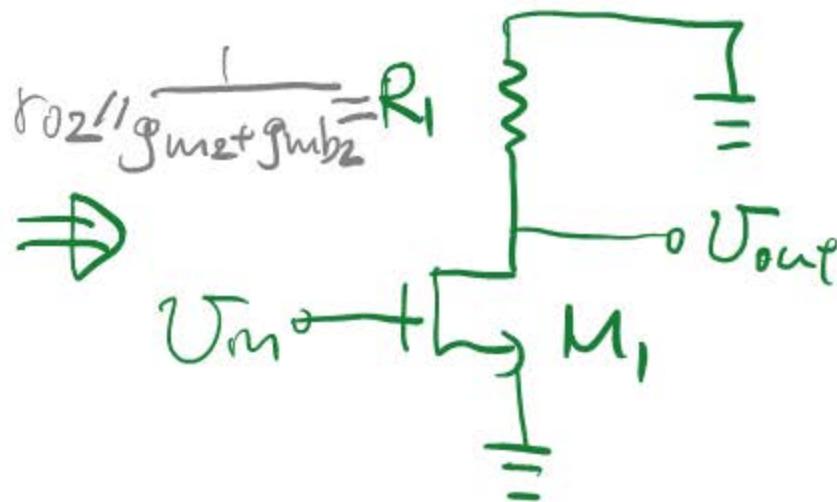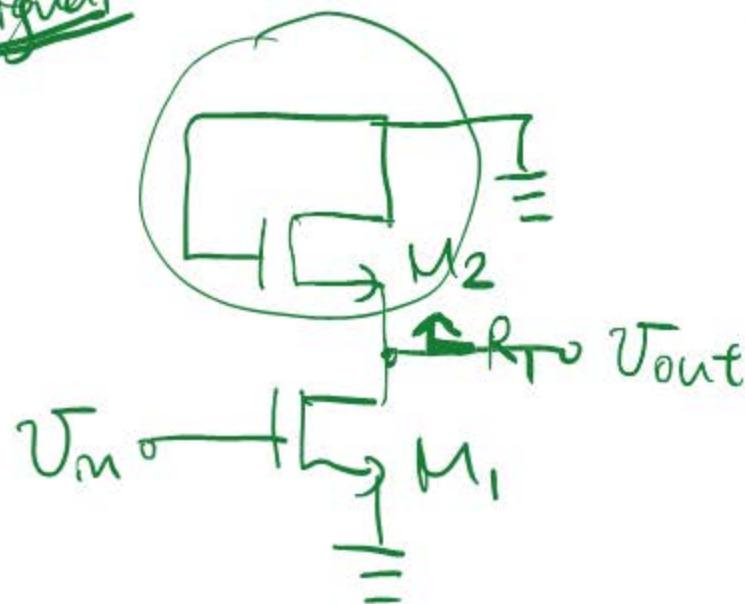


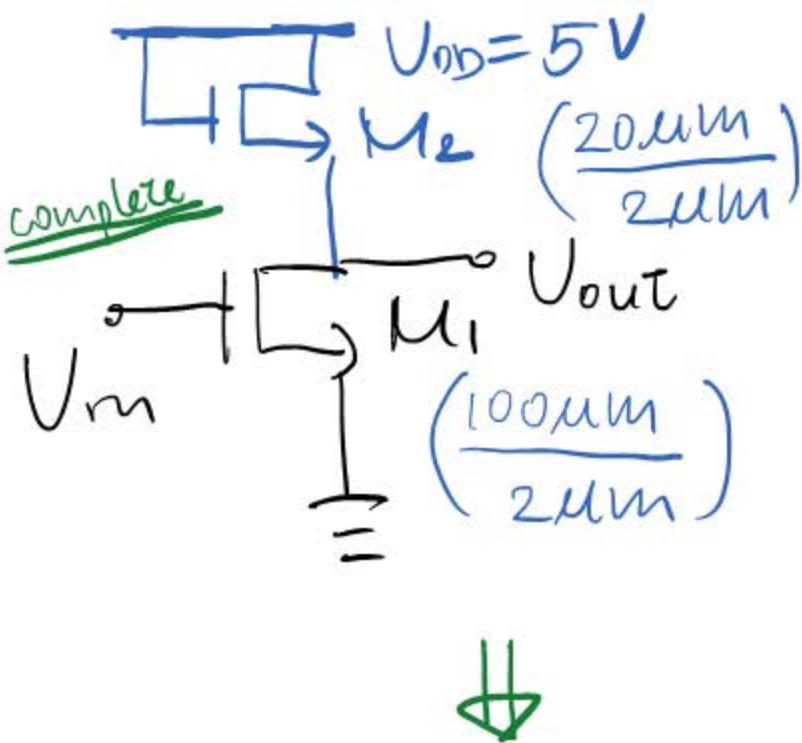

2^o Find out $V_{out} = ?$

$$V_{out} = -g_{m1} V_{in} (r_{o1} // R_1)$$
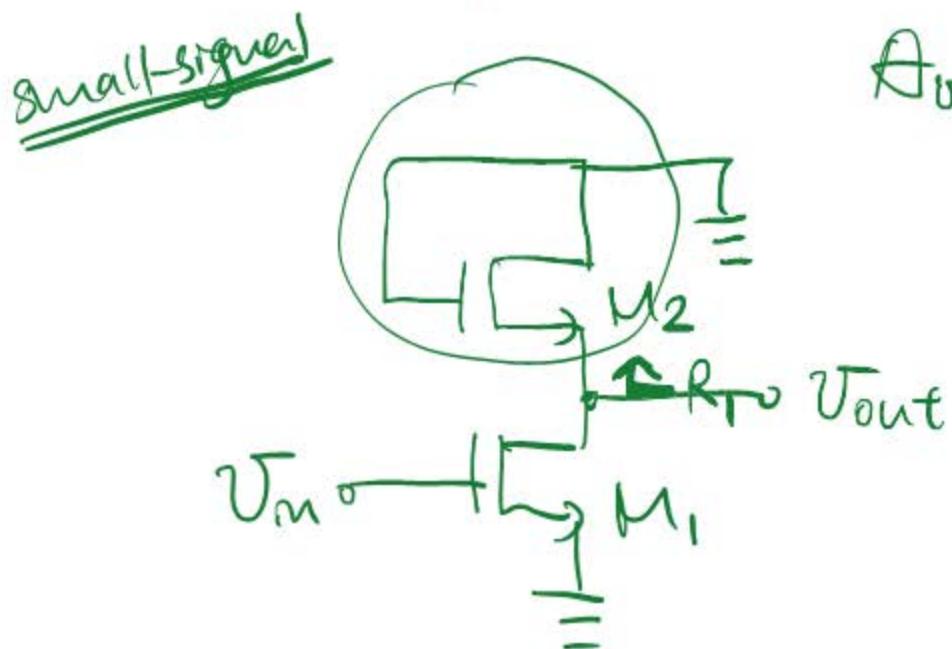
$$= -g_{m1} V_{in} \left(r_{o1} // r_{o2} // \frac{1}{g_{m2} + g_{mb2}} \right)$$




$$A_v = \frac{V_{out}}{V_{in}}$$

$$= g_{m1} \left(r_{o1} // r_{o2} // \frac{1}{g_{m2} + g_{mb2}} \right)$$

(if $\pi = 0, \gamma \neq 0$)

$$= - \frac{g_{m1}}{g_{m2} + g_{mb2}\gamma} = - \frac{g_{m1}}{g_{m2}} \left(\frac{1}{1 + \gamma} \right)$$

small-signal

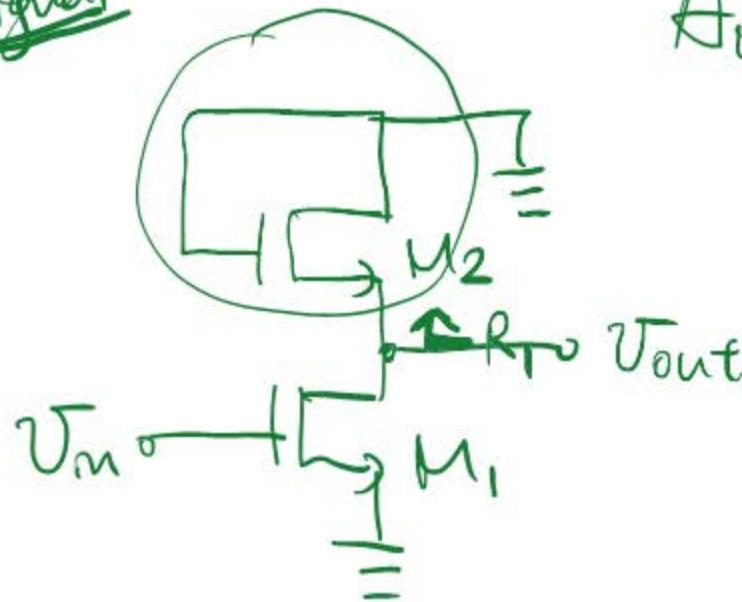

$$A_V = \frac{V_{out}}{V_m}$$

$$= g_{m1} \left(r_o / (r_o + r_s) \parallel \frac{1}{g_{m2} + g_{mb2}} \right)$$

(if $\eta = 0, r \neq 0$)

$$= - \frac{g_{m1}}{g_{m2} + g_{m2}\eta} = - \frac{g_{m1}}{g_{m2}} \left(\frac{1}{1 + \eta} \right)$$

$$= - \frac{\sqrt{2} \mu_n C_{ox} (\frac{W}{L_{eff}})_1 \frac{1}{R_1}}{\sqrt{2} \mu_p C_{ox} (\frac{W}{L_{eff}})_2 \frac{1}{R_2}} \left(\frac{1}{1 + \eta} \right)$$


$$= - \frac{(\frac{W}{L_{eff}})_1 \left(\frac{1}{1 + \eta} \right)}{(\frac{W}{L_{eff}})_2 \left(\frac{1}{1 + \eta} \right)}$$

Common-Source with Diode-Connected Load

40

DC Analysis

$$\lambda = 0 \quad \gamma \neq 0$$

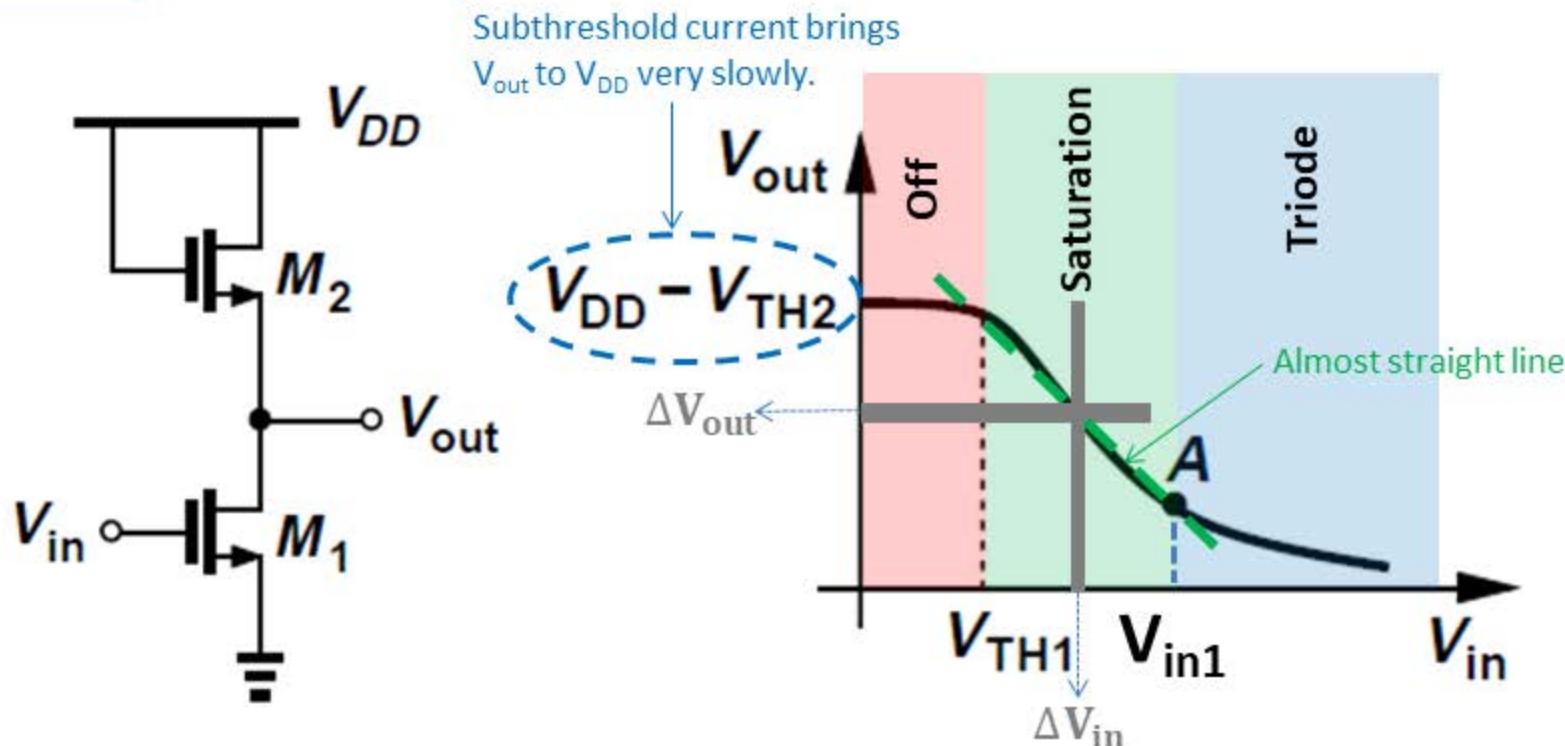

$$V_{out} = V_{in1} - V_{TH1}$$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in1} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 [V_{DD} - (V_{in1} - V_{TH1}) - V_{TH2}]^2$$

- V_{gs} increases by $\Delta V_{in} \rightarrow I_d$ increases by $\Delta V_{in} \cdot gm \rightarrow V_{out}$ decreases

Common-Source with Diode-Connected Load

DC Analysis

$$\lambda = 0 \quad \gamma \neq 0$$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1 \text{ in Saturation}$

$$\frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_1 (V_{in} - V_{TH1})^2 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L} \right)_2 [V_{DD} - V_{out} - V_{TH2}]^2$$

$$\sqrt{\left(\frac{W}{L} \right)_1} (V_{in} - V_{TH1}) = \sqrt{\left(\frac{W}{L} \right)_2} (V_{DD} - V_{out} - V_{TH2})$$

$$\sqrt{\left(\frac{W}{L} \right)_1} = \sqrt{\left(\frac{W}{L} \right)_2} \left(-\frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH2}}{\partial V_{in}} \right)$$

$$V_{out} = U_{SB2}$$

$$\sqrt{\left(\frac{W}{L} \right)_1} = \sqrt{\left(\frac{W}{L} \right)_2} \left(-\frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH2}}{\partial V_{out}} \frac{\partial V_{out}}{\partial V_{in}} \right) \\ = \eta = \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}}$$



$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$

- η is a function of V_{SB} .
- A_v is almost linear for M_1 in saturation.


Common-Source with Diode-Connected Load

Small-signal Analysis

$$\lambda = 0 \quad \gamma \neq 0$$

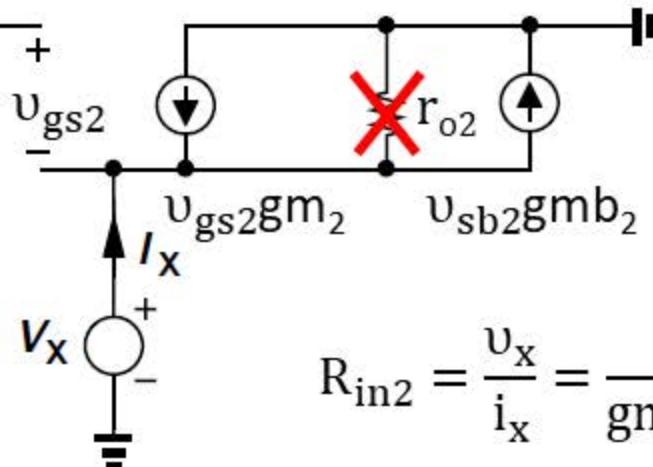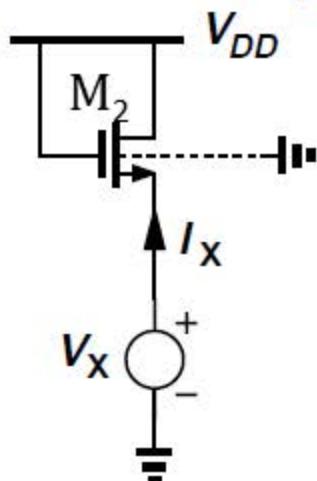
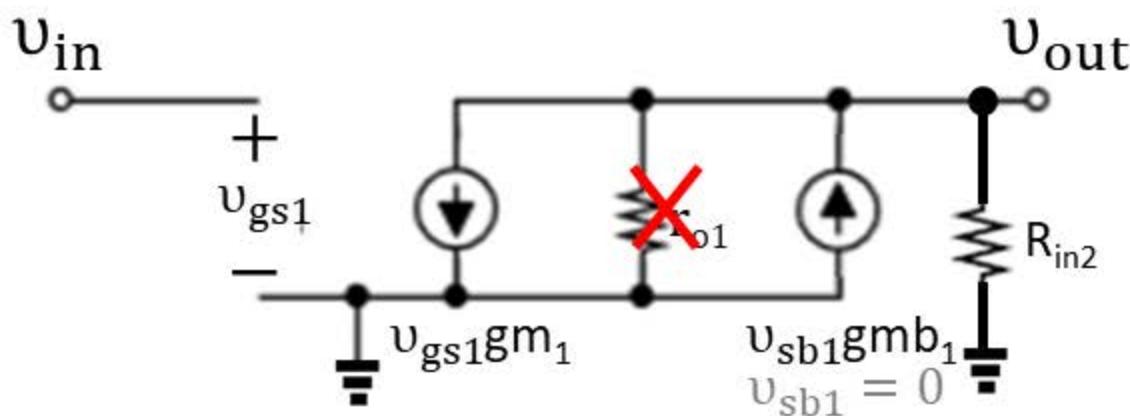
$$R_{in2} = \frac{v_x}{i_x} = \frac{1}{gm_2 + gmb_2}$$



$$A_v = \frac{v_{out}}{v_{in}} = \frac{-gm_1}{gm_2 + gmb_2}$$


$$= -\sqrt{\frac{(W/L)_1}{(W/L)_2}} \frac{1}{1 + \eta}$$

- Small-signal analysis leads to the same result as DC analysis.


Common-Source with Diode-Connected Load

Small-signal
Analysis

$$\lambda \neq 0 \quad \gamma \neq 0$$

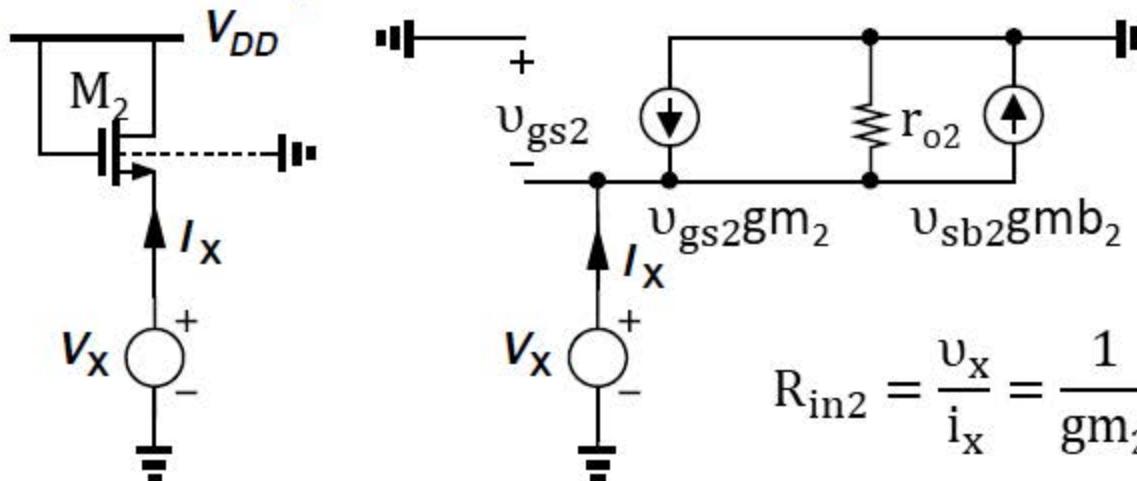
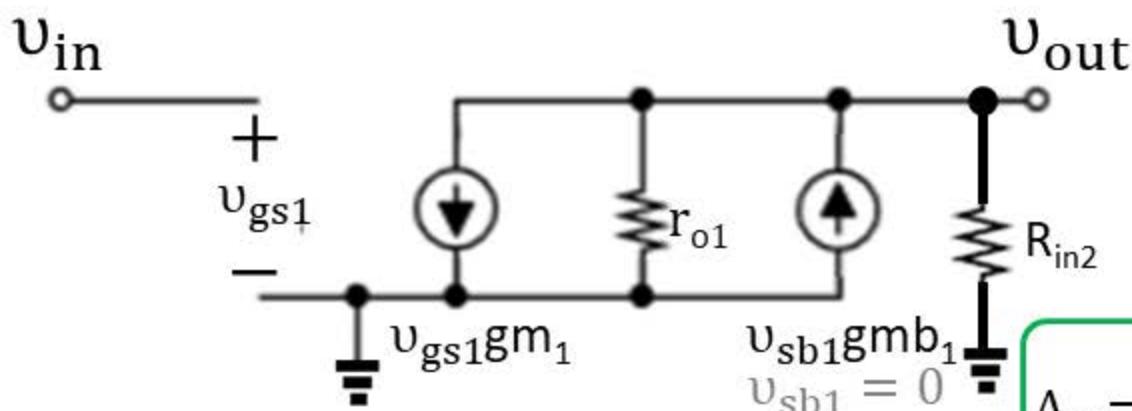
$$R_{in2} = \frac{v_x}{i_x} = \frac{1}{gm_2} \parallel \frac{1}{gmb_2} \parallel r_{o2}$$



$$v_{sb1} = 0$$

$$A_v = \frac{v_{out}}{v_{in}}$$


$$= -gm_1 \left(\frac{1}{gm_2} \parallel \frac{1}{gmb_2} \parallel (r_{o2} \parallel r_{o1}) \right)$$

$$r_o \gg 1/gm$$

Common-Source with Diode-Connected Load





Small-signal
Analysis

$$\lambda \neq 0 \quad \gamma \neq 0$$

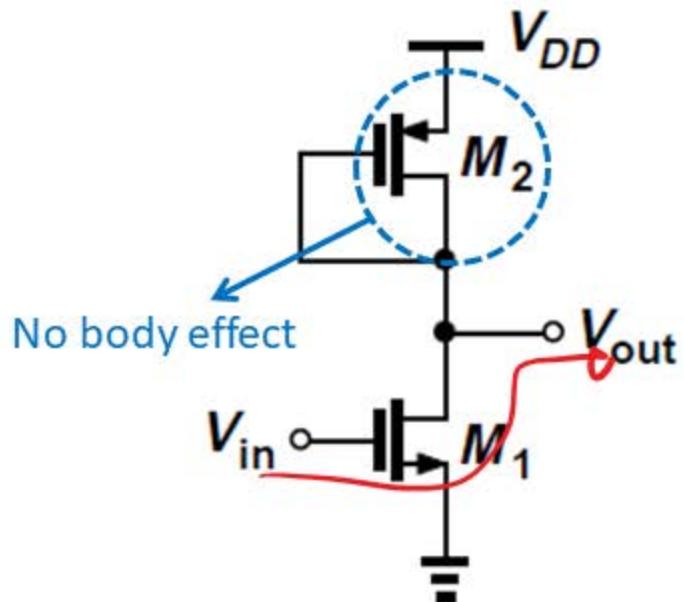

$$\begin{aligned}
 A_v &= \frac{V_{out}}{V_{in}} \\
 &= -gm_1 \left(\frac{1}{gm_2} \parallel r_{o2} \parallel r_{o1} \right) \\
 &\approx -\frac{gm_1}{gm_2} = \frac{-2L_m C_{ox} (W/L)_1}{2L_m C_{ox} (W/L)_2 + D_1} \\
 &= -\sqrt{\frac{\mu_n (W/L)_1}{\mu_p (W/L)_2}} \\
 &= -\frac{V_{SG2} - (V_{TH2})}{V_{GS1} - V_{TH1}} \quad \frac{2L_1}{\sqrt{V_{SG2} + V_{TH2}}} \\
 &\quad \frac{2L_2}{\sqrt{V_{SG2} + V_{TH2}}}
 \end{aligned}$$

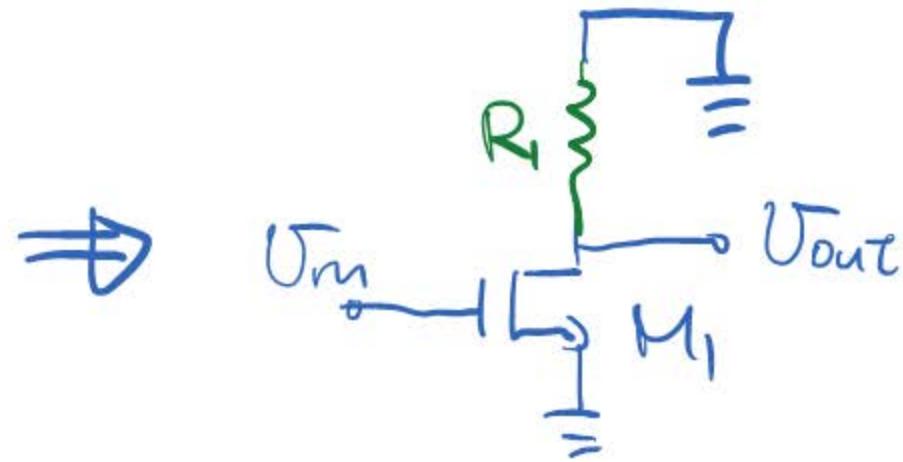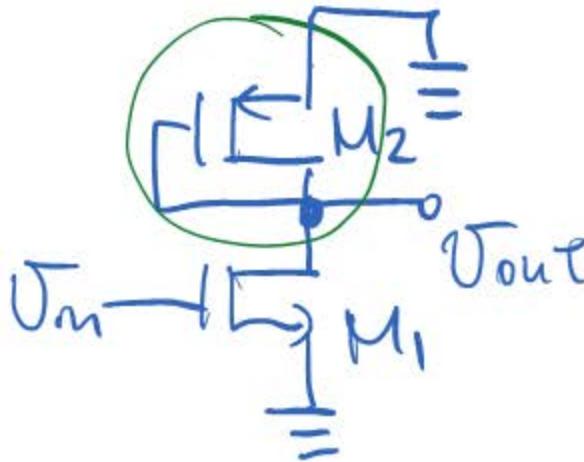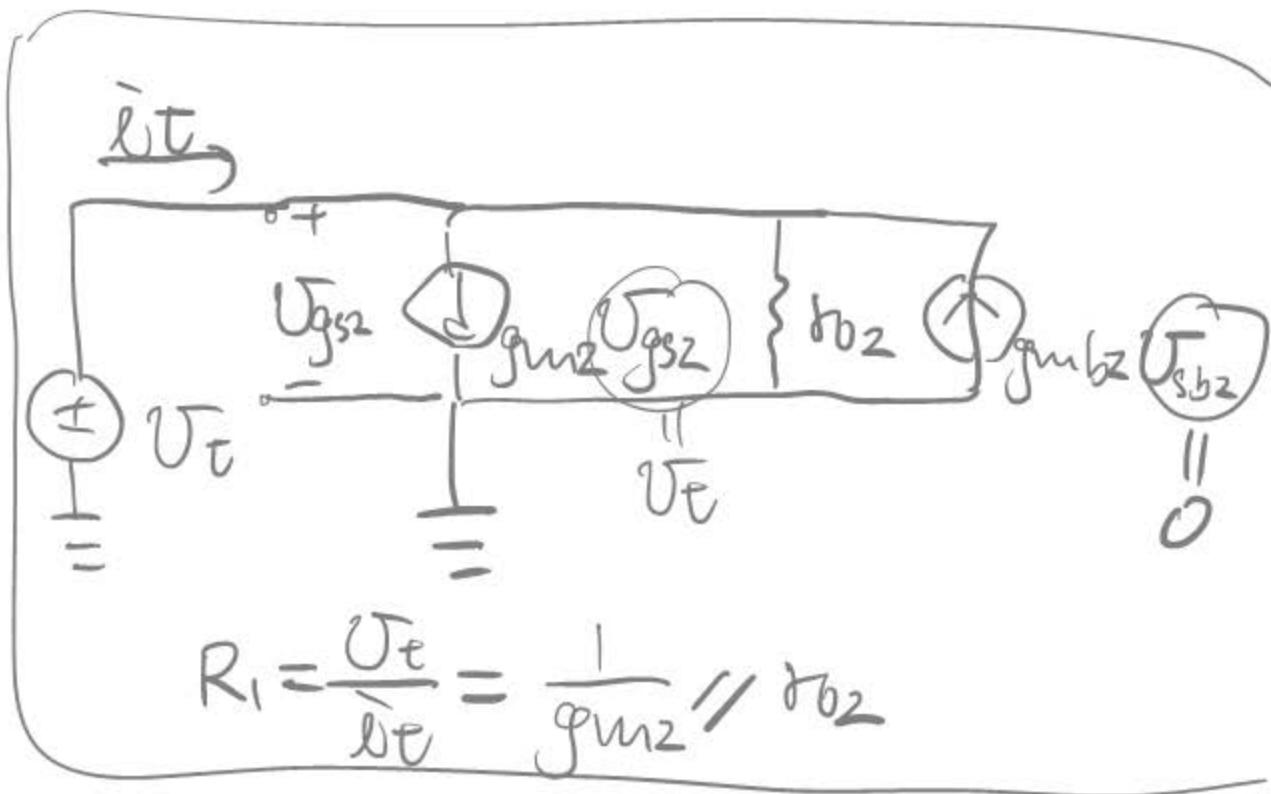
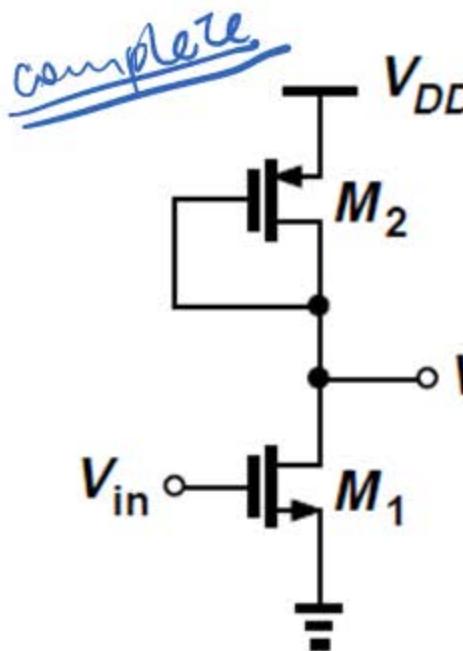
- For $A_v = 10$, $(W/L)_1 \gg (W/L)_2 \rightarrow$ Disproportionally large transistor
- For $A_v = 10$, $(V_{SG2} - V_{TH2}) = 10 \times (V_{GS1} - V_{TH1}) \rightarrow$ Limited output swing



$\lambda = 0$
 $T \neq 0$

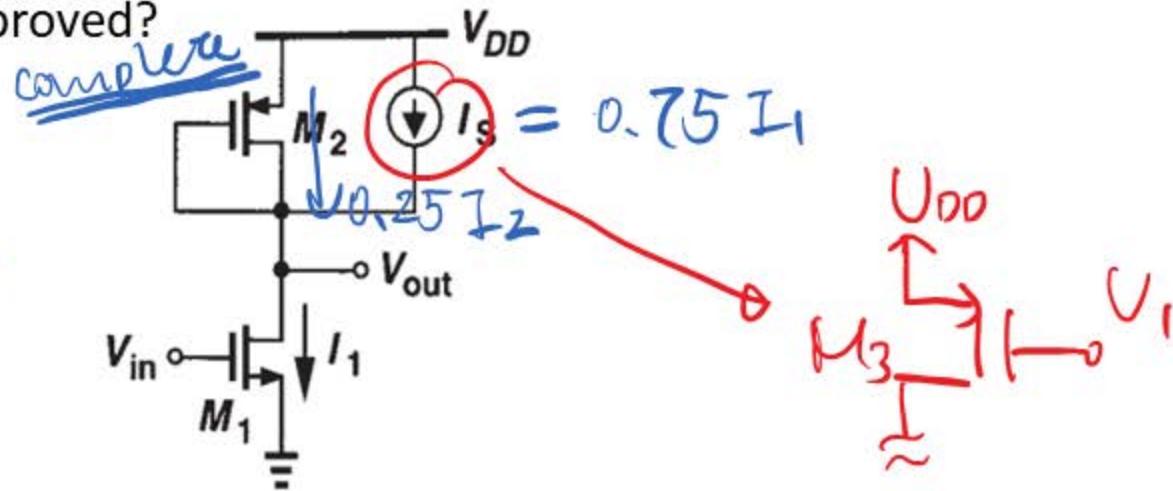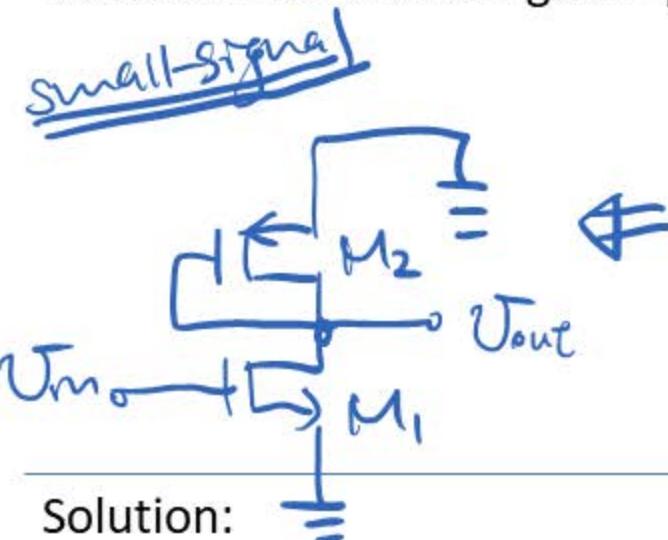Example


M_1 in saturation and $I_S = 0.75 \times I_1$. How do the disadvantages of CS stage with diode-connected load get improved?



Solution:

- Small-signal Analysis ($\lambda = 0$):

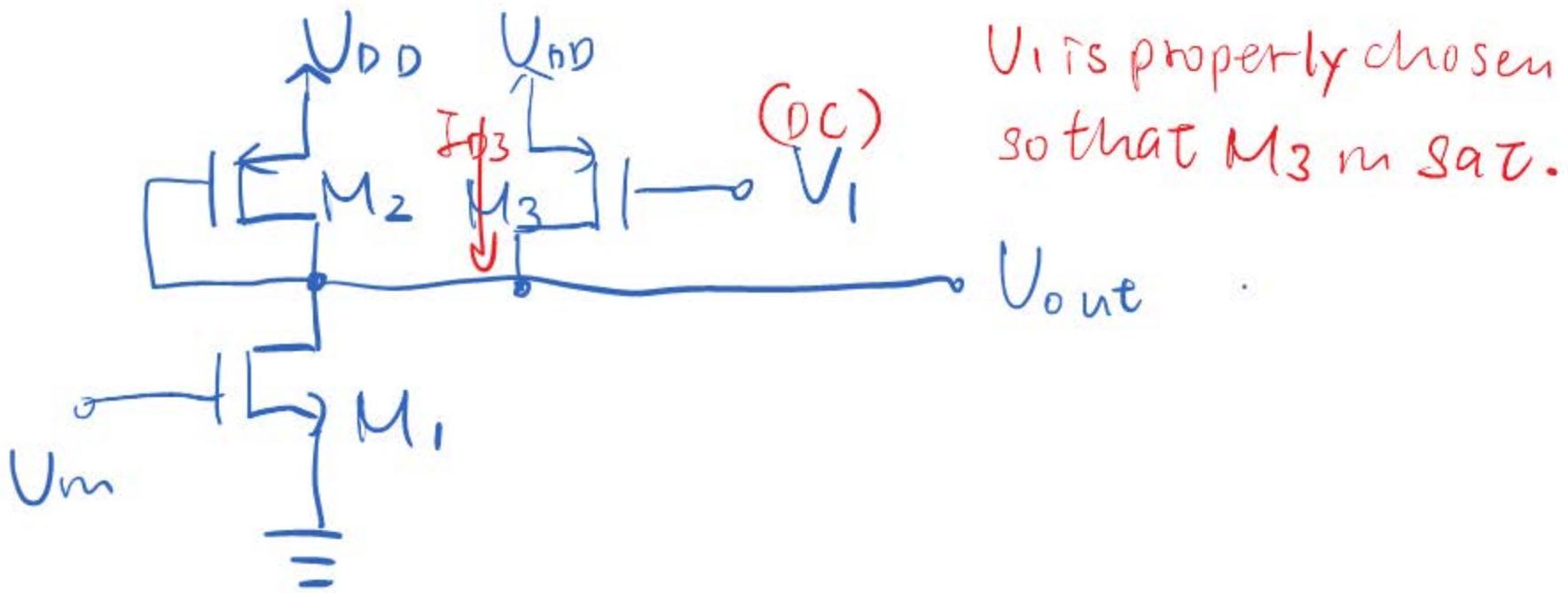
$$A_v = \frac{v_{out}}{v_{in}} = -\frac{gm_1}{gm_2} = -\frac{\sqrt{2\mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}}}{\sqrt{2\mu_p C_{ox} \left(\frac{W}{L}\right)_2 I_{D2}}} = -\frac{\sqrt{4\mu_n \left(\frac{W}{L}\right)_1}}{\sqrt{\mu_p \left(\frac{W}{L}\right)_2}} = -\frac{4(V_{SG2} - V_{TH2})}{(V_{GS1} - V_{TH1})}$$



$$I_{D3} = \frac{1}{2} \mu_p C_{ox} \left(\frac{W}{L_{eff}} \right)_3 (V_{DD} - V_1 - 0.8)^2 [1 + \gamma(V_{DD} - V_{OUT})]$$

if $\gamma = 0, \beta \neq 0$
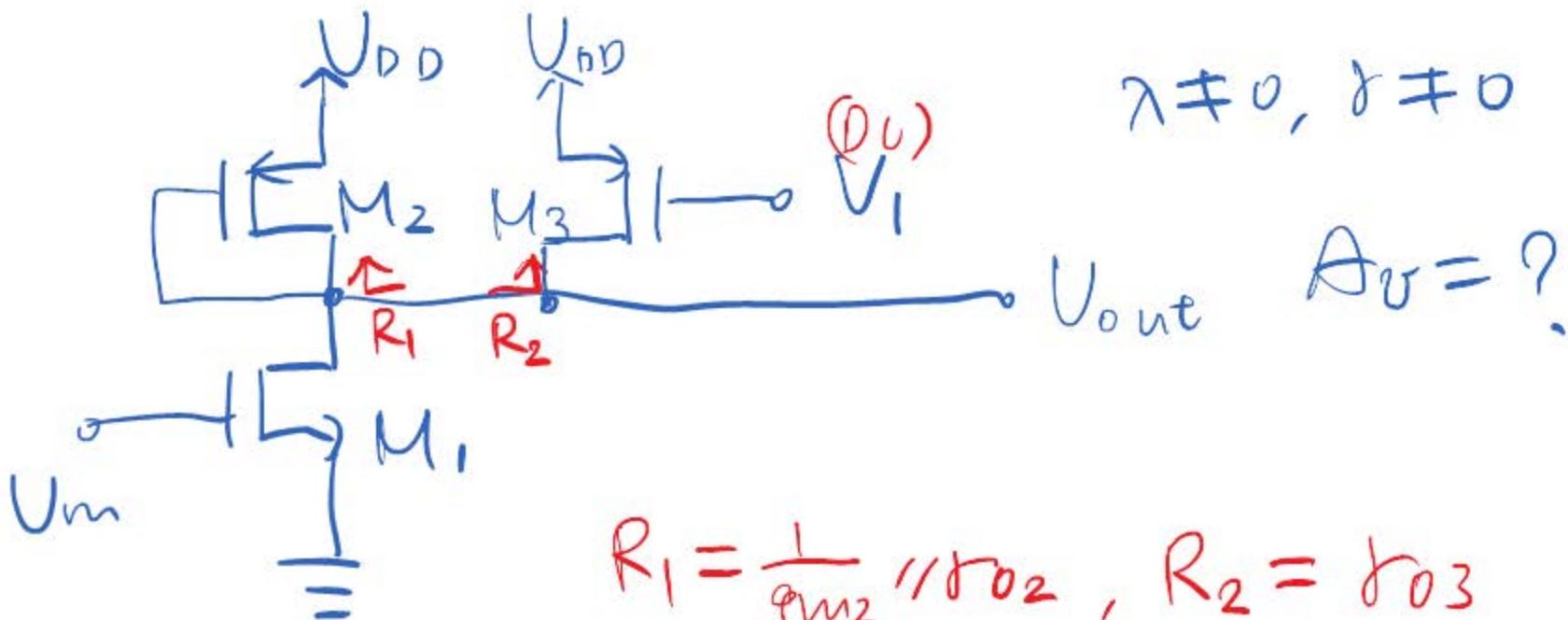
$$I_{D3} = \boxed{\text{constant}} (V_{DD} - 0.8 - V_1)^2 = \boxed{\text{constant}}$$




$$R_1 = \frac{1}{g_{m2}} // r_{o2}, R_2 = r_{o3}$$

$$A_V = -g_{m1} (r_{o1} // R_1 // R_2)$$


$$= -g_{m1} \cdot$$

$$(r_{o1} // \frac{1}{g_{m2}} // r_{o2} // r_{o3})$$

$$R_2 = \frac{r_o}{N_T} = r_{o3}$$

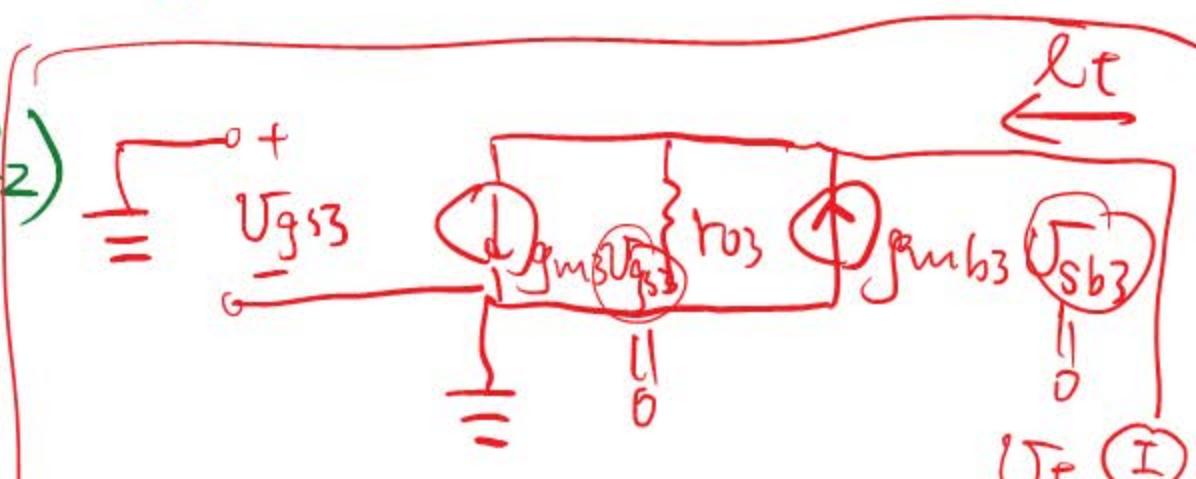

Common-Source with Current-Source Load

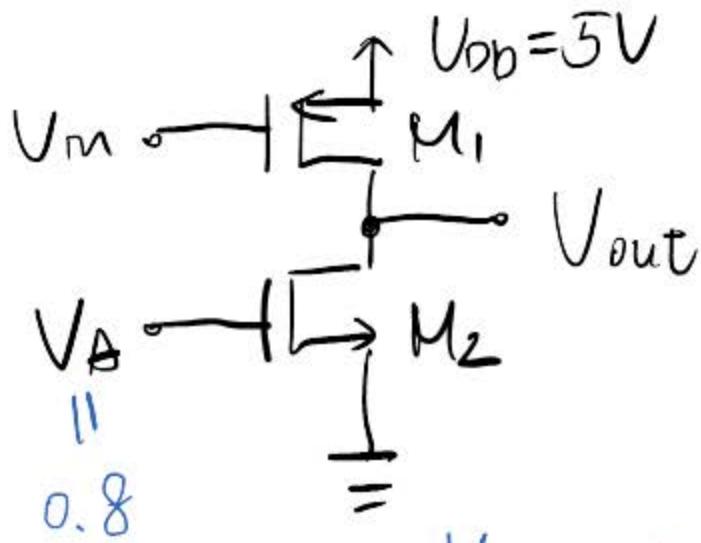

1° Find out $V_{OUT} = ?$
Then we make sure
 M_1 and M_2 in sat.

$$V_{BS1} = 0 \Rightarrow |V_{TH1}| > 0.8$$

$$V_{BS2} = 0 \Rightarrow V_{TH2} = 0.7$$

$$\lambda \neq 0, \gamma \neq 0$$

$$V_m = 4.1 + 0.0018m(2\pi 100t)$$



$$V_{out} = V_{OUT} + V_{out} = ?$$

$$\frac{1}{2} \mu_p C_o x \left(\frac{w}{L}\right)_1 (5 - 4.1 - 0.8)^2$$


$$[+ \gamma (5 - V_{OUT})]$$

$$= \frac{1}{2} \mu_n C_o x \left(\frac{w}{L}\right)_2 (0.8 - 0.7)^2$$


$$[+ \gamma V_{OUT}]$$

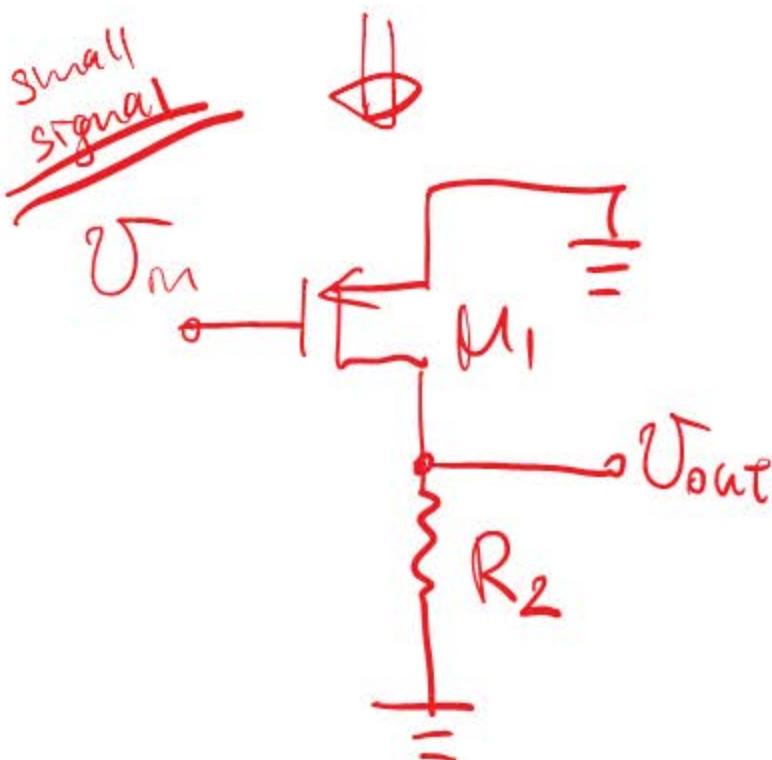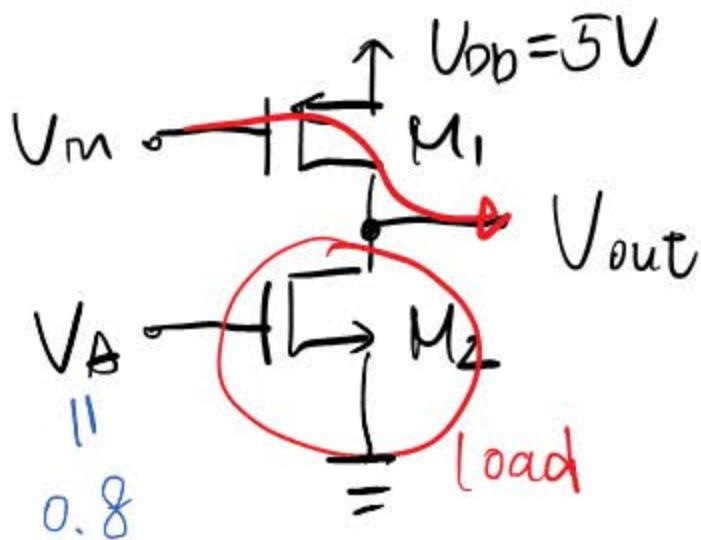

? Find out $V_{out} = ?$

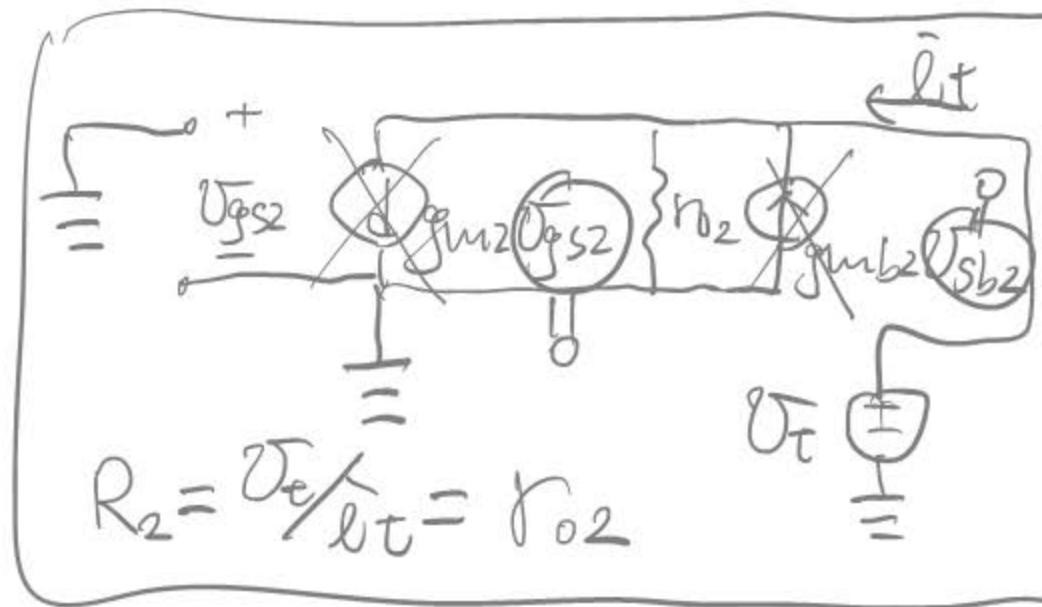
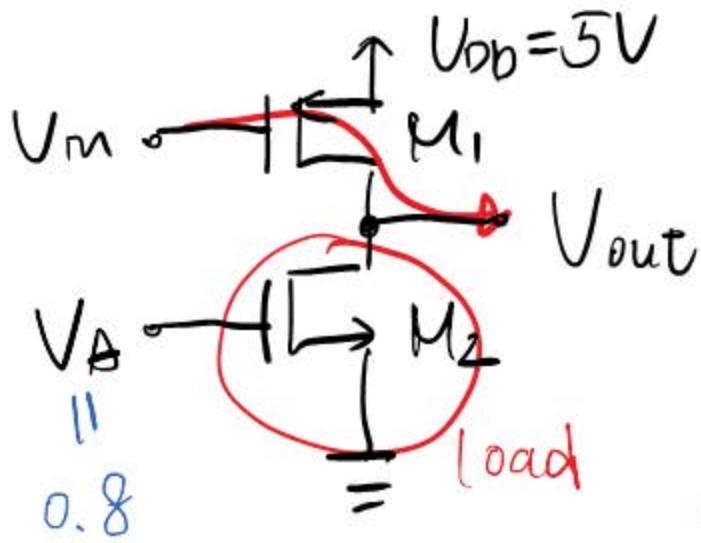
$$\begin{aligned}
 A_V &= \frac{V_{out}}{V_m} = -g_{m1}(r_{o1} \parallel R_2) \\
 &= g_{m1}(r_{o1} \parallel r_{o2})
 \end{aligned}$$





3° Find out $R_m = ?$

$$R_m = \infty$$


4° Find out $R_{out} = ?$

$$R_{out} = b_{D1} // b_{D2}$$

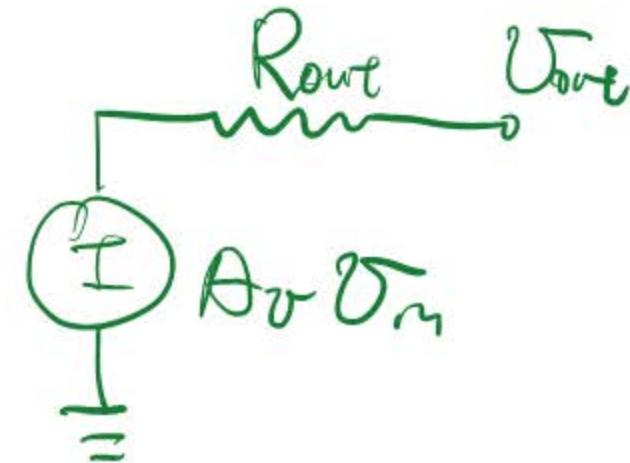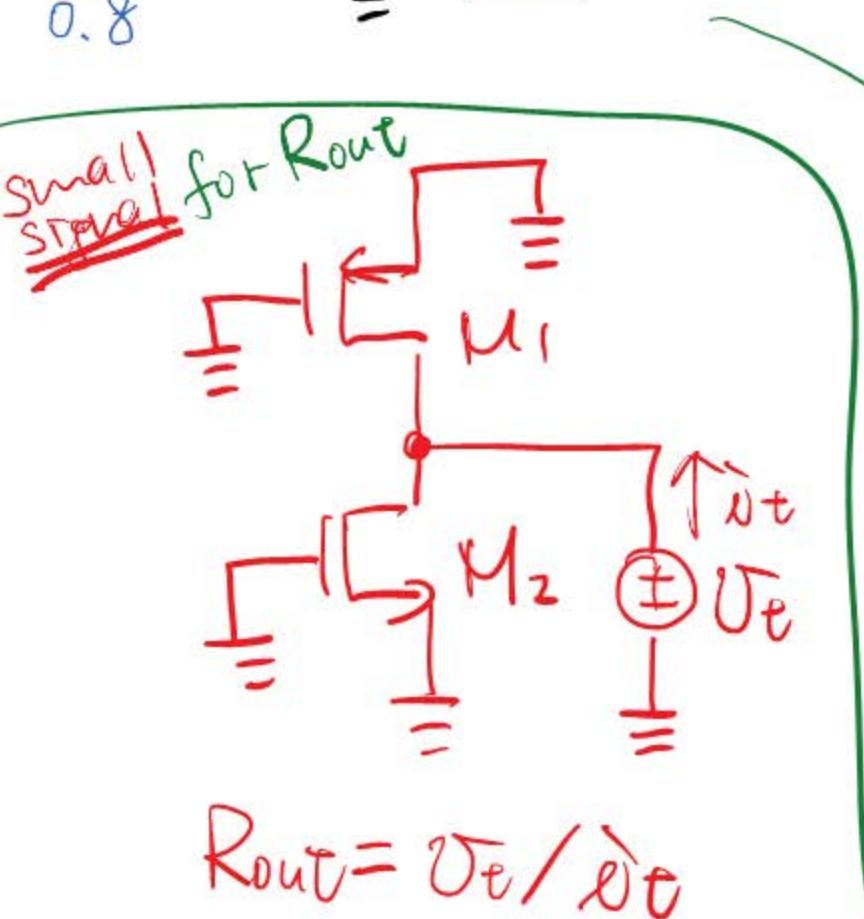

Equivalent Small Signal Circuit

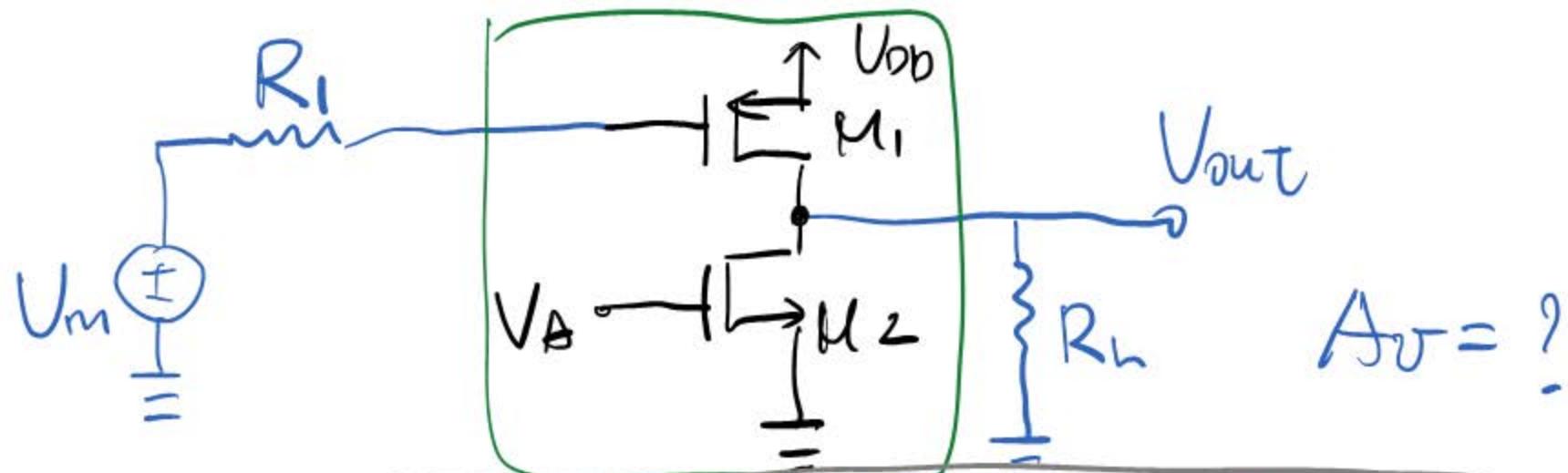
$$R_{out} = \frac{\partial U_e}{\partial I_e}$$




$$A_V = ?$$

Small signal
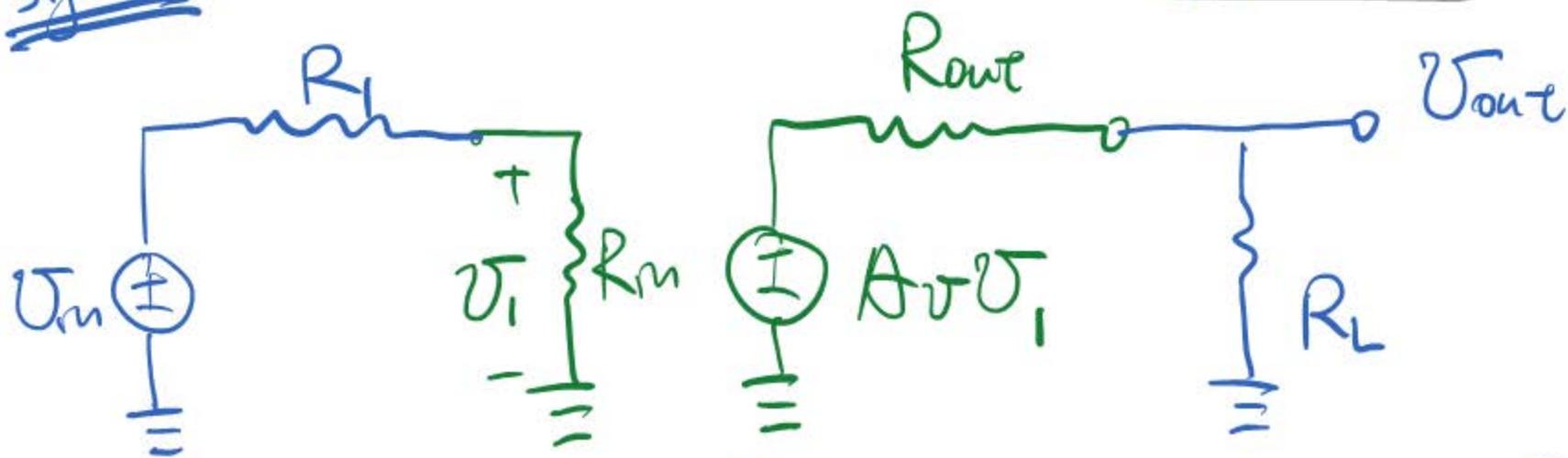
$$A_V = -g_m (r_{o1} \parallel r_{o2}) \frac{R_L}{R_{out} + R_L}$$


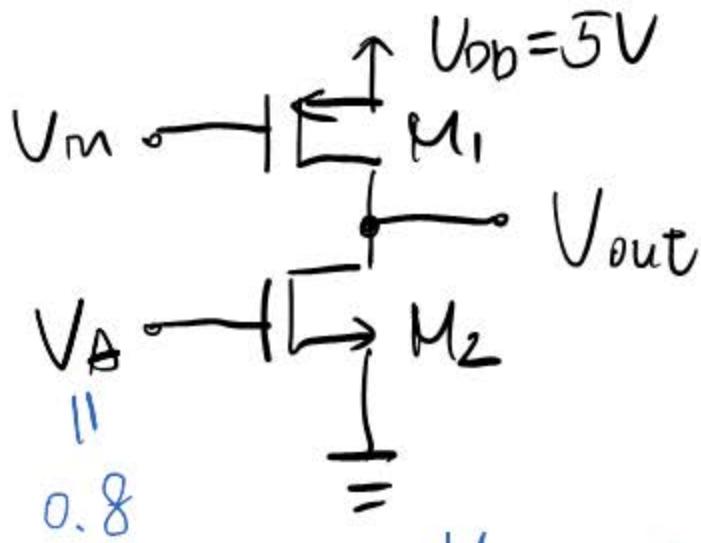
$$R_m = \infty, R_{out} = r_{o1} \parallel r_{o2}, A_V = g_m (r_{o1} \parallel r_{o2})$$



5° Find out available output swing range.
 $0.1 \sim 4.9$

$$V_{out, max} = 5 - (5 - 4.1 - 0.8)$$

$$= 4.9$$

$$= V_{DD} - [V_{GS1} - (V_{TH1})]$$

overdrive
of M₁

$$V_{out, min} = 0.8 - 0.7$$

$$= [V_{GS2} - V_{TH2}]$$

= 0.1 overdrive
of M₂.

$$\gamma \neq 0, \beta \neq 0$$



$$Vm = 4.1 + 0.0018m(2\pi 100t)$$

$$V_{out} = V_{outT} + V_{outC} = ?$$

Common-Source with Current-Source Load


Small-signal Analysis

$$\lambda \neq 0 \quad \gamma \neq 0$$

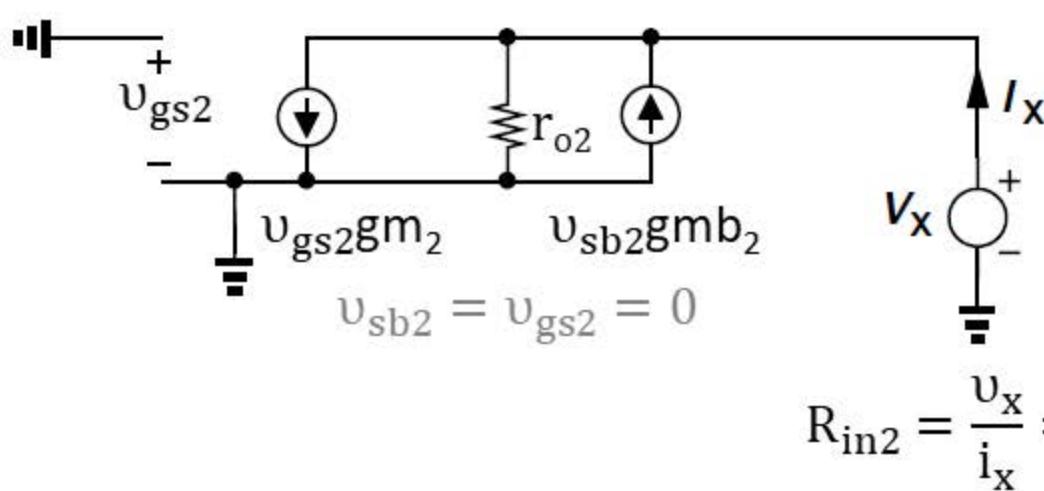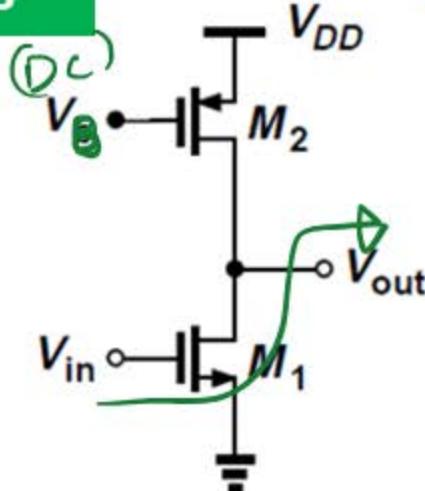

$$v_{sb2} = v_{gs2} = 0$$



$$R_{in2} = \frac{v_x}{i_x} = r_{o2}$$

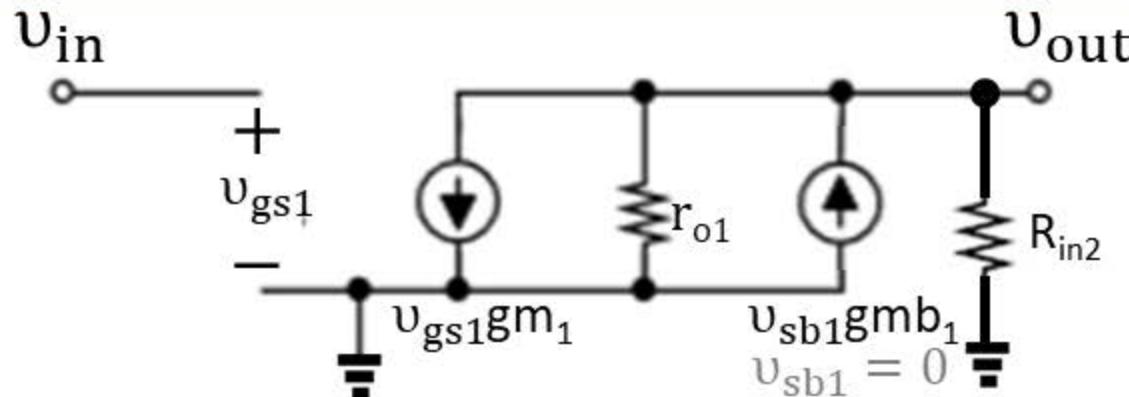

$$A_v = \frac{v_{out}}{v_{in}}$$

$$= -gm_1(r_{o2} \parallel r_{o1})$$

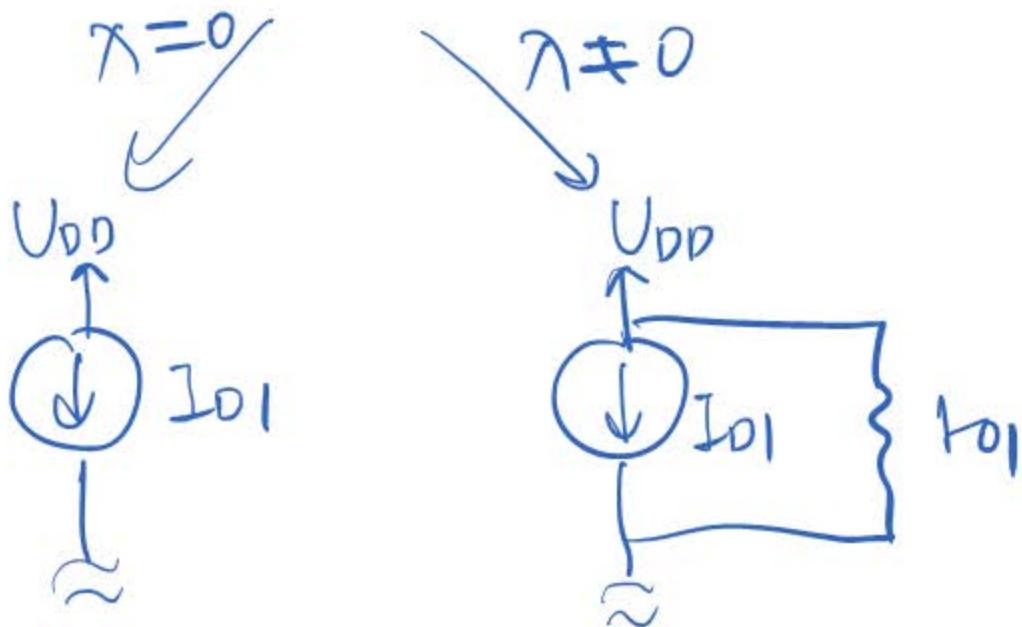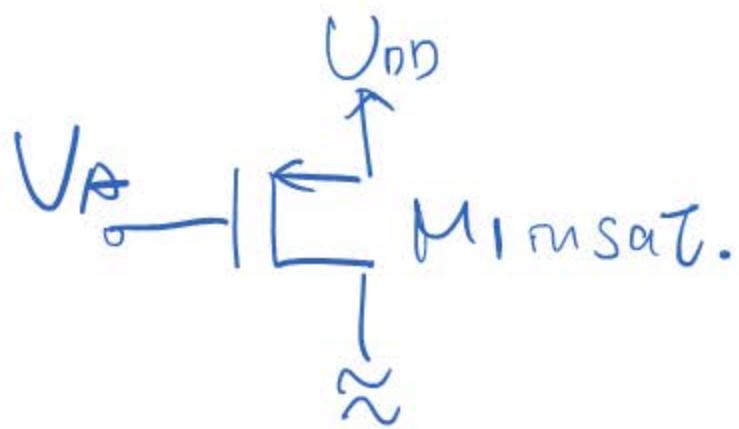- To achieve high A_v , the output swing is severely limited in the CS stages with resistive load and diode-connected load.
- Here $V_{out, max} = V_{DD} - (V_{SG2} - V_{TH2})$, which can be quite close to V_{DD} .




Common-Source with Current-Source Load

57

Small-signal Analysis

$$\lambda \neq 0 \quad \gamma \neq 0$$

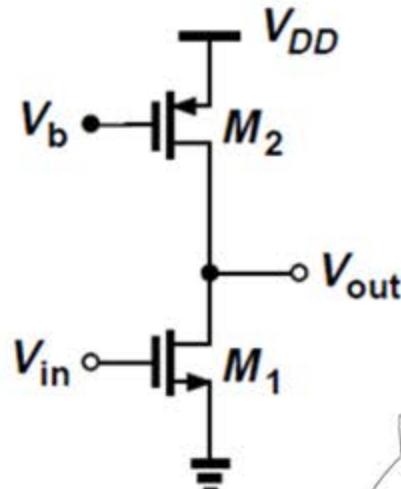

$$A_v = \frac{V_{\text{out}}}{V_{\text{in}}} = -gm_1(r_{o2} \parallel r_{o1})$$

$$r_o \approx \frac{1}{\lambda I_D} \quad \lambda \propto \frac{1}{L}$$

$$gm_1 = \mu n C_{\text{ox}} \left(\frac{W}{L_{\text{eff}}} \right) \left(V_{\text{GS1}} - V_{\text{TH1}} \right)$$


large (H \uparrow V_{DS})

- $V_{\text{out, max}} = V_{DD} - (V_{SG2} - V_{TH2})$
- $V_{\text{out, min}} = (V_{GS1} - V_{TH1})$
- For high gm_1 and small $(V_{GS1} - V_{TH1})$, W of M_1 needs to be large.
- For high r_{o1} and r_{o2} , L of M_1 and M_2 need to be large and L of M_1 and M_2 needs to be increased proportionally. The cost is the **large parasitic drain junction capacitance** at the output.


Degeneration

Common-Source with Source Degradation

Amplifier Equivalent Circuit

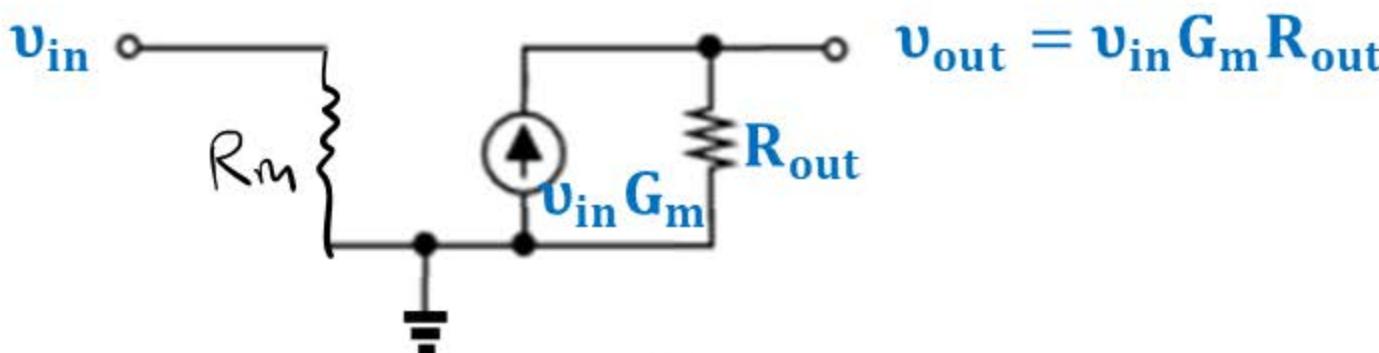


$$v_{out} = v_{in} G_m R_{out}$$

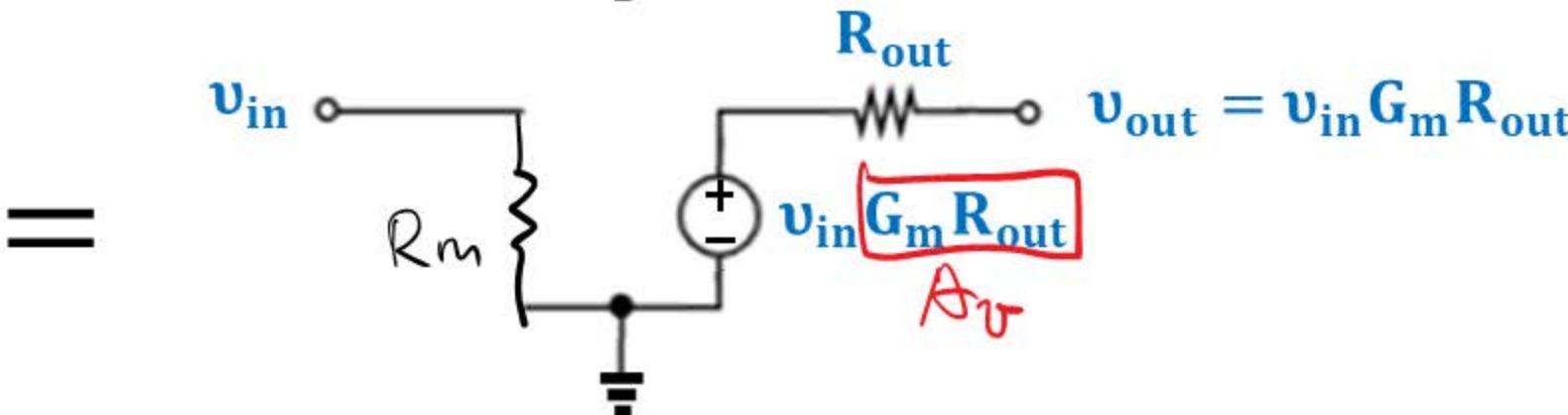


$$v_{out} = v_{in} G_m R_{out}$$

- How to calculate G_m ? v_{out} shorted to ground. $G_m = i_{out}/v_{in}$
- How to calculate R_{out} ? v_{in} shorted to ground and v_{out} connected to v_{test} .
 $R_{out} = v_{test}/i_{test}$

Amplifier Equivalent Circuit


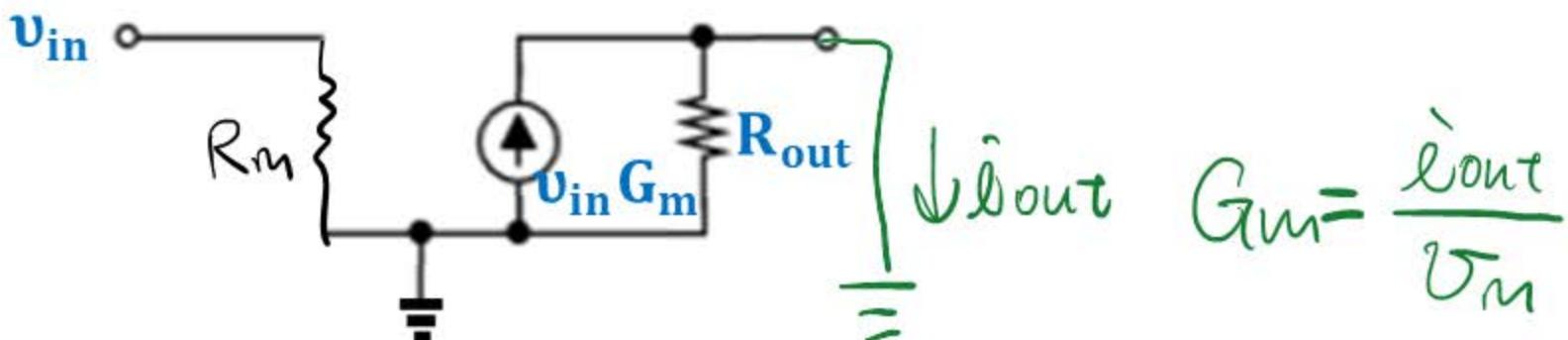


$$G_m = \frac{i_{out}}{v_{in}}$$

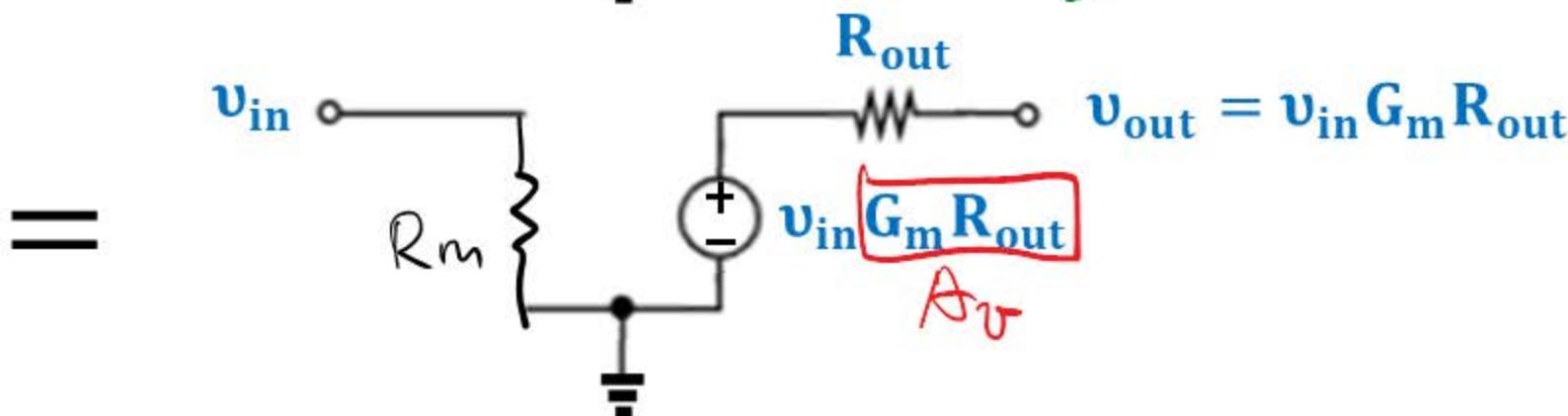


$$v_{out} = v_{in} G_m R_{out}$$

Amplifier Equivalent Circuit

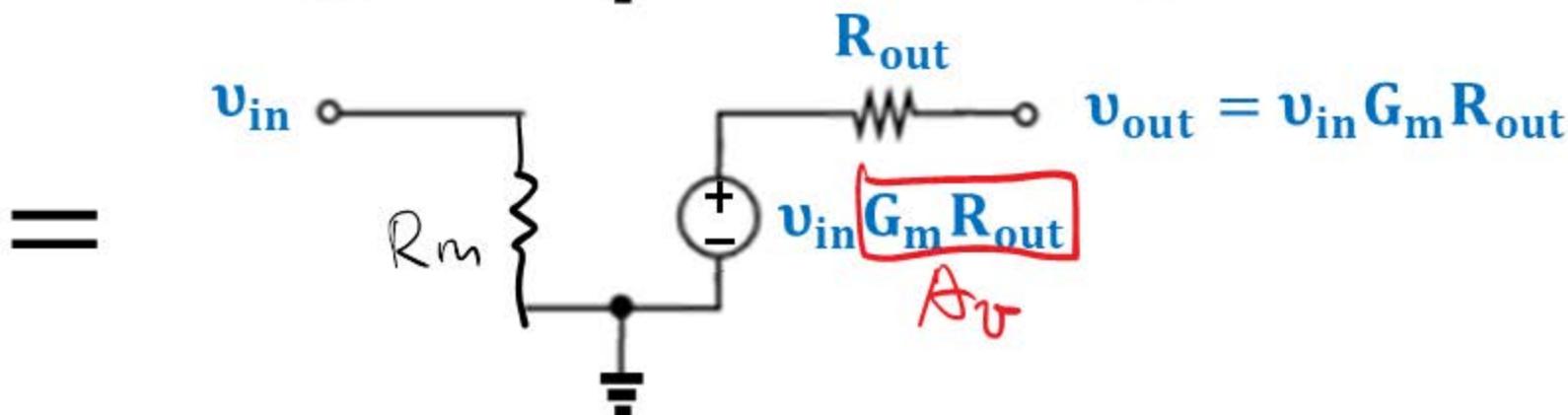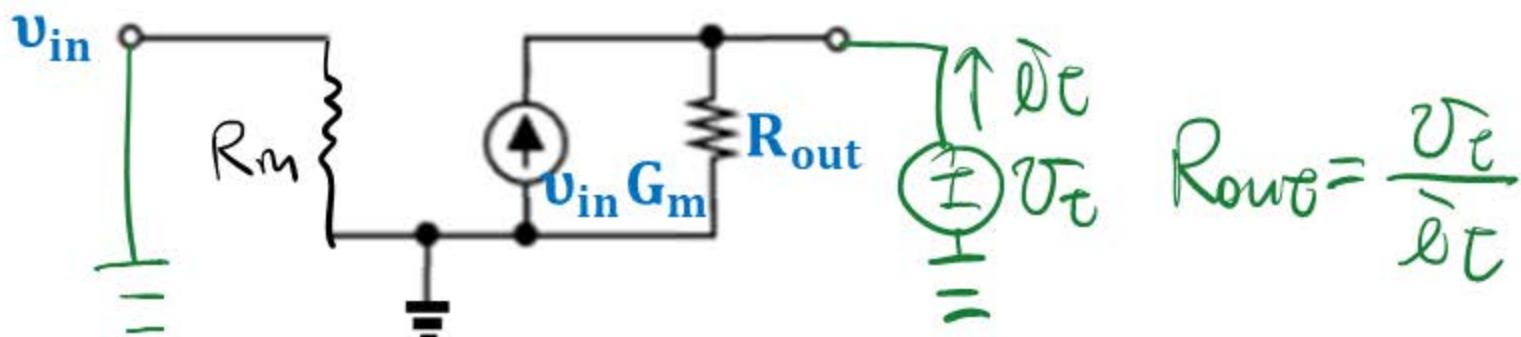

complete

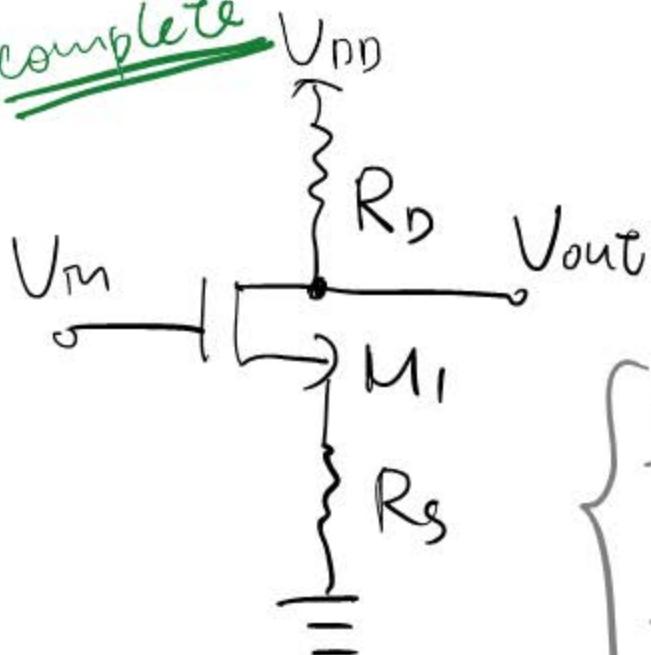


$$\eta \neq 0, \gamma \neq 0 \\ A_{\text{v}} = ?$$

$$G_m = \frac{\bar{I}_{\text{out}}}{V_m}$$

$$\left\{ \begin{array}{l} \frac{U_a}{R_s} + (U_a - U_m) g_m + \frac{U_a}{r_{b1}} + g_{mb1} U_a = 0 \\ -\frac{U_a}{R_s} = \bar{I}_{\text{out}} \end{array} \right.$$

Equivalent small signal



Small signal

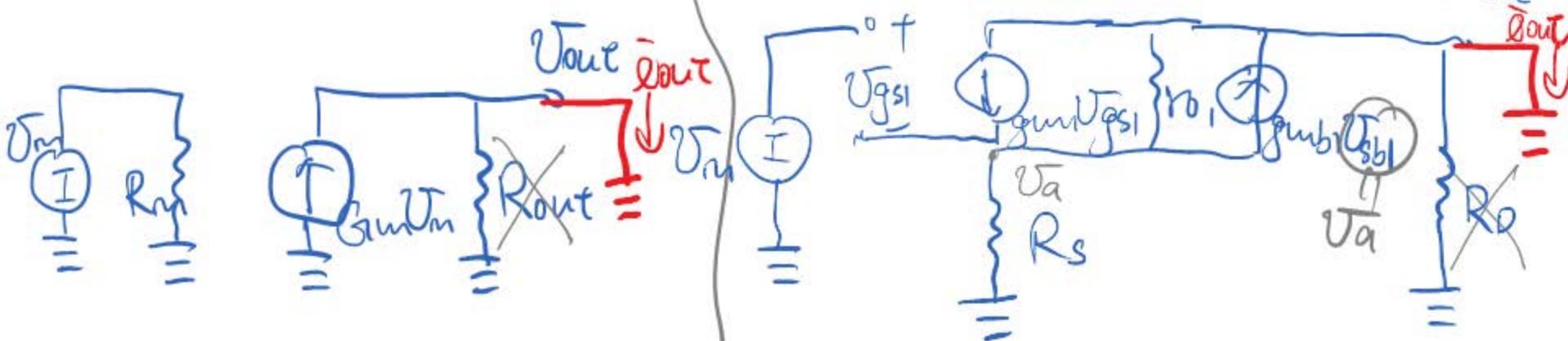

Common-Source with Source Degradation

Small-signal
Analysis

$$\lambda \neq 0 \quad \gamma \neq 0$$

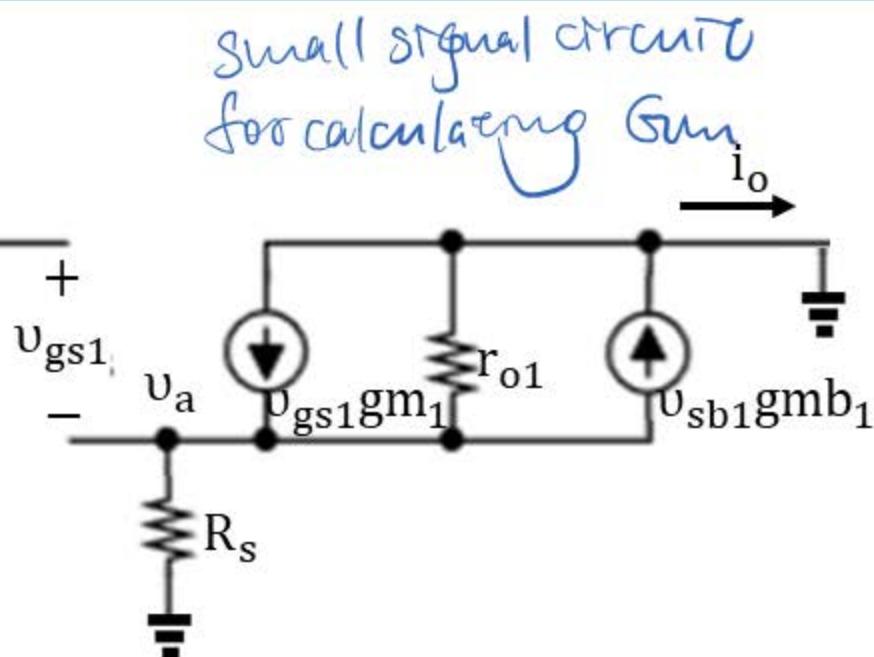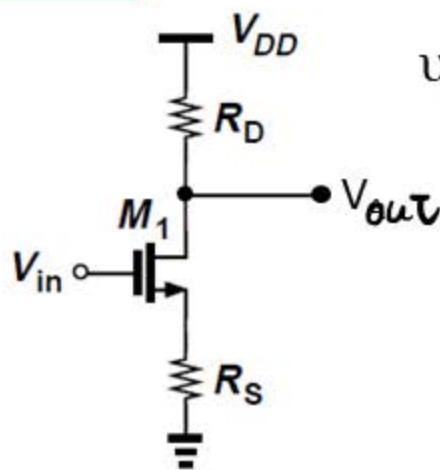

$$\left\{ \begin{array}{l} i_o = \frac{-v_a}{R_s} \\ (v_{in} - v_a)gm_1 + i_o = \frac{v_a}{r_{o1}} + v_a gmb_1 \end{array} \right.$$

$$G_m = \frac{i_o}{v_{in}} = \frac{-gm_1 r_{o1}}{R_s + r_{o1} + (gm_1 + gmb_1)r_{o1}R_s} \approx -\frac{1}{R_s}$$


Intrinsic gain of M_1

If $gmb_1 \ll gm_1$
If $(gm_1 + gmb_1)r_{o1}R_s \gg r_{o1}$ and R_s


Common-Source with Source Degradation

DC Analysis

$$\alpha(U_m - U_{TH})^2 \quad R_s = 0$$

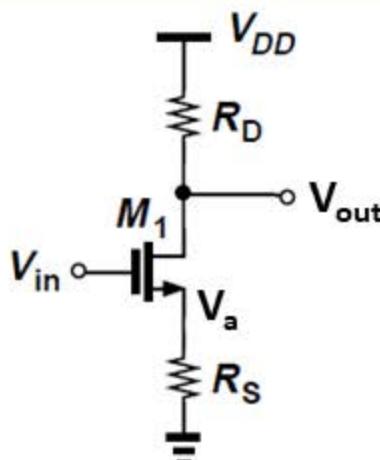


$$R_s \neq 0$$

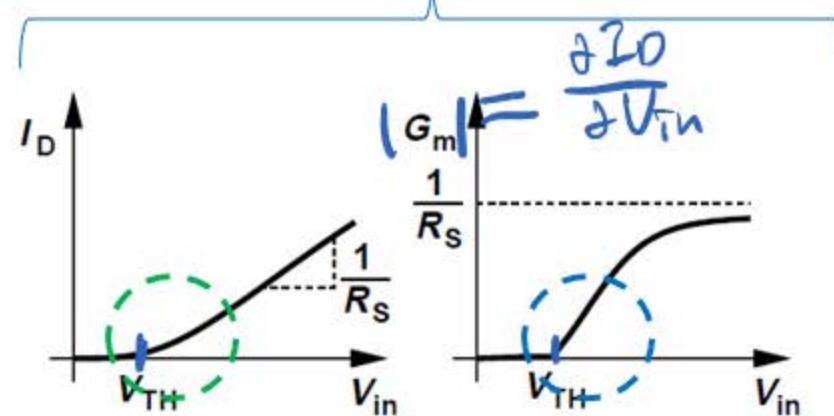

- At low V_{in} (gm small), turn-on behavior of $R_s \neq 0$ is similar to that of $R_s = 0$.
- At large V_{in} (gm large), the effect of R_s , i.e. degradation, becomes more significant.
- $V_{in} = 0 \text{ V} \rightarrow M_1 \text{ off, no current flowing} \rightarrow V_a = 0 \text{ V and } V_{out} = V_{DD}$

complete

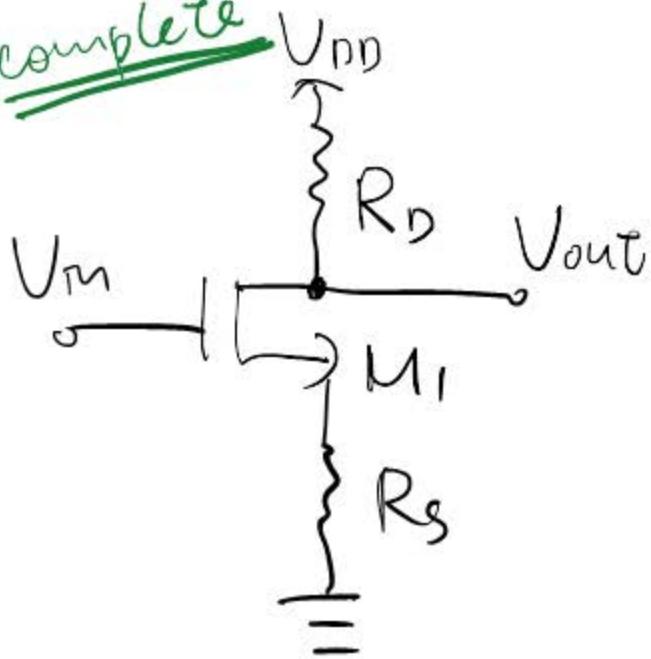


$\eta \neq 0, \beta \neq 0$


$$A_v = ?$$

$$R_{out} = \frac{V_e}{I_e}$$

Equivalent small signal

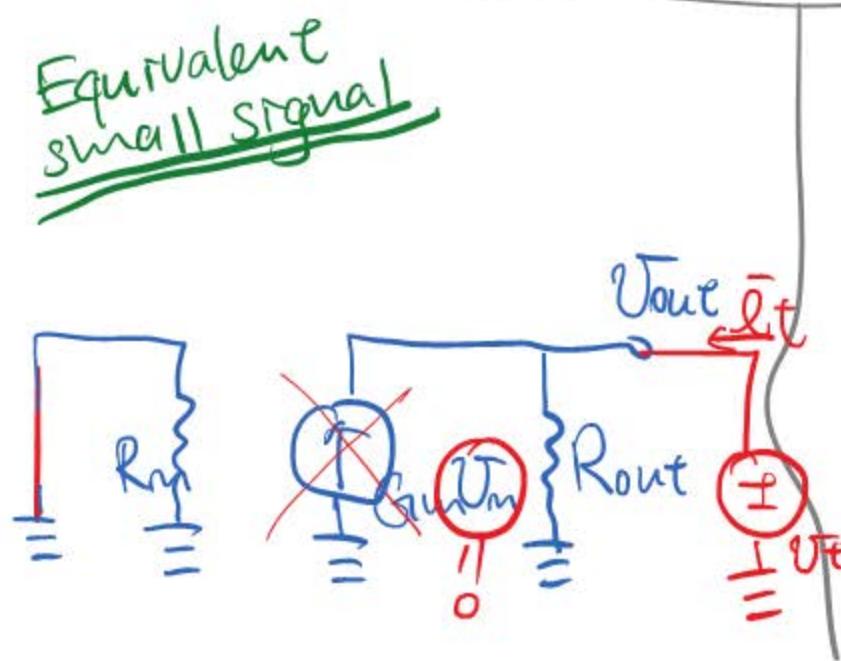


Small signal

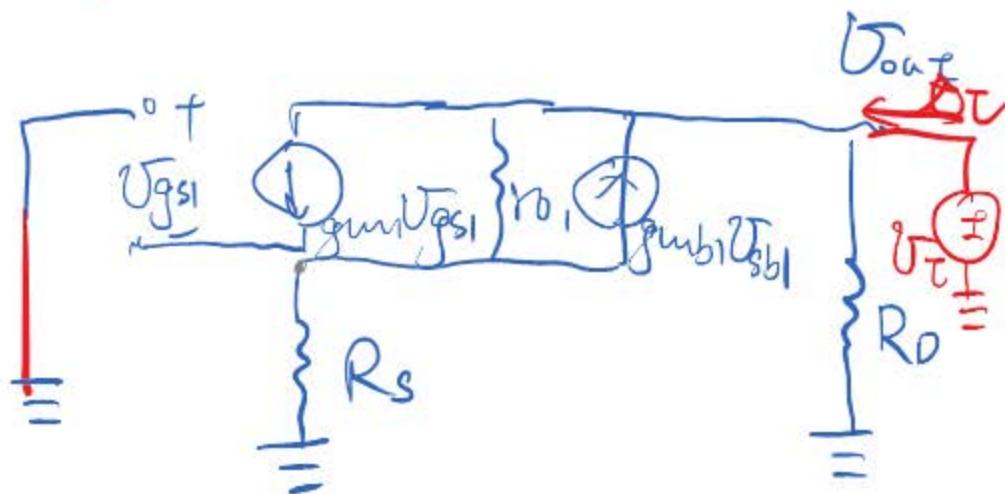

Common-Source with Source Degradation

Small-signal
Analysis

$$\lambda \neq 0 \quad \gamma \neq 0$$

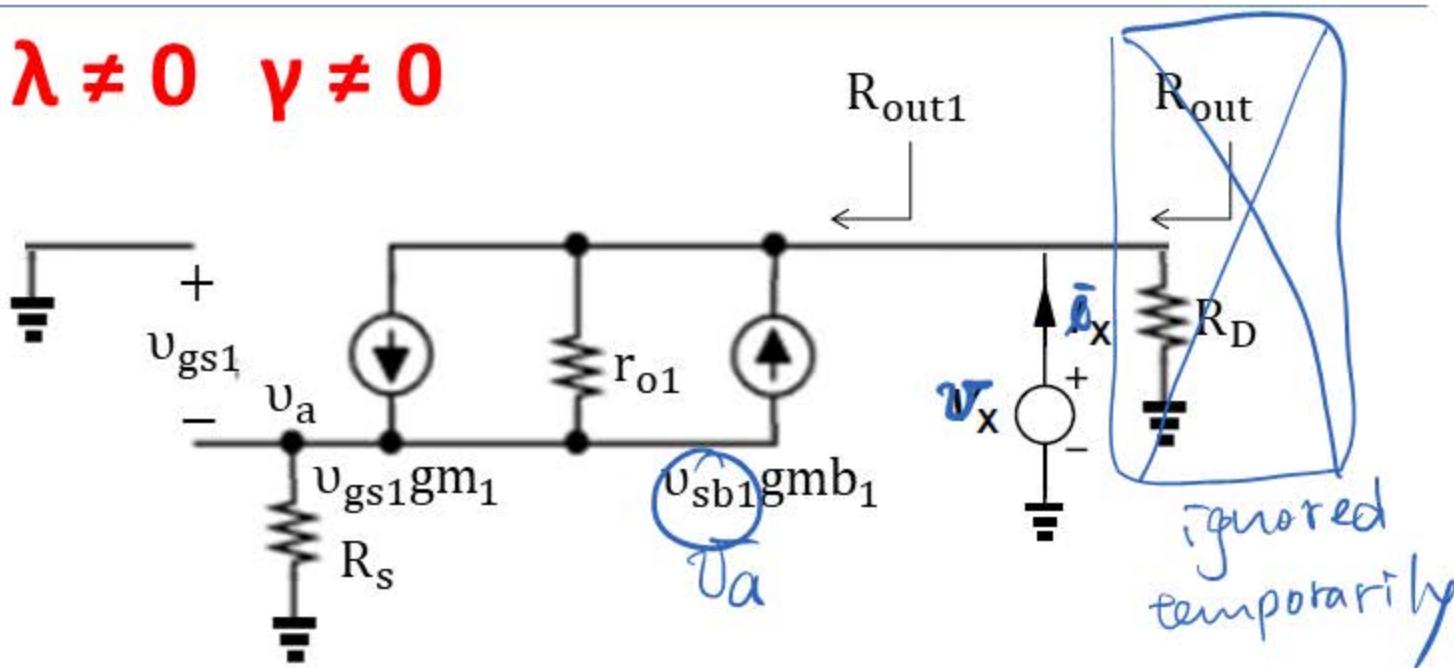

$$\begin{cases} i_x = \frac{v_a}{R_s} \\ v_a g m_1 + v_a g m b_1 + \frac{v_a - v_x}{r_o} + i_x = 0 \end{cases}$$


$$R_{out} = R_{out1} \parallel R_D = [R_s + r_{o1} + (g m_1 + g m b_1) r_{o1} R_s] \parallel R_D \approx R_D$$

$$\frac{v_x}{i_x} = R_{out} \quad \text{if } (g m_1 + g m b_1) r_{o1} R_s \gg R_D$$

Common-Source with Source Degradation

Small-signal
Analysis

$$\lambda \neq 0 \quad \gamma \neq 0$$

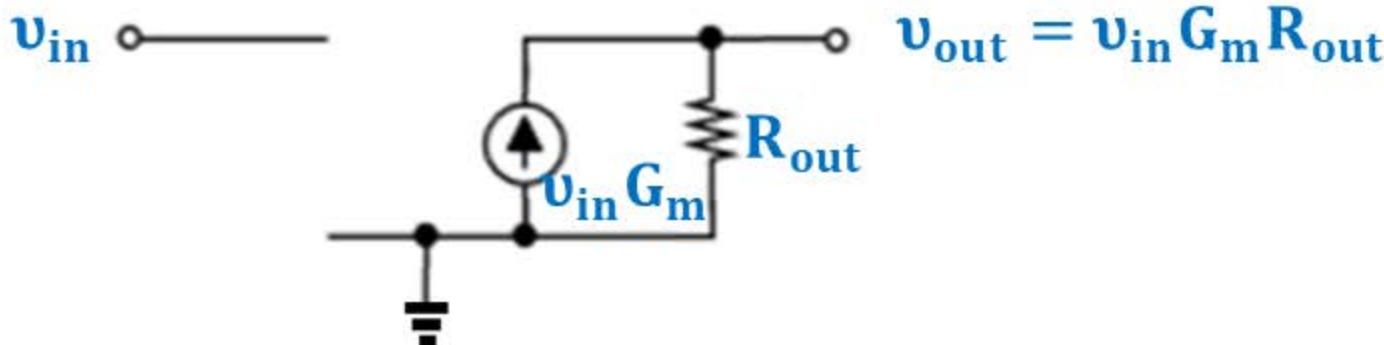

$$A_v = \frac{v_{out}}{v_{in}} = G_m R_{out}$$



$$= \frac{-g_{m1}r_{o1}}{(R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S)} \cdot \frac{(R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S)R_D}{[R_S + r_{o1} + (g_{m1} + g_{mb1})r_{o1}R_S] + R_D}$$

$$\approx -\frac{R_D}{R_S} \quad \text{If } (g_{m1} + g_{mb1})r_{o1}, \text{ the intrinsic gain, is large.}$$

$f_{gm_{mb}} \ll f_{gm}$

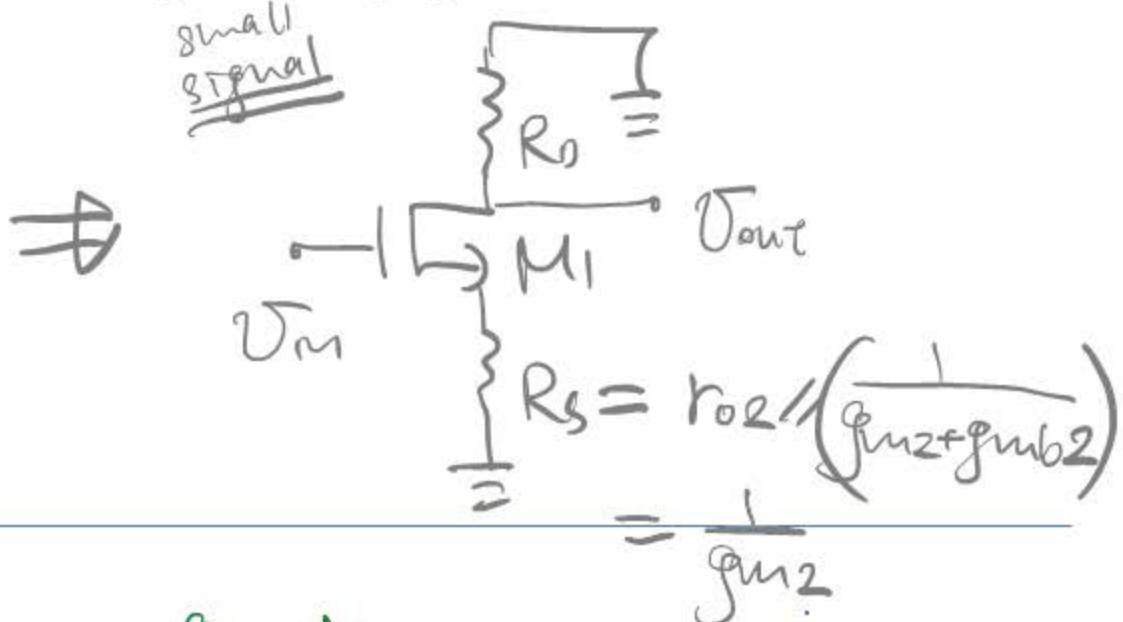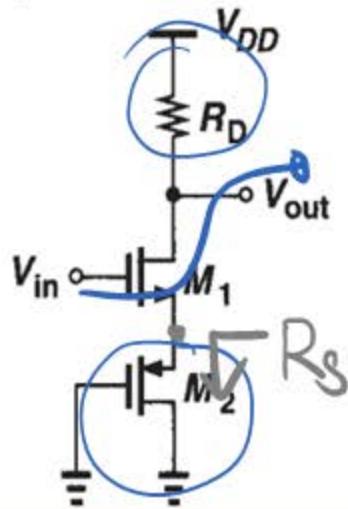Example

Assuming $\lambda = \gamma = 0$, calculate the small signal voltage gain of the circuit below.




Solution:

$$G_m = -\frac{1}{\frac{1}{gm_1} + \frac{1}{gm_2}} = \frac{-gm_1 \delta \omega_1}{R_s + \delta \omega_1 + (gm_1 + gm_{b1}) \delta \omega_1 R_s}$$

$$R_{out} = R_D$$

$$A_v = G_m R_{out}$$
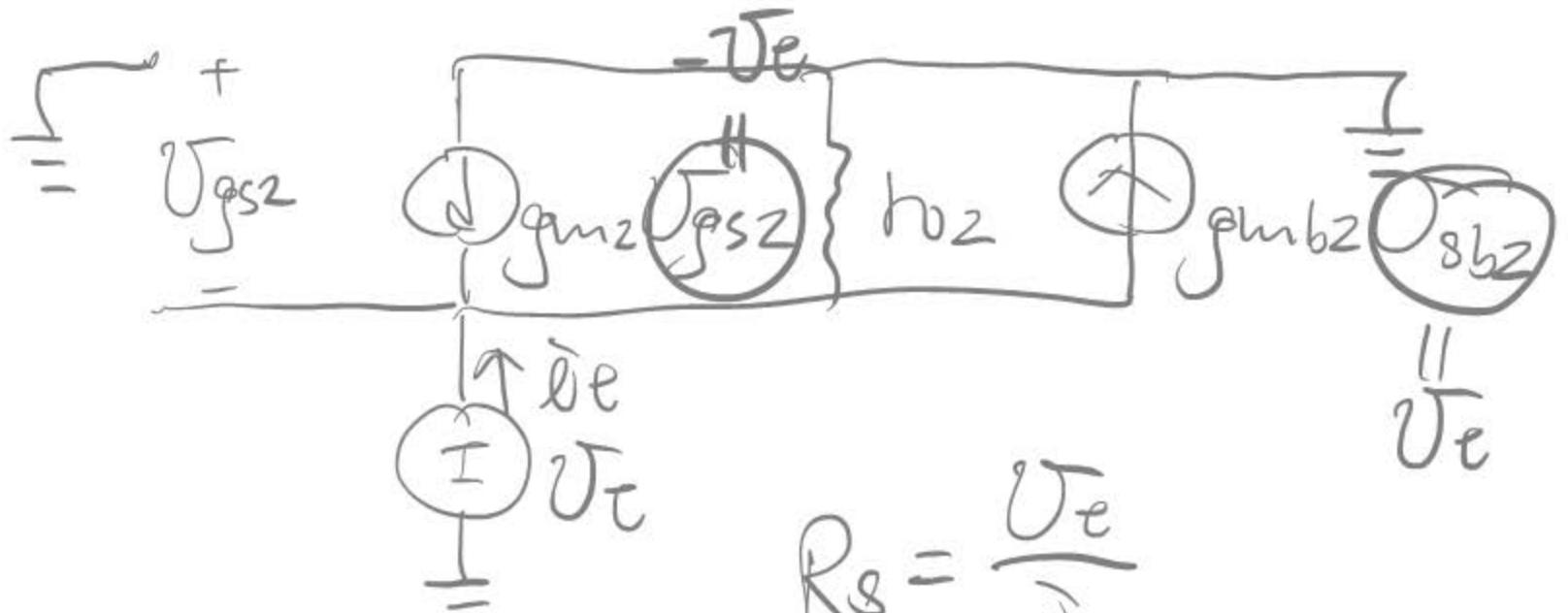
$$= \frac{-gm_1 \delta \omega_1}{\delta \omega_1 + gm_1 \delta \omega_1 R_s}$$




$$R_S = \frac{U_e}{\hat{U}_e}$$

$$= r_{o2} / \left(\frac{1}{g_{m2} + g_{mb2}} \right)$$

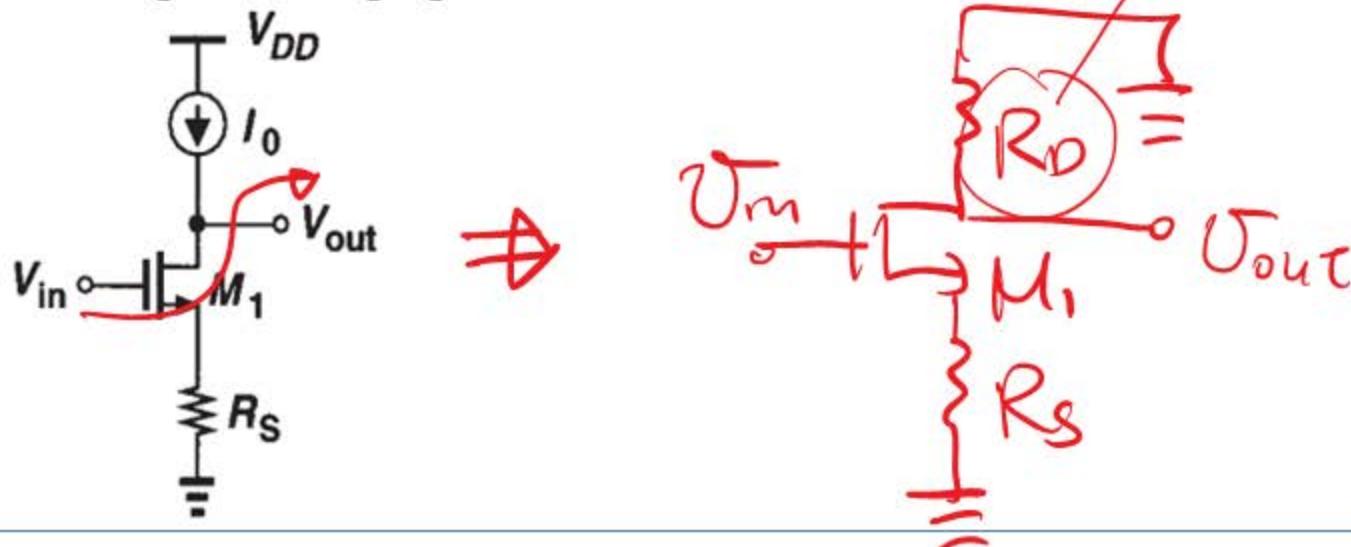Example

Calculate the small signal voltage gain of the circuit below.




Solution:

$$G_m = \frac{-gm_1 r_{o1}}{r_{o1} + R_S + (gm_1 + gmb_1)r_{o1}R_S}$$

$$R_{out} = r_{o1} + R_S + (gm_1 + gmb_1)r_{o1}R_S$$

$$A_v = G_m R_{out} = -gm_1 r_{o1}$$

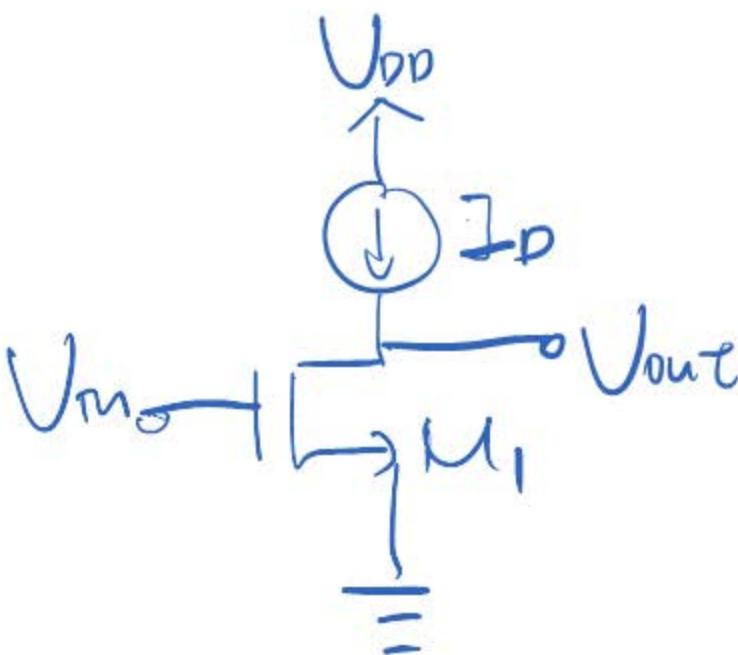
- I_o is ideal current source \rightarrow Voltage across R_s is constant
 \rightarrow M_1 source shorted to ground
- R_D replaced by current source \rightarrow Nonlinearity issue arises again




$$U_{SB1} = 0$$

$$U_{SBI} = 0$$

$$A_V = -g_{m1} h_{o1}$$

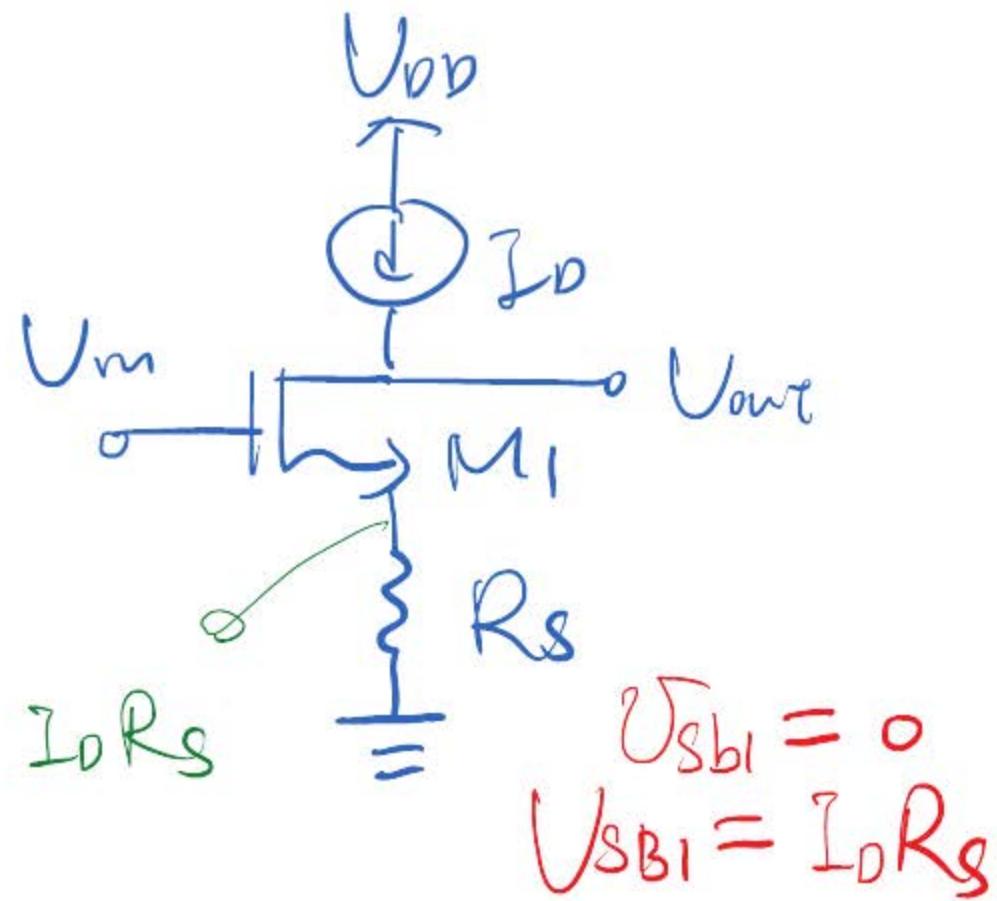


$$A_V = -g_{m1} h_{o1}$$

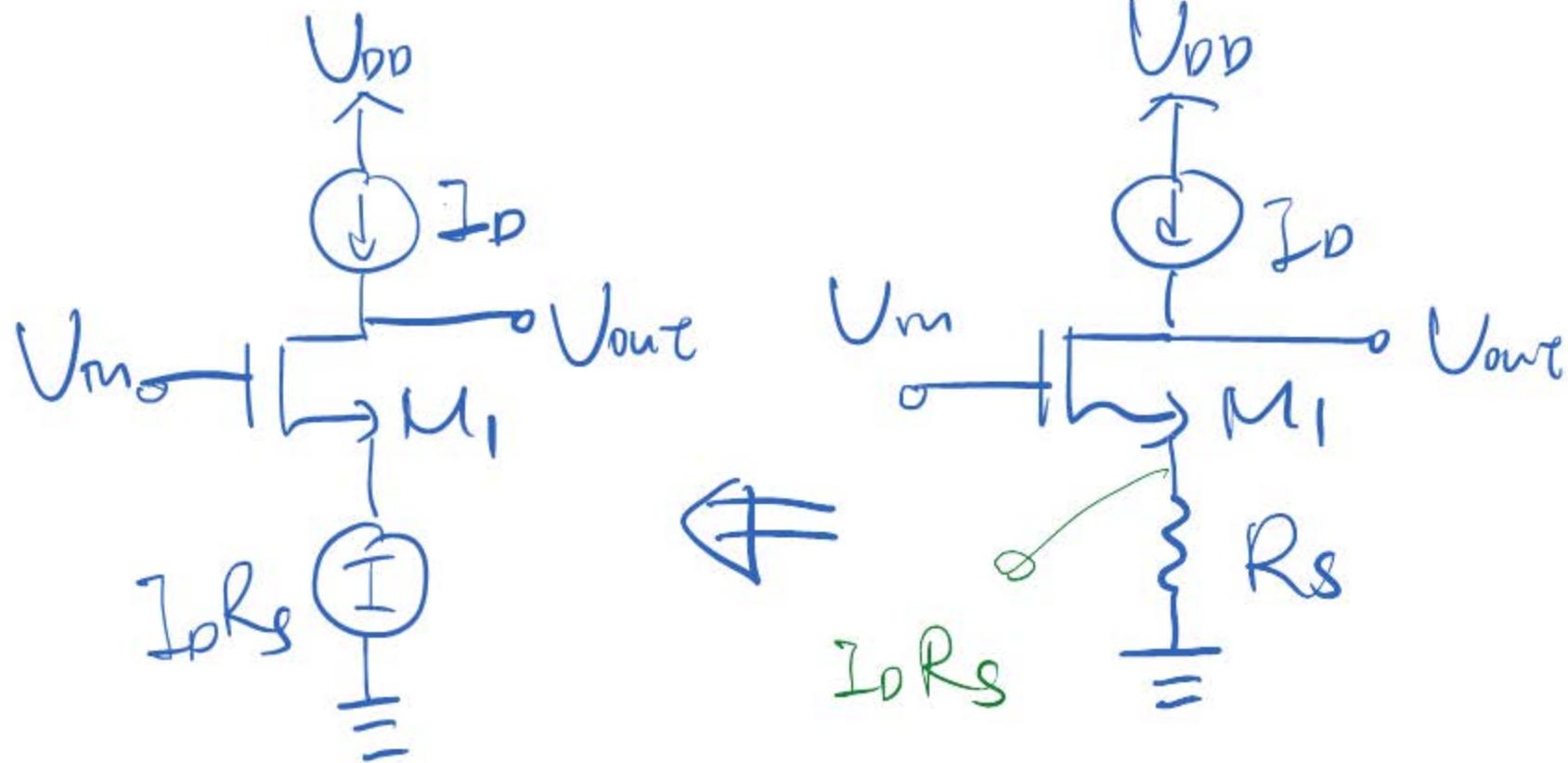

$$\Delta v = -g_{m1} \Delta I_D$$

Example

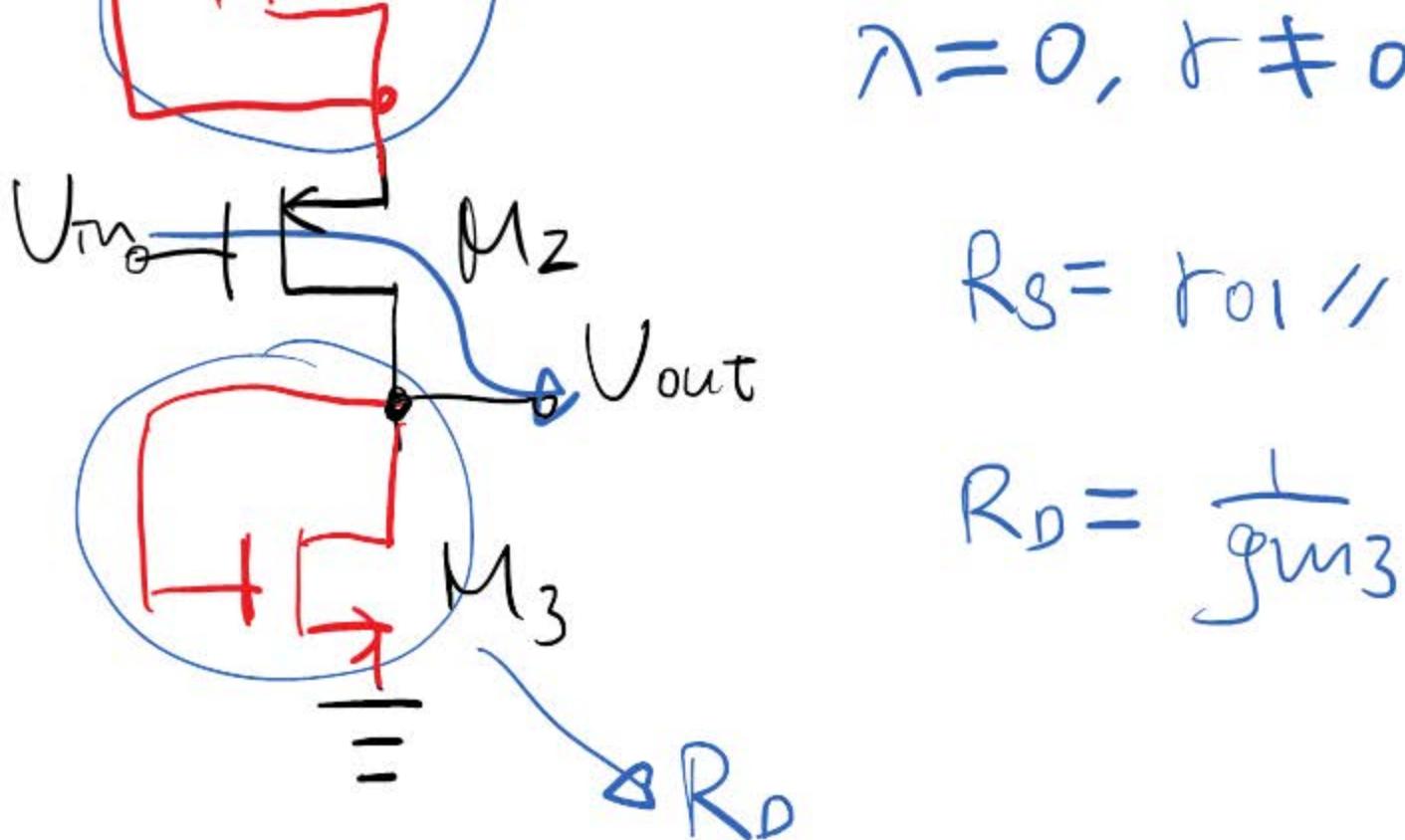


$$G_m = ? \quad R_{out} = ?$$

$$\lambda = 0, \tau \neq 0$$

$$R_S = r_{01} \parallel \frac{1}{g_{m1}} = \frac{1}{g_{m1}}$$

$$R_D = \frac{1}{g_{m3}}$$
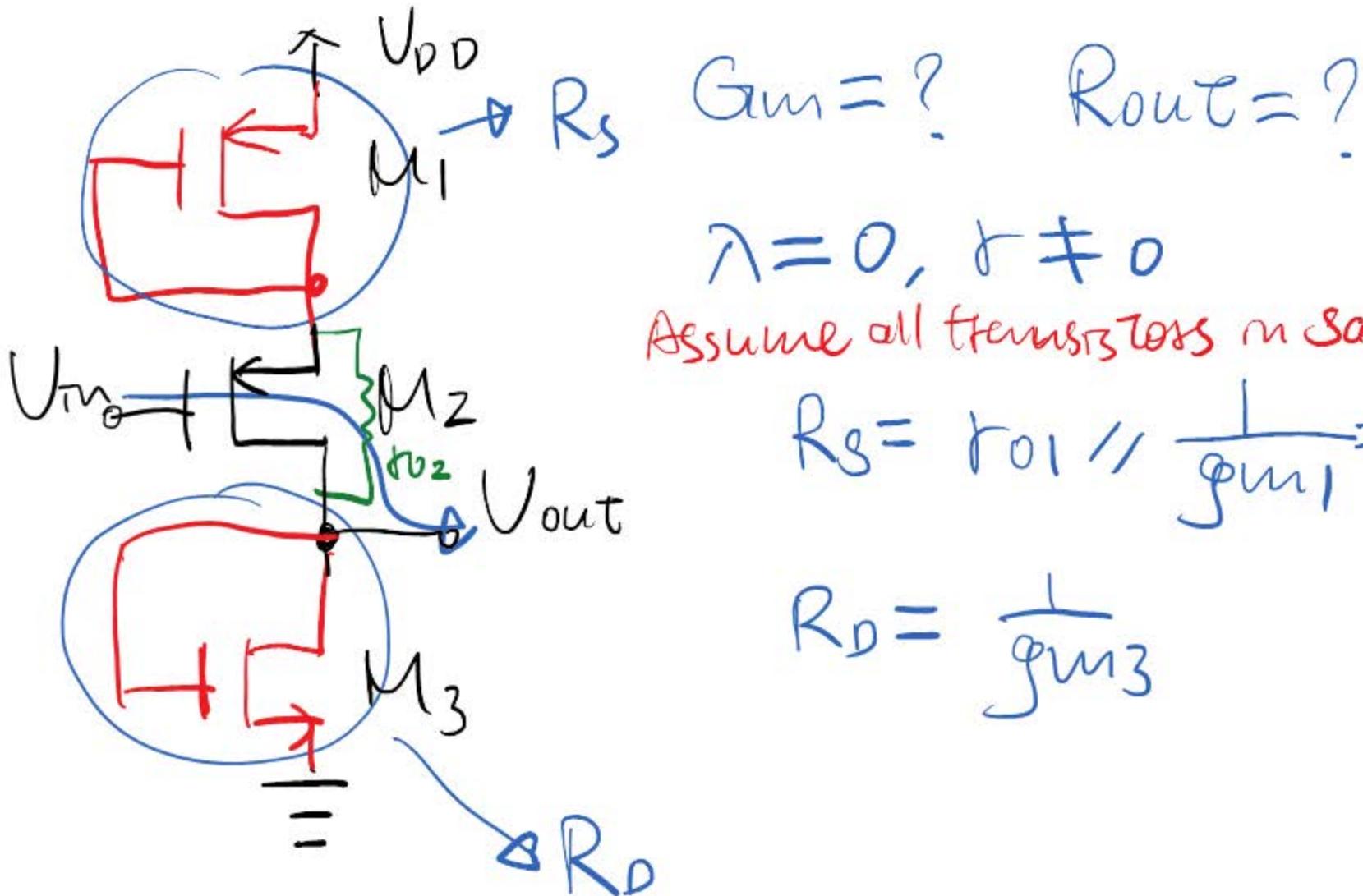
$$G_m = \frac{-g_{m2}r_{02}}{r_{02} + R_S + (g_{m2} + g_{mb2})r_{02}R_S} = \frac{-g_{m2}}{1 + (g_{m2} + g_{mb2})R_S}$$





$$\begin{aligned}
 R_{out} &= R_D \parallel \left(r_{o2} + R_S + \boxed{(g_{m2} + g_{mb2}) r_{o2} R_S} \right) = \frac{1}{g_{m3}}
 \end{aligned}$$

~~miseric gnm of M2~~

Common - Dtarh


Source Follower (Buffer)

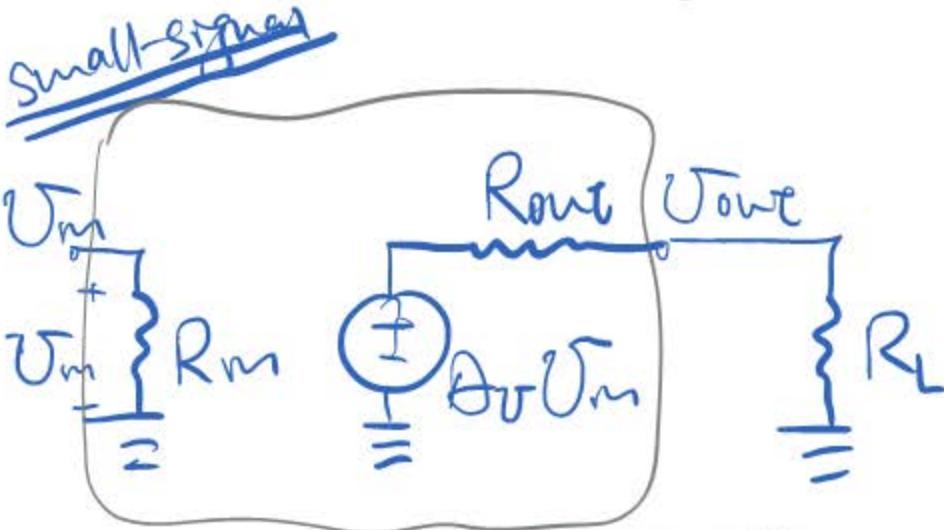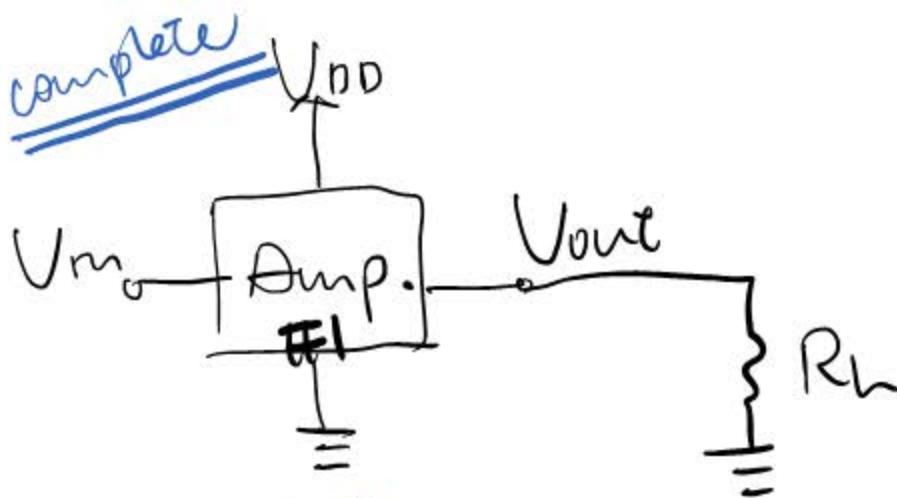

$$\frac{V_{out}}{V_m} = A_v \cdot \frac{R_h}{R_{out} + R_h}$$

large small

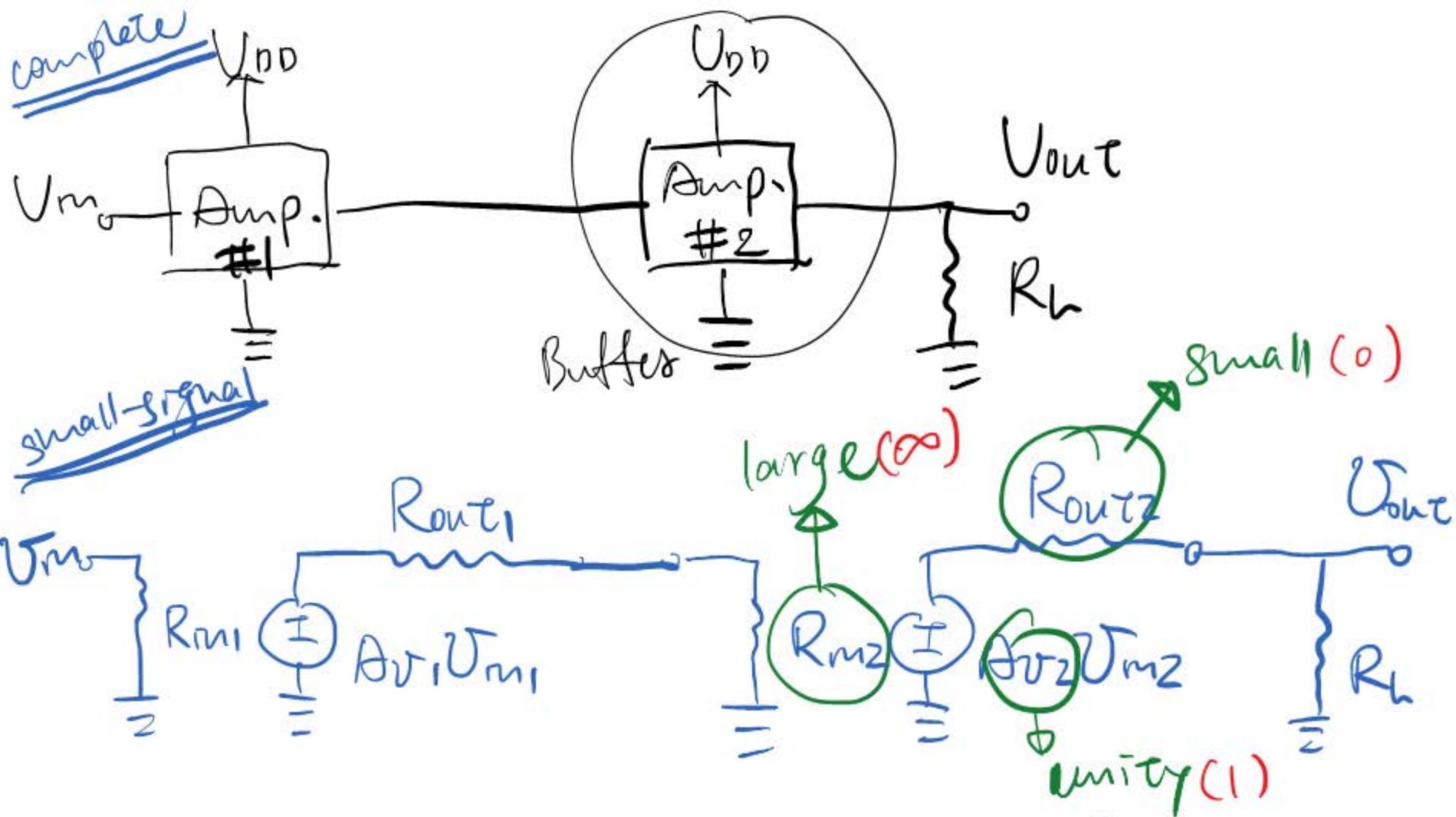$\neq A_v$ consumed
by the factor $\frac{R_h}{R_{out} + R_h}$




$$\frac{U_{out}}{U_m} = \theta_{V1} \frac{R_{m2}}{R_{out1} + R_{m2}} \theta_{V2} \frac{R_h}{R_{out2} + R_h}$$


large small

Ideal Amplifier


Voltage Amp.

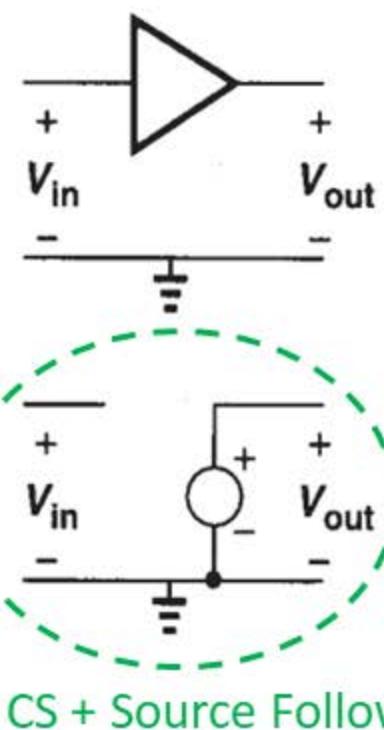


Transimpedance Amp.

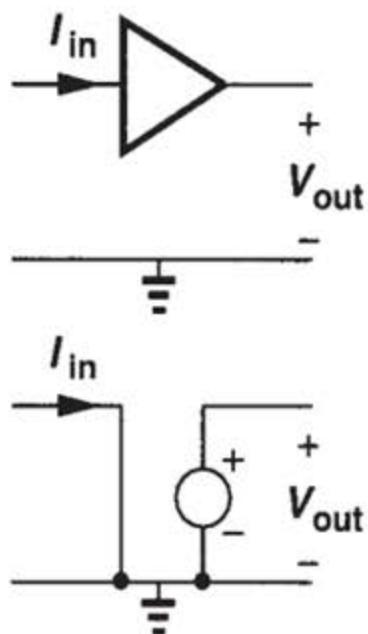


Transconductance Amp.

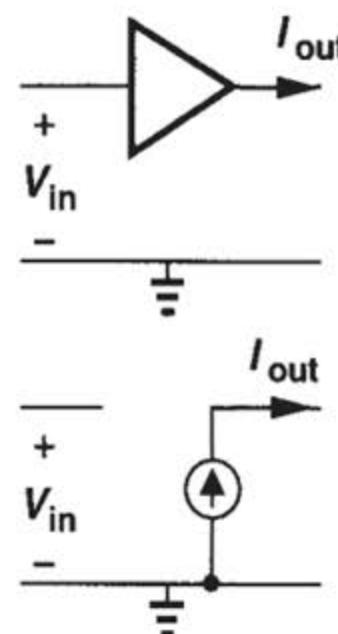


Current Amp.

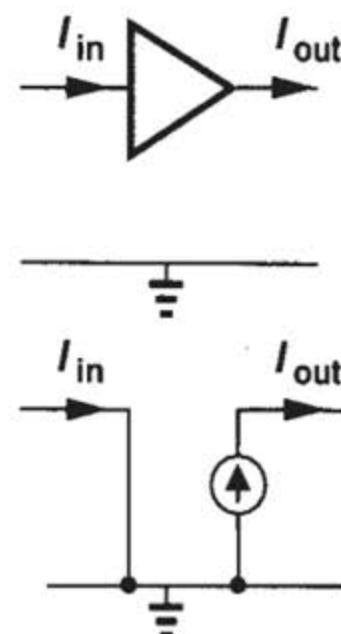

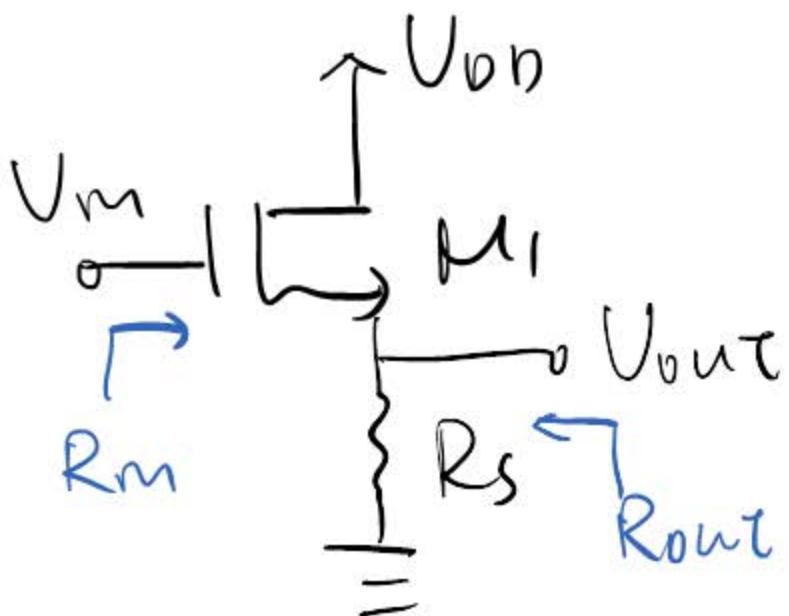- For driving a low impedance load, source follower, as a buffer, provides **no gain** but **large input impedance** and **low output impedance**.




small-signal

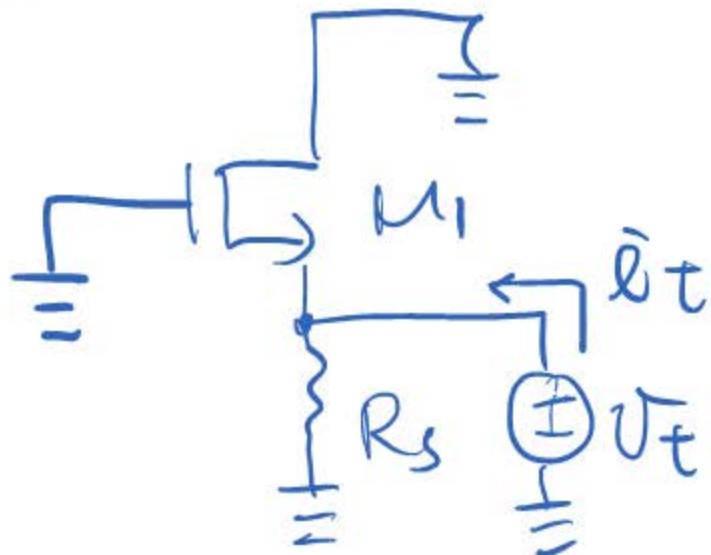

$$R_m = \infty$$

$$R_{out} = R_s \parallel r_{ds} / \left(g_m + g_{mb} \right)$$

$$R_{out} = \frac{U_f}{\delta t}$$

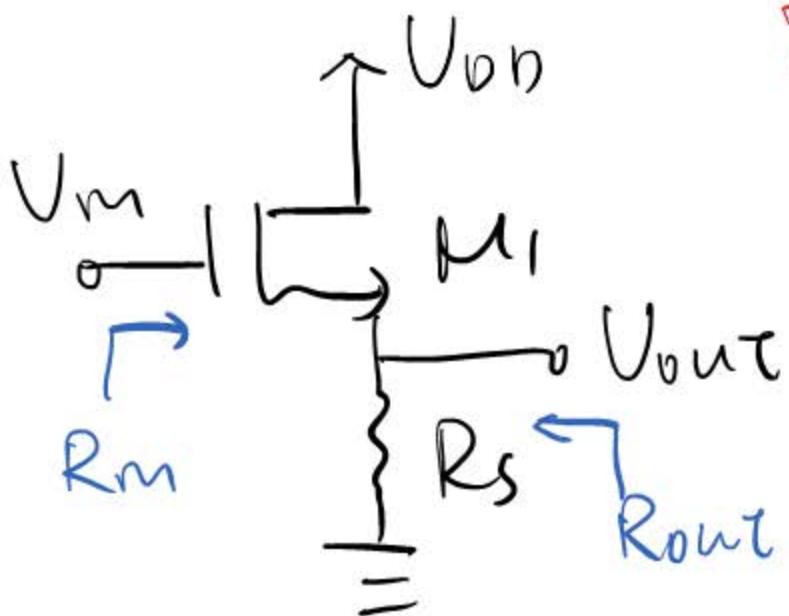



$$\begin{aligned} & \text{If } \gamma \neq 0, \beta \neq 0 \\ & R_m = \infty \end{aligned}$$

$$\begin{aligned} R_{out} &= R_s \parallel r_{o1} / \left(\frac{1}{g_{m1} + g_{mb1}} \right) \\ A_v &= \frac{U_{out}}{U_m} \end{aligned}$$

~~small-signal~~
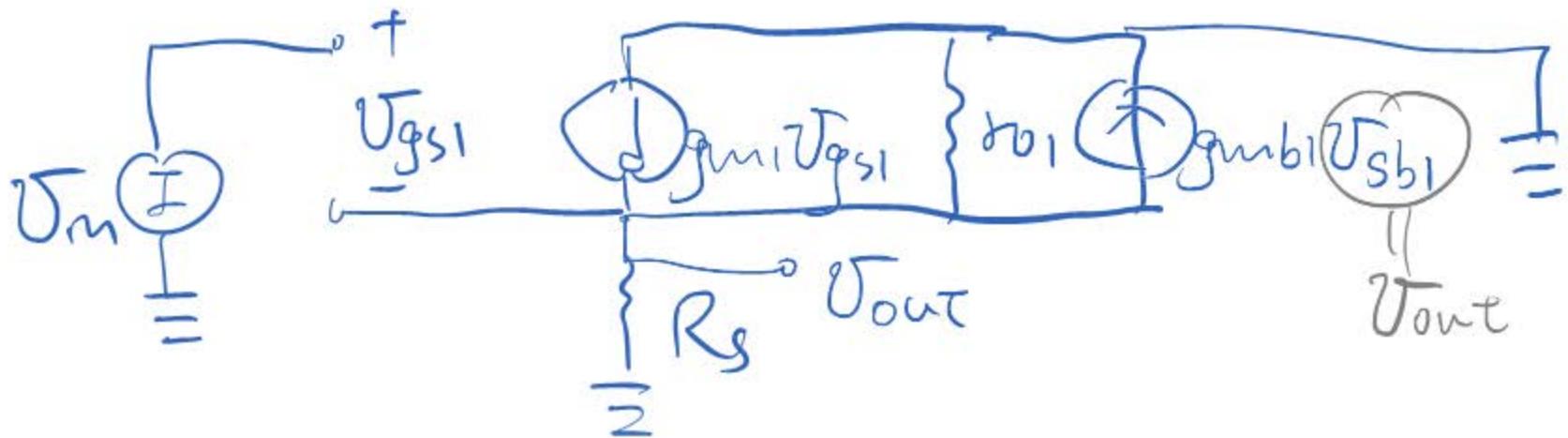
$$\frac{U_{out}}{R_s} + (U_{out} - U_m) g_{m1} + \frac{U_{out}}{r_{o1}} + g_{mb1} U_{out} = 0$$



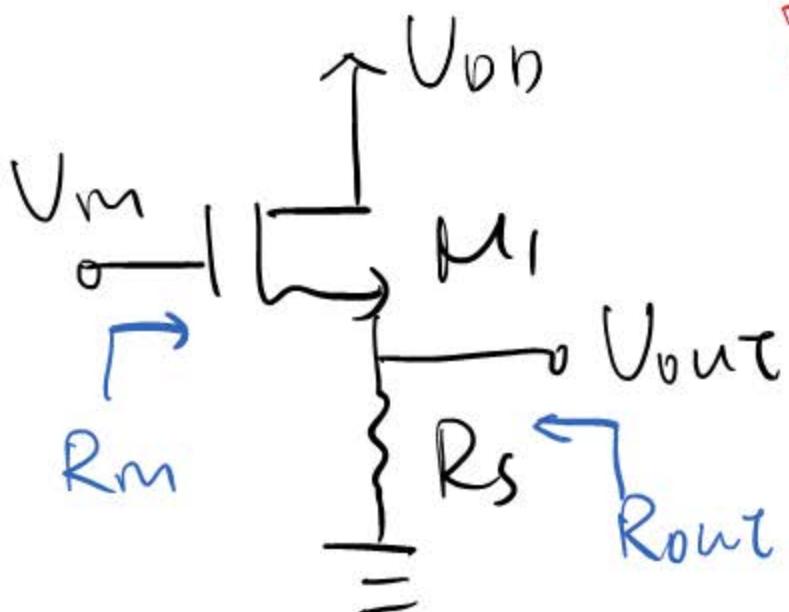



$$\gamma \neq 0, \delta \neq 0$$

$$G_m = ? = \frac{\dot{I}_{out}}{V_m} = g_m$$

$$\dot{I}_{out} = g_m I_m$$

small-signal

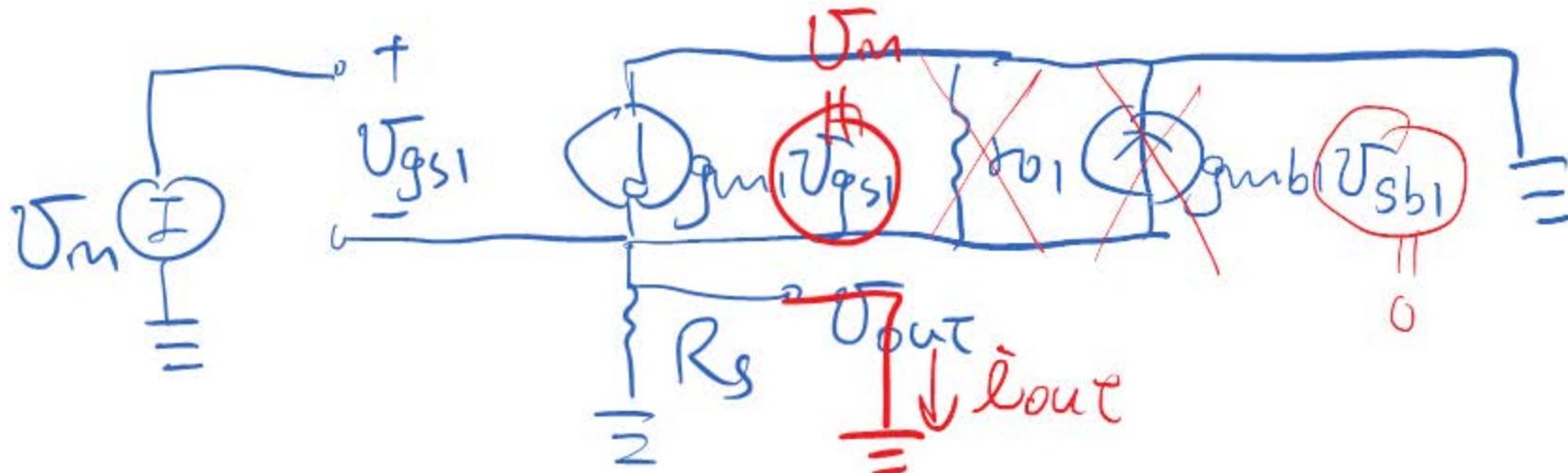

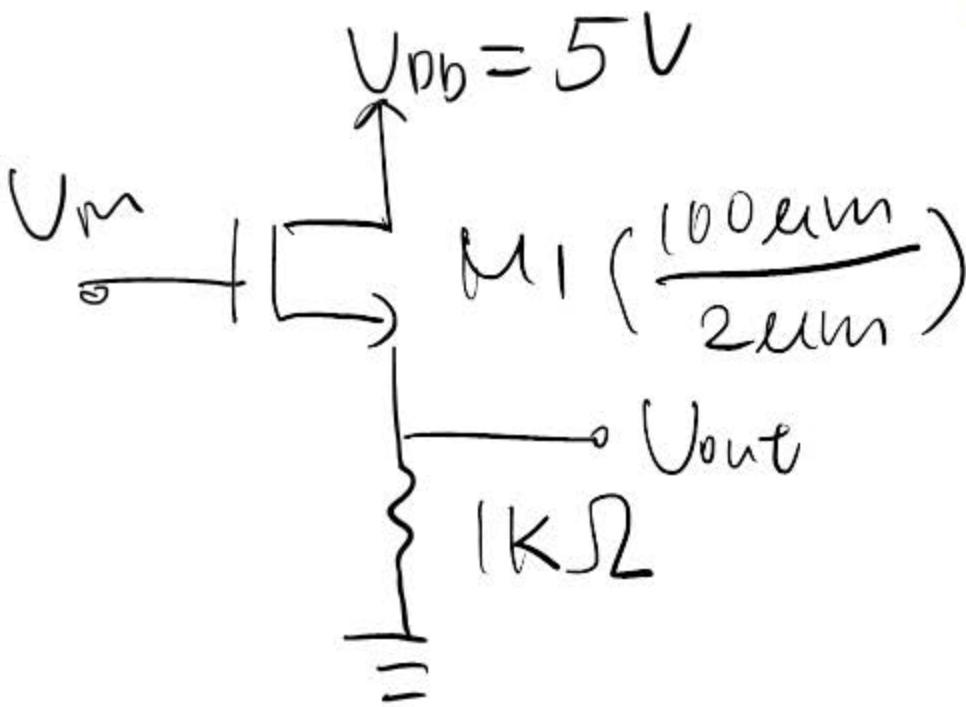

$\gamma \neq 0, \alpha \neq 0$
 $V_{out} = ?$
 DC biasing analysis.
 M₁ must be in sat.

$$\frac{V_{out}}{1k} = \frac{1}{2} \mu m C_{ox} \left(\frac{\omega}{L_{eff}} \right).$$

$$V_m = 3 + 0.0018m(2\pi V_{out})$$
 $V_{out} = ?$

$$(3 - V_{out} - V_{TH})^2$$


$$[1 + \chi(5 - V_{out})]$$

Source Follower

DC Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

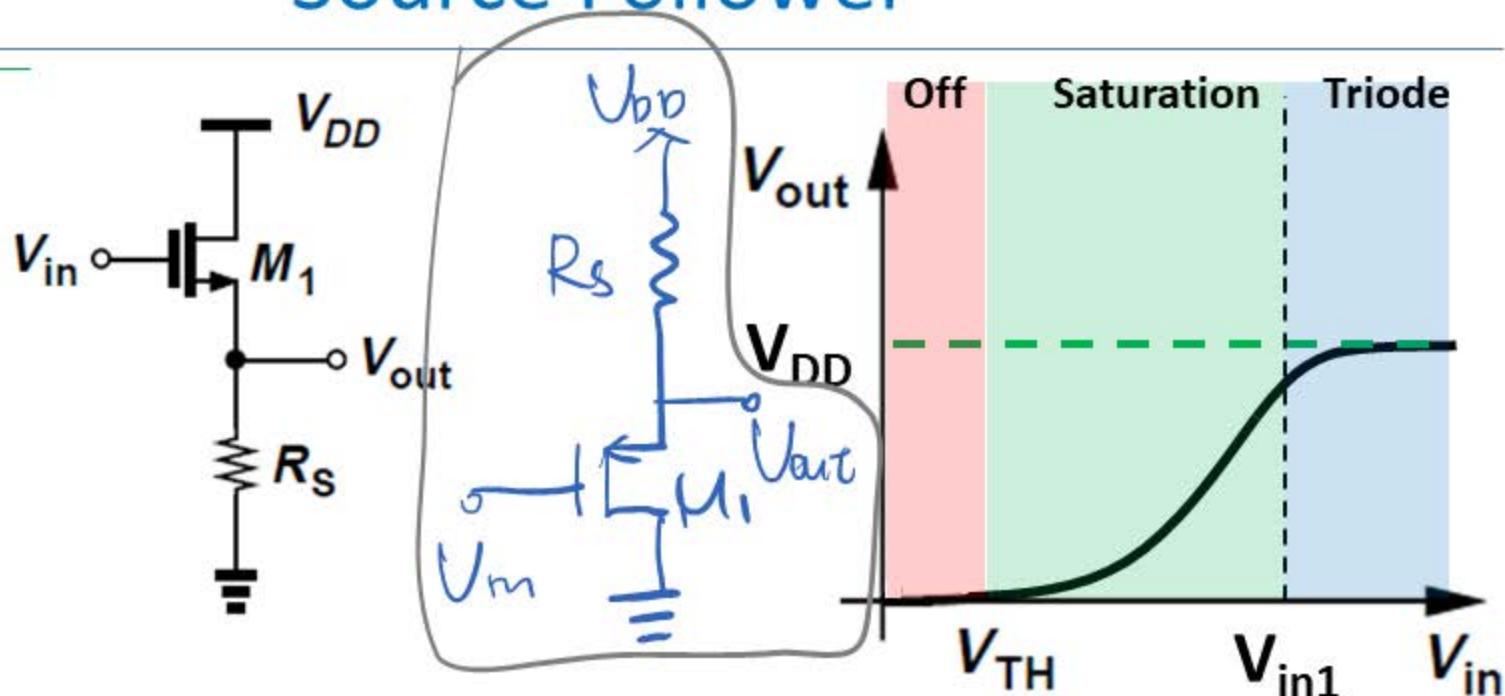

- $V_{in} < V_{TH} \rightarrow M_1 \text{ Off}$

$$V_{out} = 0$$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1 \text{ in Saturation}$

$$R_s \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eff}} (V_{in} - V_{out} - V_{TH})^2 = V_{out}$$

- $V_{in} > V_{in1} \rightarrow M_1 \text{ in Triode}$

$$R_s \mu_n C_{ox} \frac{W}{L_{eff}} \left[(V_{in} - V_{out} - V_{TH})(V_{DD} - V_{out}) - \frac{1}{2} (V_{DD} - V_{out})^2 \right] = V_{out}$$

$$\begin{aligned} V_{DD} - V_{out} &= V_{in1} - V_{out} - V_{TH} \\ \rightarrow V_{in1} &= V_{DD} + V_{TH} \end{aligned}$$

Source Follower

DC Analysis

$\lambda = 0$

$\gamma \neq 0$

- $V_{in1} > V_{in} > V_{TH} \rightarrow M_1 \text{ in Saturation}$

$$V_{out\tau} = V_{SB}$$

$$R_S \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})^2 = V_{out}$$

$$R_S \frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2(V_{in} - V_{out} - V_{TH}) \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH}}{\partial V_{in}} \right) = \frac{\partial V_{out}}{\partial V_{in}}$$

$$R_S \left[\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH}) \right] \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH}}{\partial V_{out}} \frac{\partial V_{out}}{\partial V_{in}} \right) = \frac{\partial V_{out}}{\partial V_{in}}$$

$= gm$

$\frac{\partial V_{TH}}{\partial V_{out}} = \frac{V_{TH}}{2V_{SB}}$

$= \eta = \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}}$

$$A_v = \frac{gmR_S}{1 + gmR_S(1 + \eta)} = \frac{gmR_S}{1 + (gm + gmb)R_S} \approx \frac{1}{1 + \eta}$$


If $(gm + gmb)R_S \gg 1$

Source Follower

Small-signal Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

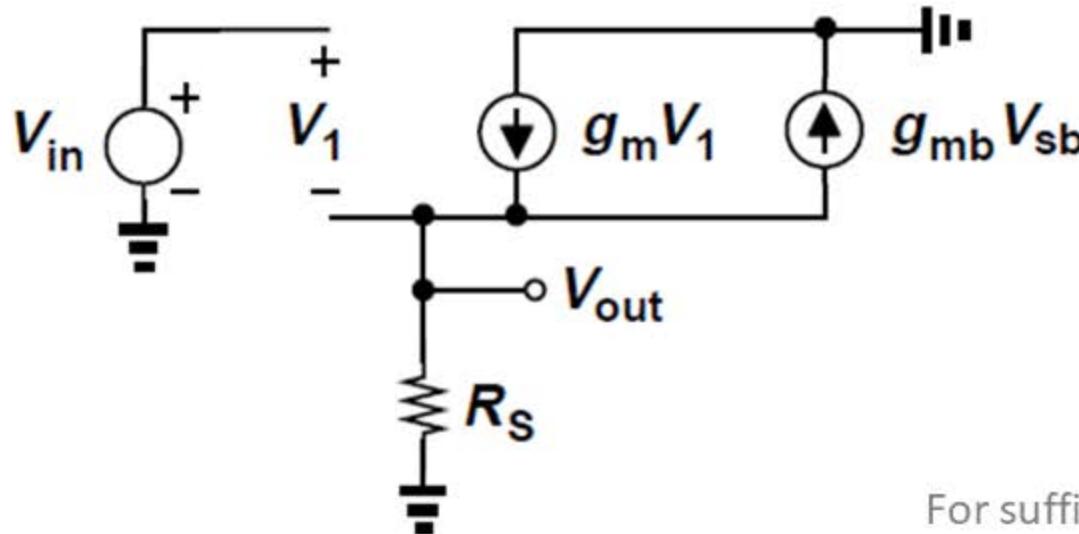


For sufficiently large
 V_{in} , I_D and thus gm .

$$G_m = gm$$

$$R_{out} = R_S \parallel \left(\frac{1}{gm + gmb} \right)$$

$$A_v = \frac{gmR_S}{1 + (gm + gmb)R_S} \approx \frac{1}{1 + \eta}$$

If $(gm + gmb)R_S \gg 1$

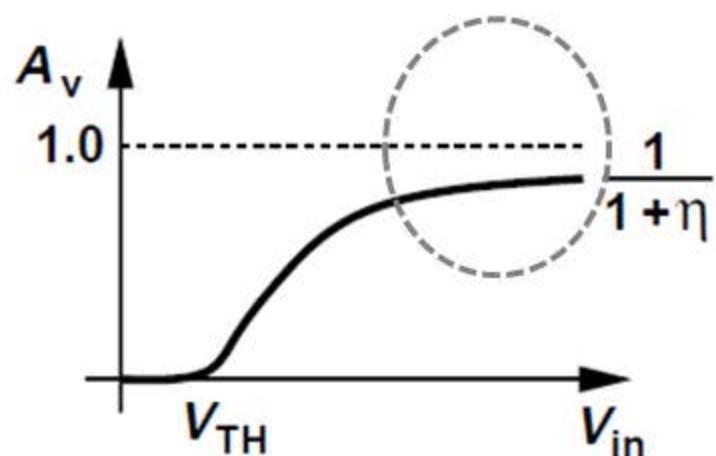


Source Follower

Small-signal Analysis

$$\lambda \neq 0$$

$$\gamma \neq 0$$

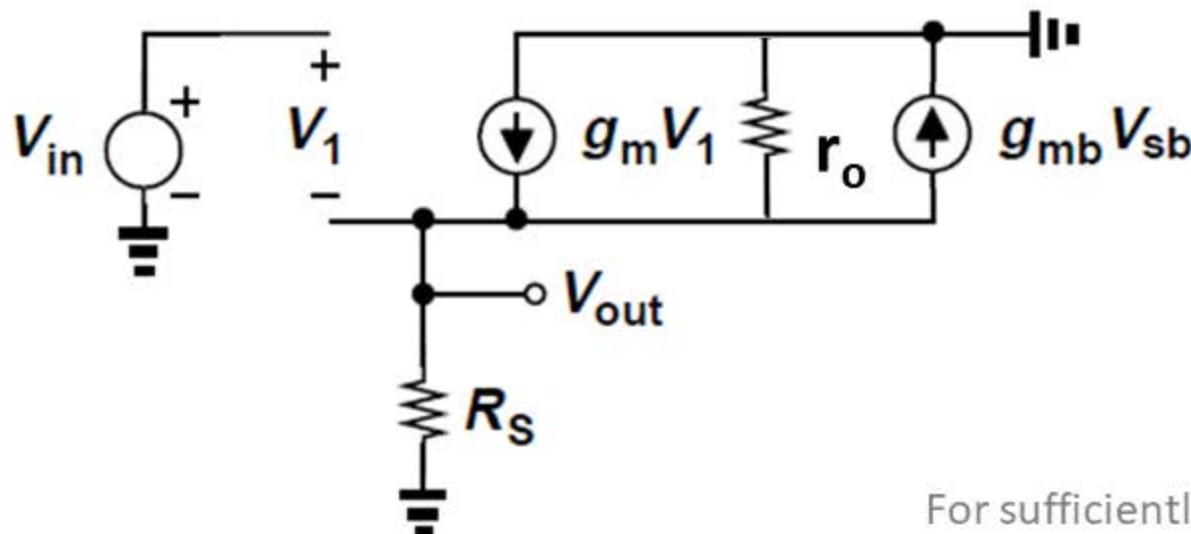


For sufficiently large V_{in} , I_D and thus gm .


$$G_m = gm$$

$$R_{out} = r_o \parallel R_S \parallel \left(\frac{1}{gm + gmb} \right)$$
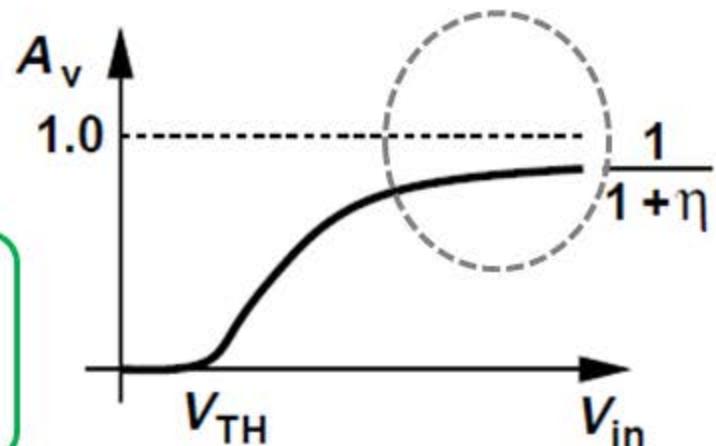
$$A_v = \frac{gmr_o R_S}{r_o + R_S + (gm + gmb)r_o R_S} \approx \frac{1}{1 + \eta}$$




If $(gm + gmb)r_o R_S \gg r_o$ and R_S

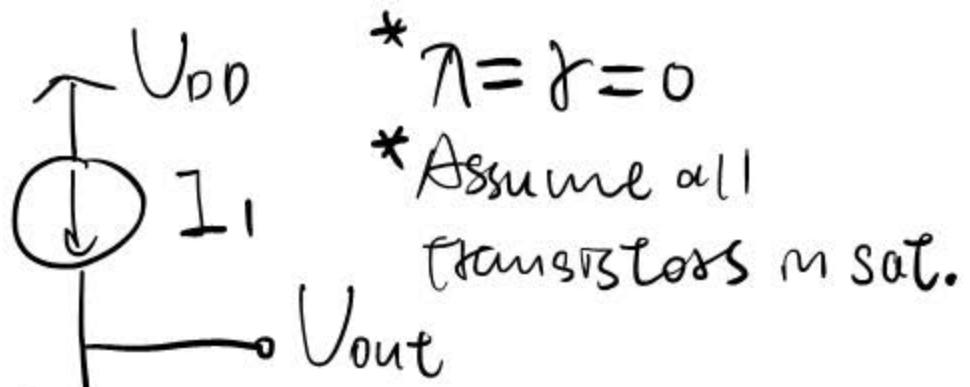

$$V_{BS1} > 0 \Rightarrow |V_{THP}| > 0.8 \text{ if } \gamma \neq 0$$

$$\frac{1}{2} \left(\frac{1}{L_P C_{ox}} \right) \left(\frac{\omega}{\omega_{eff}} \right) (V_{out} - V_{in} - |V_{THP}|)^2 = I_1$$

constants

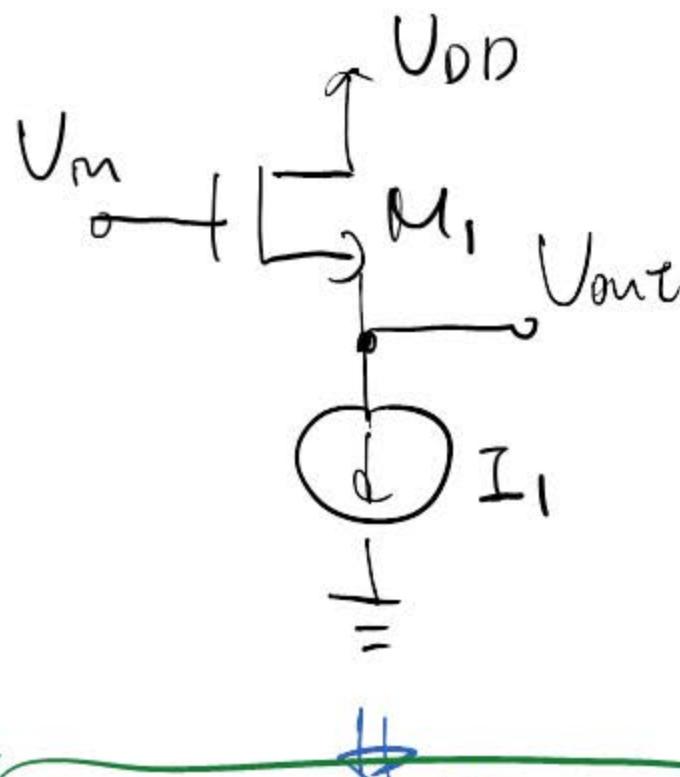



$$\lambda \neq 0, \gamma \neq 0$$

All transistors operate in SAT.



$$R_m = ? \quad R_{out} = ? \quad A_v = ?$$

$$R_m = \infty$$
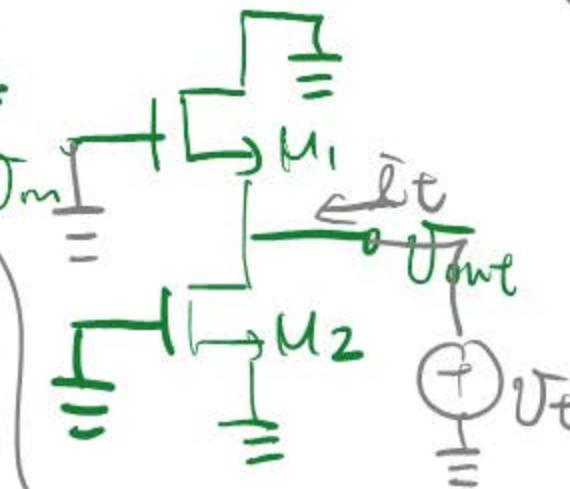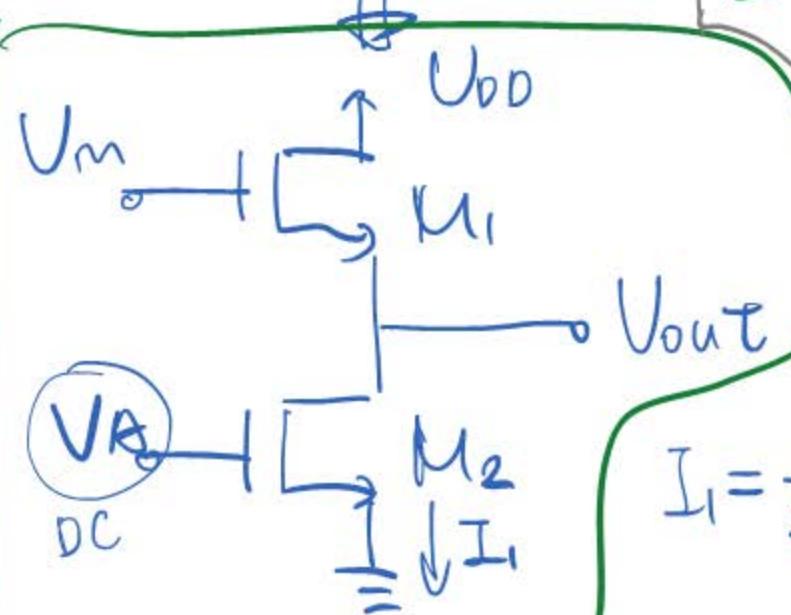
$$R_{out} = r_{o2} // g_{m1} // \left(\frac{1}{g_{m1} + g_{mb1}} \right)$$


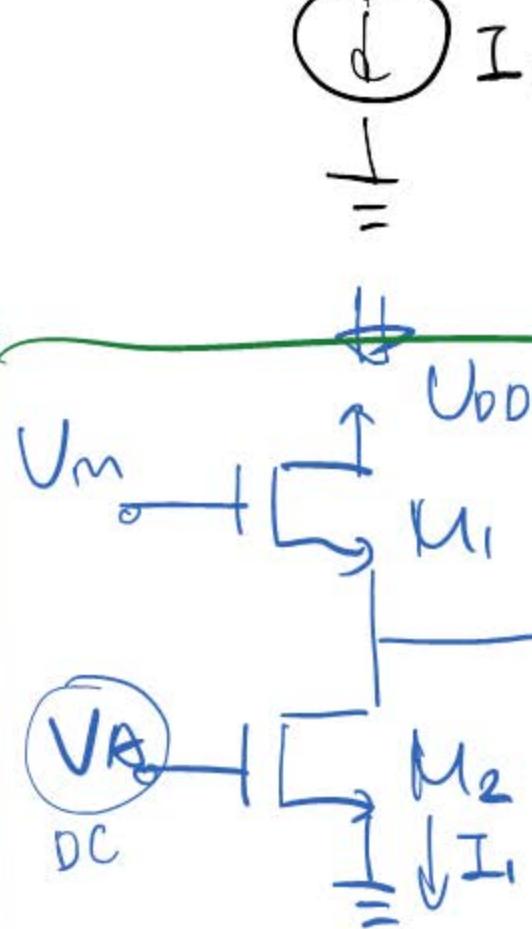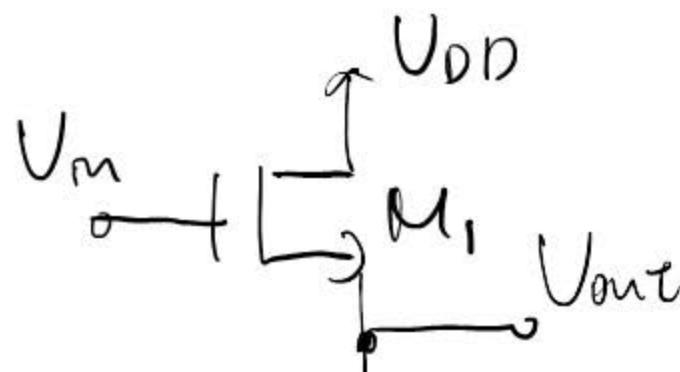
$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (U_A - 0.7)^2 (1 + \gamma V_{out})$$



$$\lambda \neq 0, \gamma \neq 0$$

All transistors operate in SAT.


$$R_m = ? \quad R_{out} = ? \quad A_v = ?$$

$$= G_m R_{out}$$

$$R_m = \infty$$

$$R_{out} = r_{o2} // g_{m1} // \left(\frac{1}{g_{m1} + g_{mb1}} \right)$$

$$G_m = g_{m1}$$


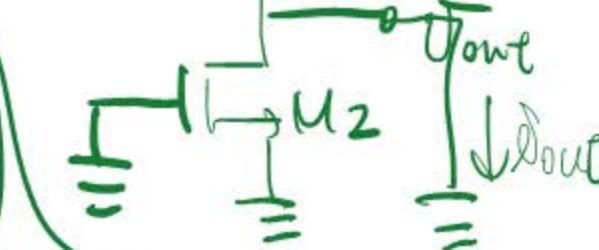


$$I_1 = \frac{1}{2} \mu_n C_{ox} \left(\frac{W}{L_{eff}} \right) (U_A - 0.7)^2 (1 + \gamma V_{out})$$

Source Follower with Current Source

DC Analysis

$$\lambda = 0 \\ \gamma \neq 0$$

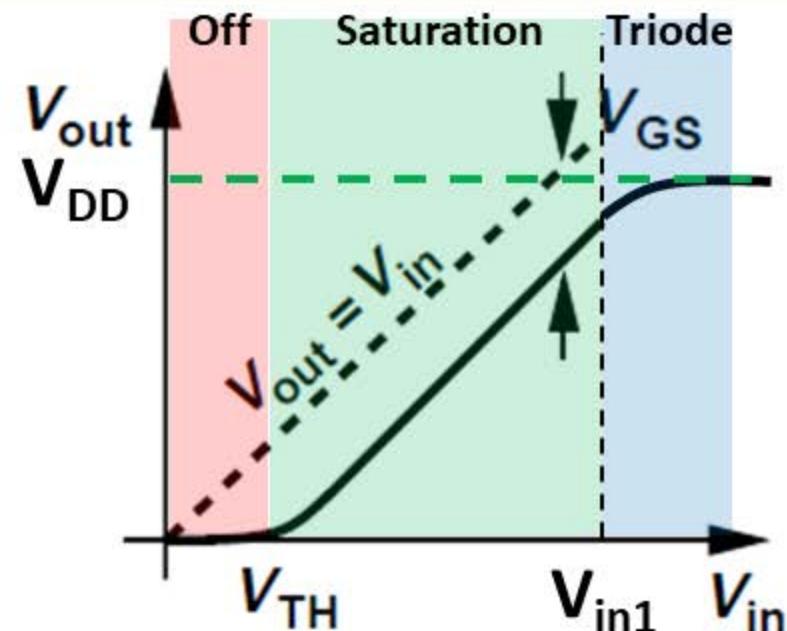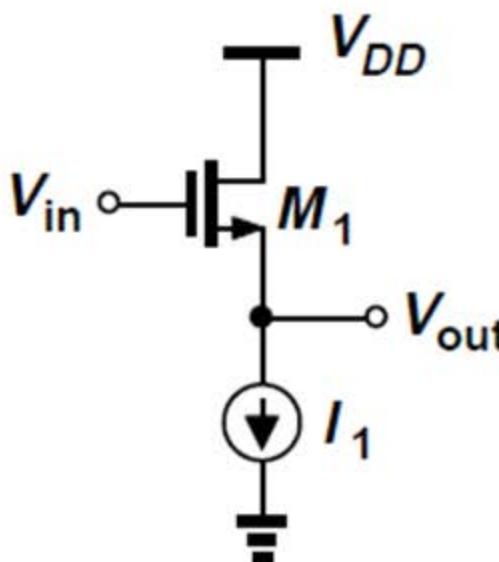

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH})^2 = I_1$$

$$\frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2(V_{in} - V_{out} - V_{TH}) \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \frac{\partial V_{TH}}{\partial V_{in}} \right) = 0$$

$$\boxed{\mu_n C_{ox} \frac{W}{L} (V_{in} - V_{out} - V_{TH}) \left(1 - \frac{\partial V_{out}}{\partial V_{in}} - \boxed{\frac{\partial V_{TH}}{\partial V_{out}} \frac{\partial V_{out}}{\partial V_{in}}} \right) = 0}$$

$= gm$ $= \eta$

$$A_v = \frac{1}{1 + \eta}$$


If $\gamma = 0$, $A_v = 1$.

Source Follower with Current Source

Small-signal Analysis

$$\lambda = 0$$

$$\gamma \neq 0$$

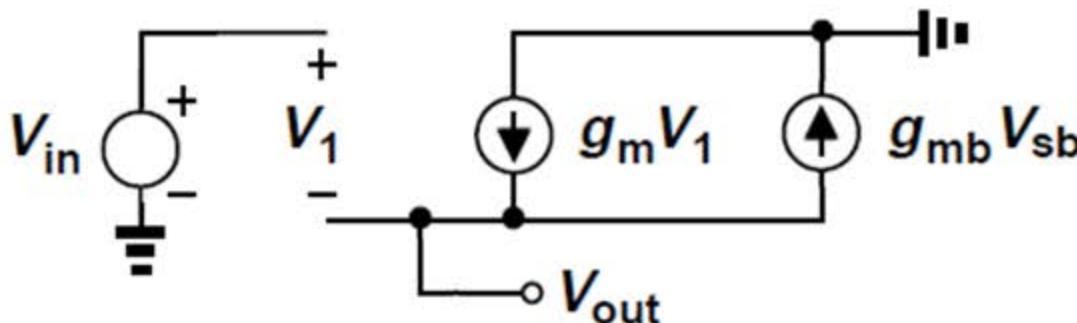


$$G_m = gm$$

$$R_{out} = \frac{1}{gm + gmb}$$

$$A_v = \frac{1}{1 + \eta}$$

If $\gamma = 0$, $A_v = 1$.

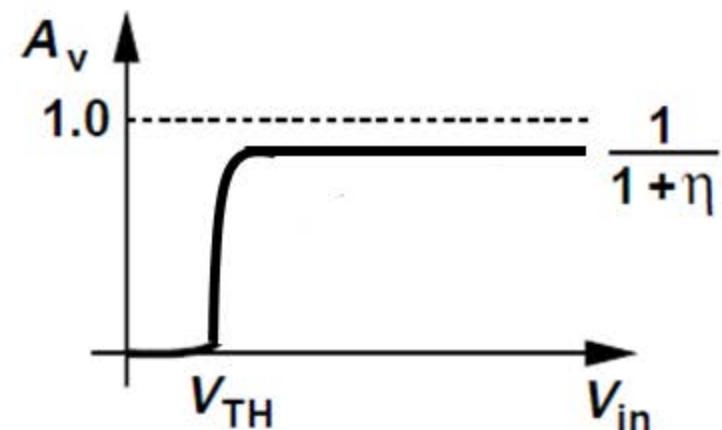


Source Follower with Current Source

Small-signal Analysis

$$\lambda \neq 0$$

$$\gamma \neq 0$$

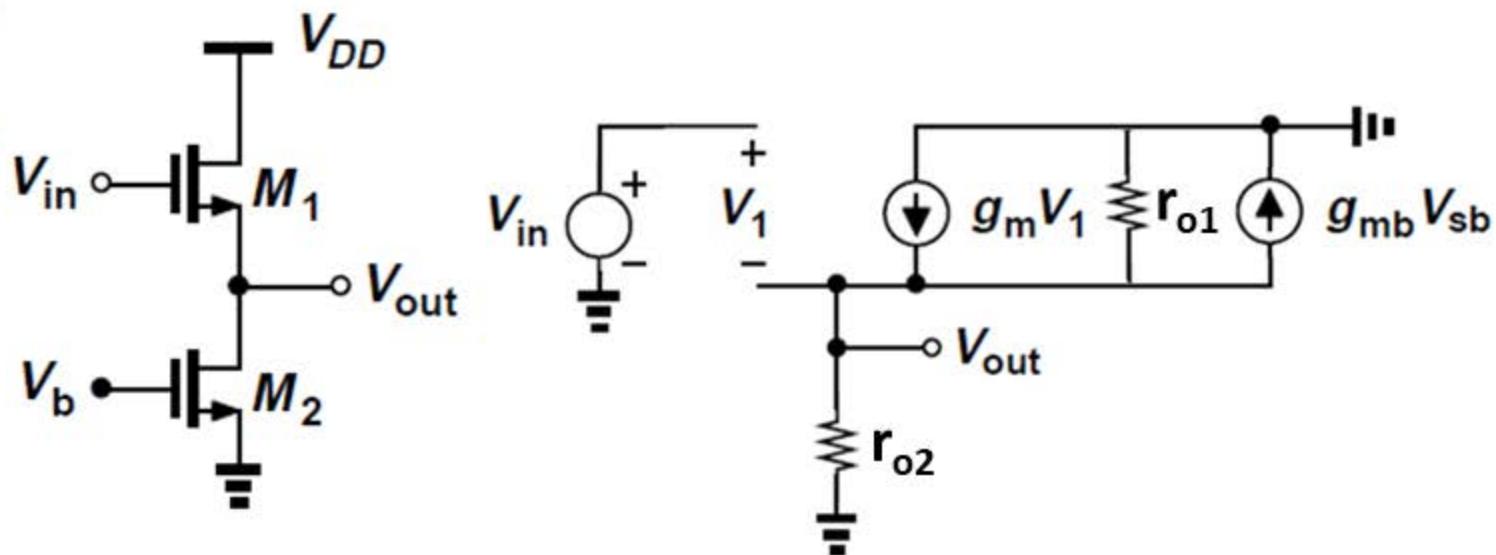

$$G_m = g_{m1}$$

$$R_{out} = r_{o1} \parallel r_{o2} \parallel \left(\frac{1}{g_{m1} + g_{mb1}} \right)$$

$$A_v = \frac{g_m r_{o1} r_{o2}}{r_{o1} + r_{o2} + (g_m + g_{mb}) r_{o1} r_{o2}}$$

If r_{o1} and r_{o2} large,
 A_v is linear.



Source Follower with Current Source ($V_{BS} = 0$)

93

Small-signal Analysis

$$\lambda \neq 0$$

$$\gamma \neq 0$$

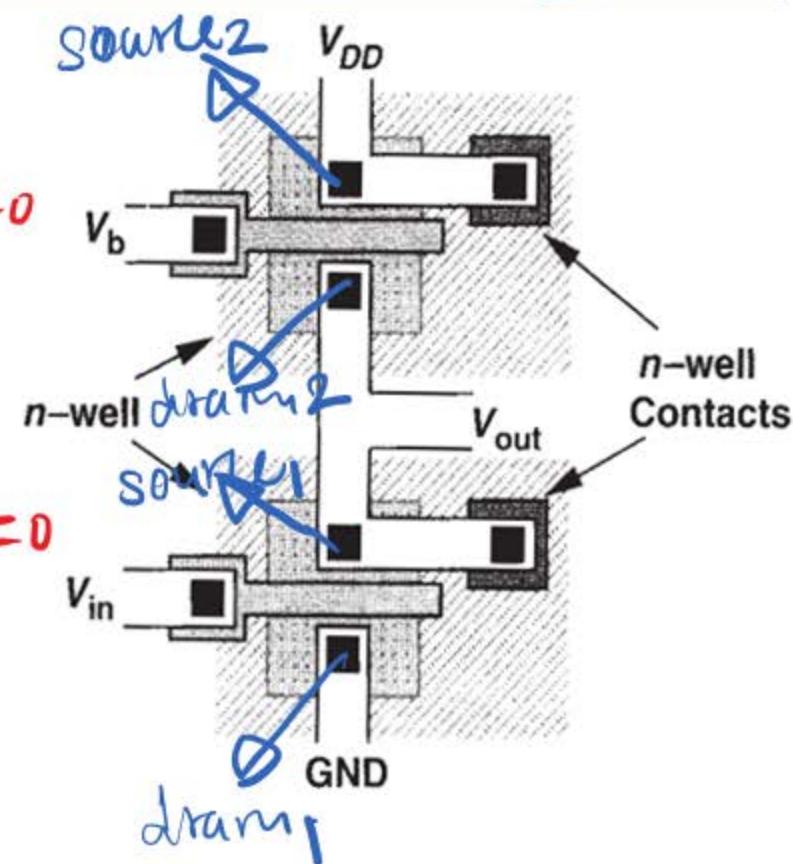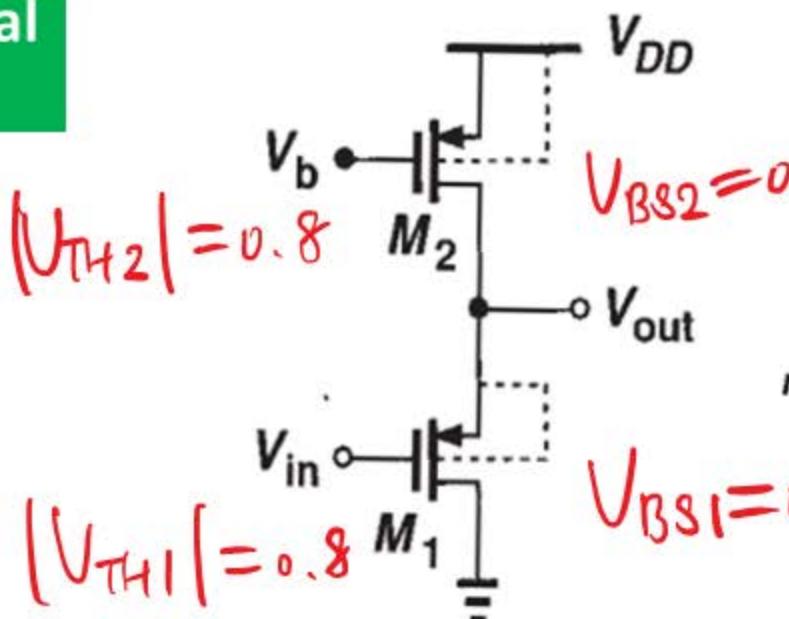



$$G_m = gm_1$$

$$R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_1}$$

$$A_v = \frac{gm_1 r_{o1} r_{o2}}{r_{o1} + r_{o2} + gm_1 r_{o1} r_{o2}}$$

- The sacrifice here is the higher output impedance due to smaller mobility of holes relative to electrons.

Source Follower as Level Shifter

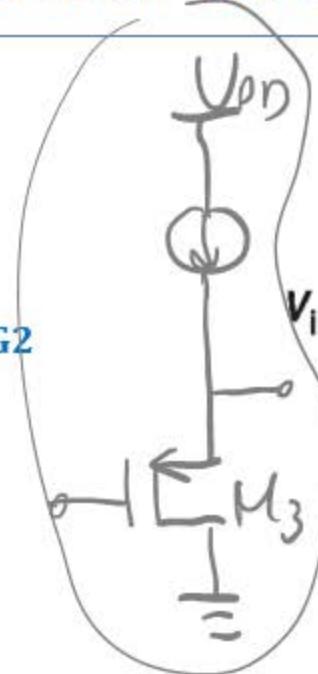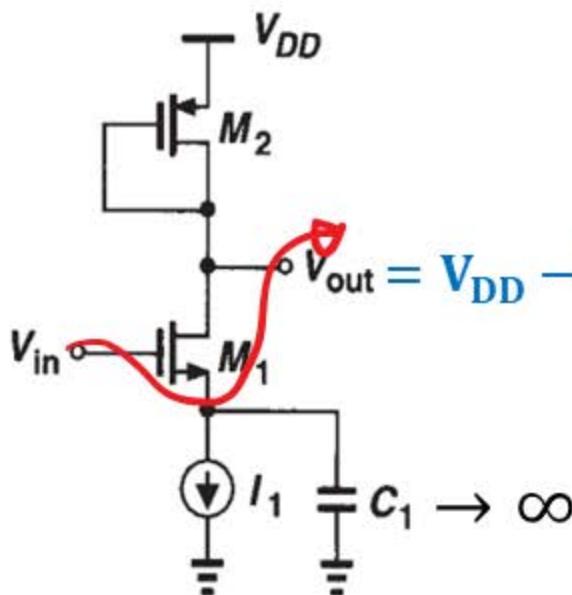

$$V_{in} \leq V_{DD} - V_{SG2} + V_{TH1}$$


$$V_{in} - V_{GS3} \leq V_{DD} - V_{SG2} + V_{TH1}$$

$$\begin{cases} G_m = -gm_1 \\ R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_2} \end{cases}$$

$$\begin{cases} G_{m(left)} = gm_3 \\ R_{out(left)} = r_{o3} \parallel \frac{1}{gm_3 + gmb_3} \end{cases}$$

$$\begin{cases} R_{in(right)} = \infty \\ G_{m(right)} = -gm_1 \\ R_{out(right)} = r_{o1} \parallel r_{o2} \parallel \frac{1}{gm_2} \end{cases}$$

Source Follower as Level Shifter

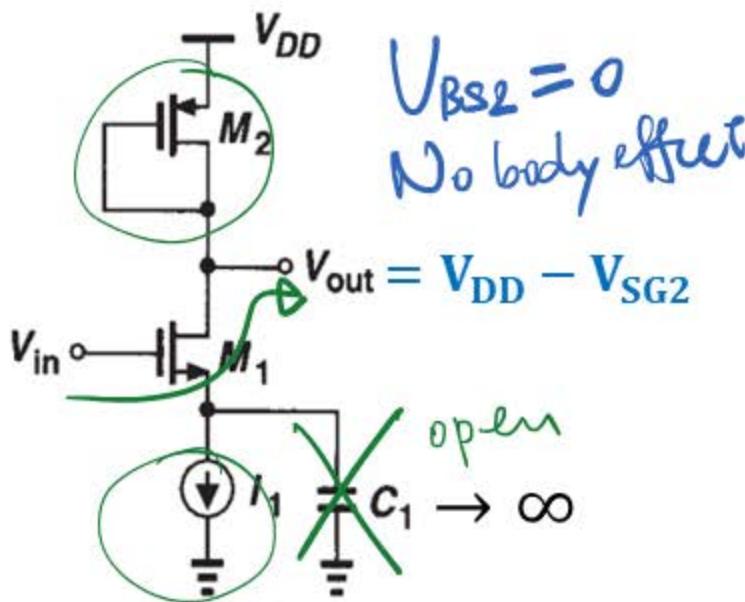

$$V_{in} \leq \frac{V_{DD} - V_{SG2}}{V_{out}} + V_{TH1}$$

When V_m higher than
 $V_{out} + V_{TH1}$, M_1 will
 be driven into triode.



1° DC biasing analysis

$$I_1 = \frac{1}{2} \mu_P C_{ox} \left(\frac{W}{L_{left}} \right) V_{DD}$$

$$(V_{DD} - V_{out} - (V_{TH2})^{0.8})^2 \\ [C_1 + \gamma(V_{DD} - V_{out})]$$

$$V_{out} = ?$$


Source Follower as Level Shifter

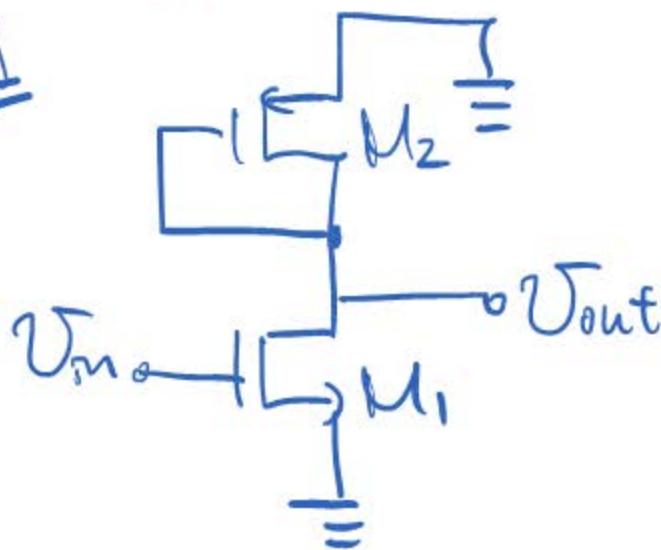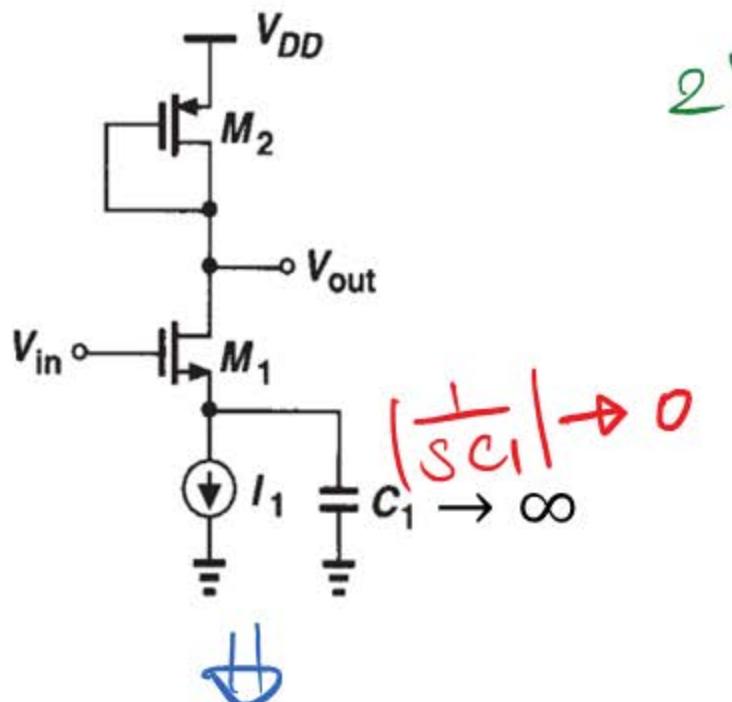


2° Small signal analysis

$$\left\{ \begin{array}{l} G_m = -g_{m1} \\ R_{out} = r_{o1} \parallel r_{o2} \parallel \frac{1}{g_{m2}} \\ R_m = \infty \end{array} \right.$$
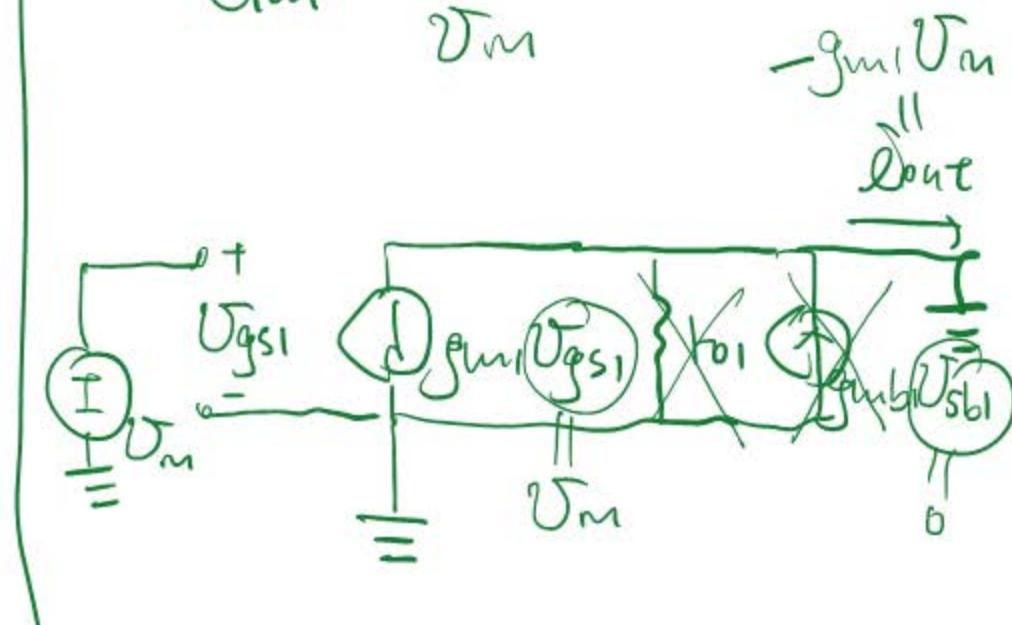
$$G_m = \frac{\partial U_{out}}{\partial U_m}$$




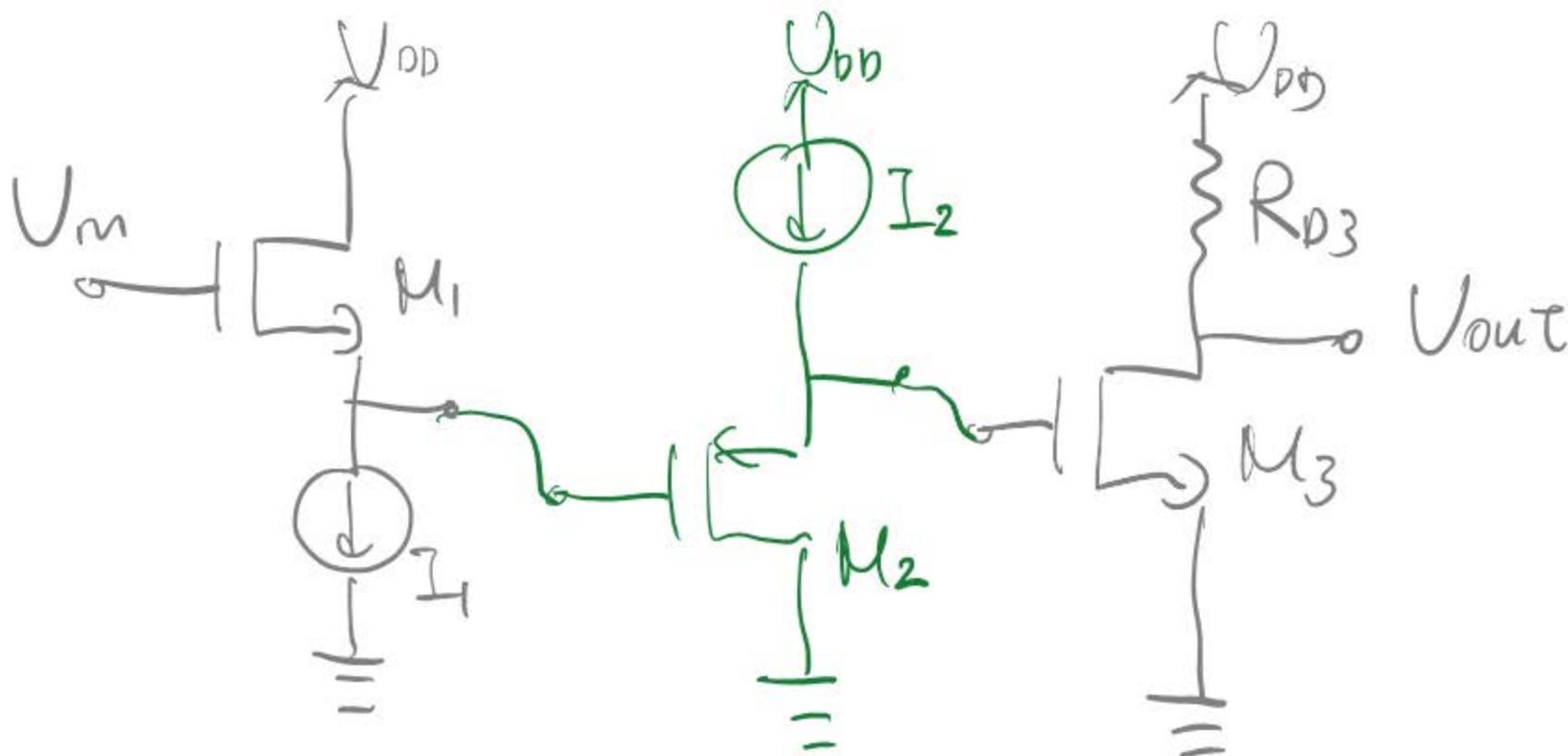

Assume $\lambda = t = 0$, $A_V = ?$


$$A_V = 1 \times 1 \times (-g_m R_{D3})$$

CS + Source Follower

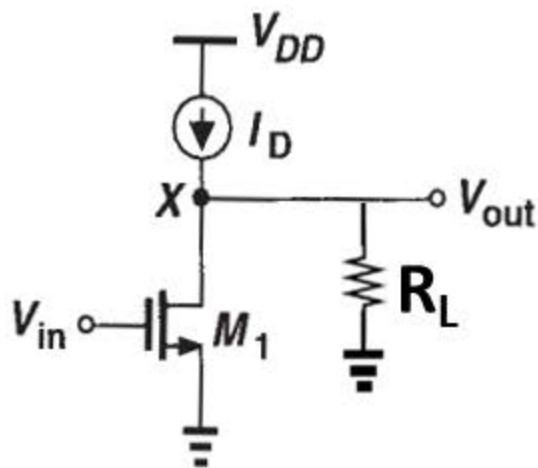

$$A_v = -gm_1(r_{o1} \parallel R_L)$$

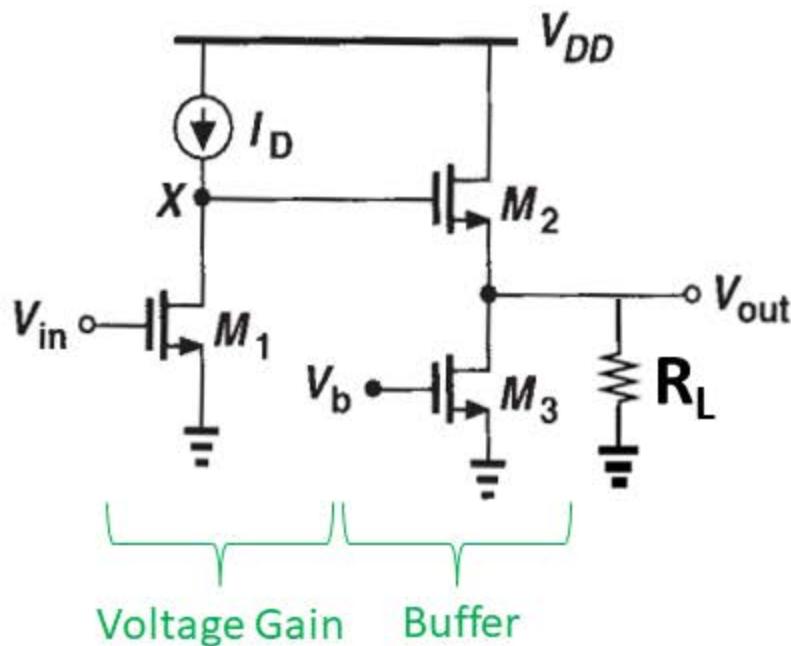
- Voltage gain severely reduced when R_L very small



$$A_v = -gm_1 r_{o1} \times$$


$$gm_2 \left(r_{o2} \parallel \frac{1}{gm_2 + gmb_2} \parallel r_{o3} \parallel R_L \right)$$

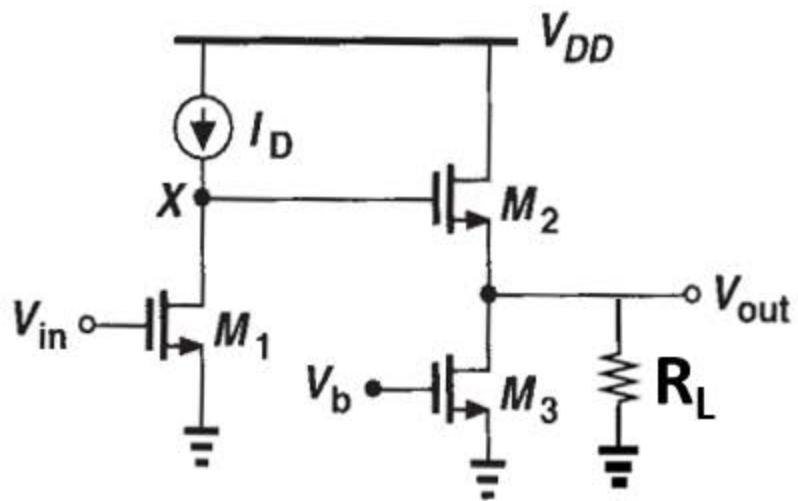- Voltage gain maintained when R_L very small



$$A_v = -g_{m1} r_{o1} \times$$
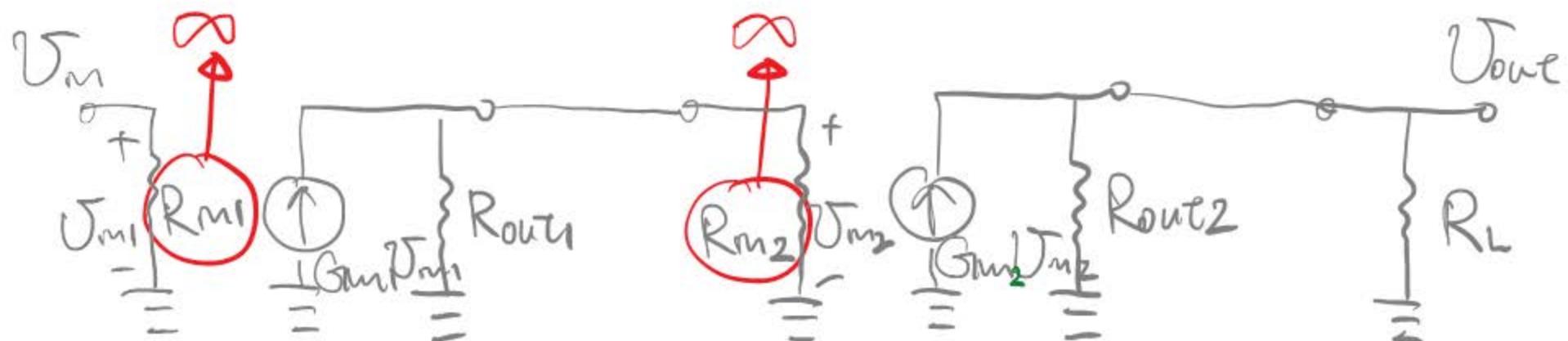
$$g_{m2} \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \parallel r_{o3} \parallel R_L \right)$$



$$G_{m1} = -g_{m1}$$


$$R_{out1} = r_{o1}$$

$$G_{m2} = g_{m2}$$

$$R_{out2} = r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \parallel r_{o3}$$

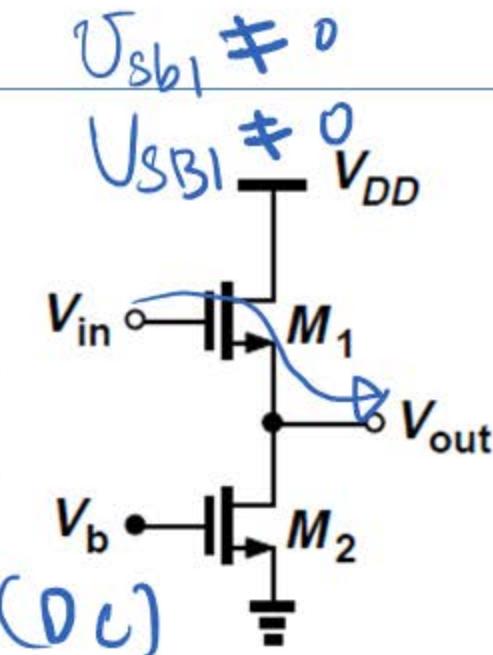Example

$(W/L)_1 = 20/0.5$, $I_D = 0.2 \text{ mA}$, $V_{THO} = 0.6 \text{ V}$, $2\phi_F = 0.7 \text{ V}$, $\mu_n C_{ox} = 50 \mu\text{A/V}^2$, $\gamma = 0.4 \text{ V}^{1/2}$ and $\lambda = 0$. (a) Calculate V_{out} for $V_{in} = 1.2 \text{ V}$. (b) Minimum $(W/L)_2$ for which M_2 remains saturated.



Solution:

$$(a) I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L_{eq}} (V_{in} - V_{out} - V_{TH1})^2 \rightarrow V_{out} = 0.153 \text{ V} = V_{SB1}$$

$$V_{TH1} = V_{THO} + \gamma (\sqrt{2\Phi_F + V_{out}} - \sqrt{2\Phi_F}) = 0.635 \text{ V} \rightarrow V_{out} \approx 0.118 \text{ V}$$

$$(b) V_{out} = 0.118 \text{ V} \geq V_{GS2} - V_{TH2} \text{ for } M_2 \text{ to stay in Sat.}$$


$$I_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS2} - V_{TH2})^2 \rightarrow \left(\frac{W}{L}\right)_2 \geq \frac{283}{0.5}$$

Example

Calculate the small signal voltage gain of the circuit below.

Assume all in Sat.

Assume $\gamma \neq 0$, $\beta \neq 0$

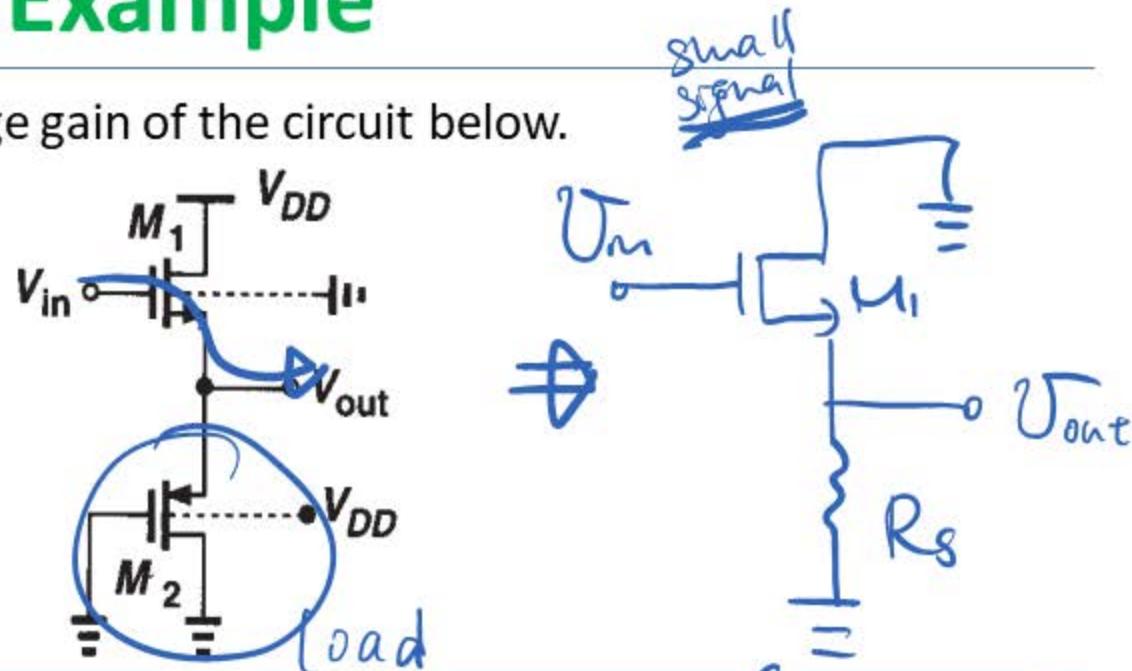

Solution:

$$G_m = g_{m1}$$

$$R_{out} = \frac{1}{g_{m1} + g_{mb1}} \parallel r_{o1} \parallel \frac{1}{g_{m2} + g_{mb2}} \parallel r_{o2}$$

$$A_v = G_m R_{out}$$


$$R_s = r_{o2} \parallel \left(\frac{1}{g_{m2} + g_{mb2}} \right)$$

CS }
SF }

both are Voltage-in-Voltage-out
amplifiers.

Common-Gate (CG)

Current-in-Voltage-out

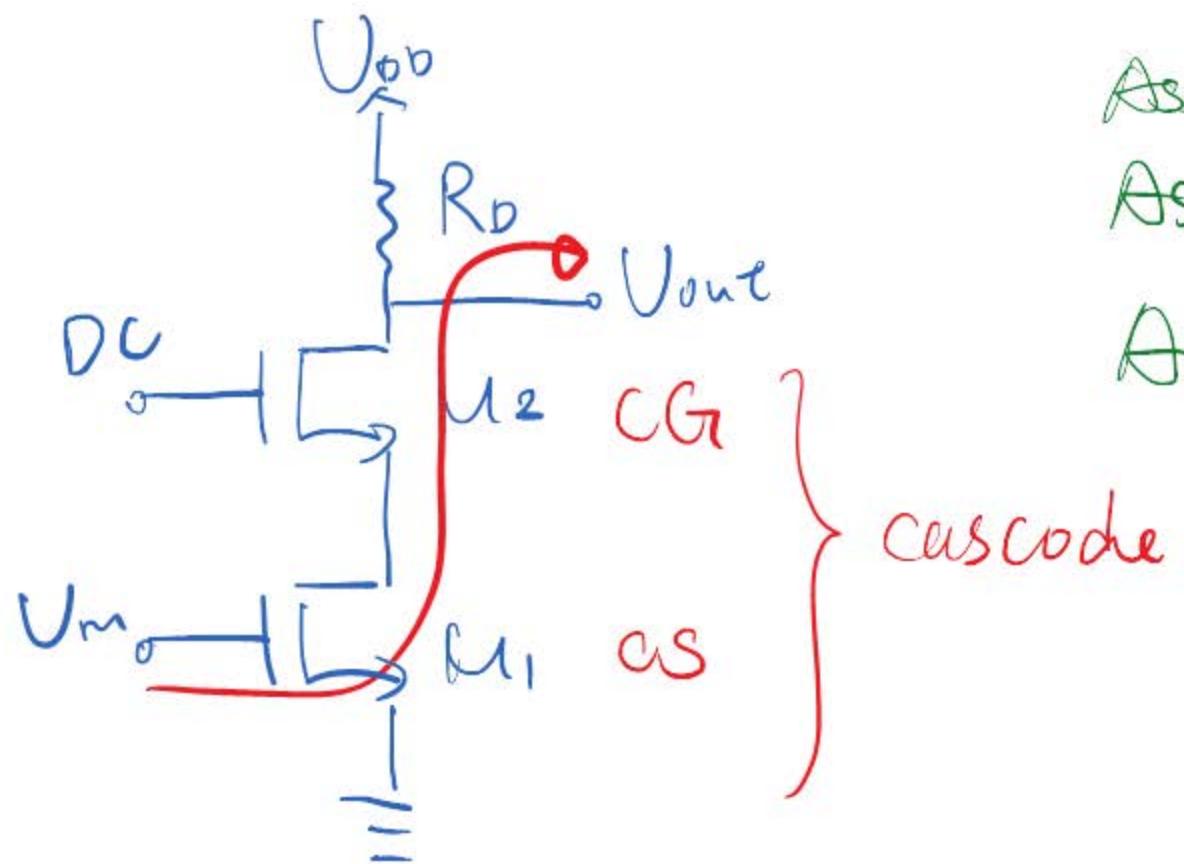


Assume M_1 and M_2 in Sat.

Assume $\lambda \neq 0$, $\delta \neq 0$

$$A_V = ?$$

Small signal

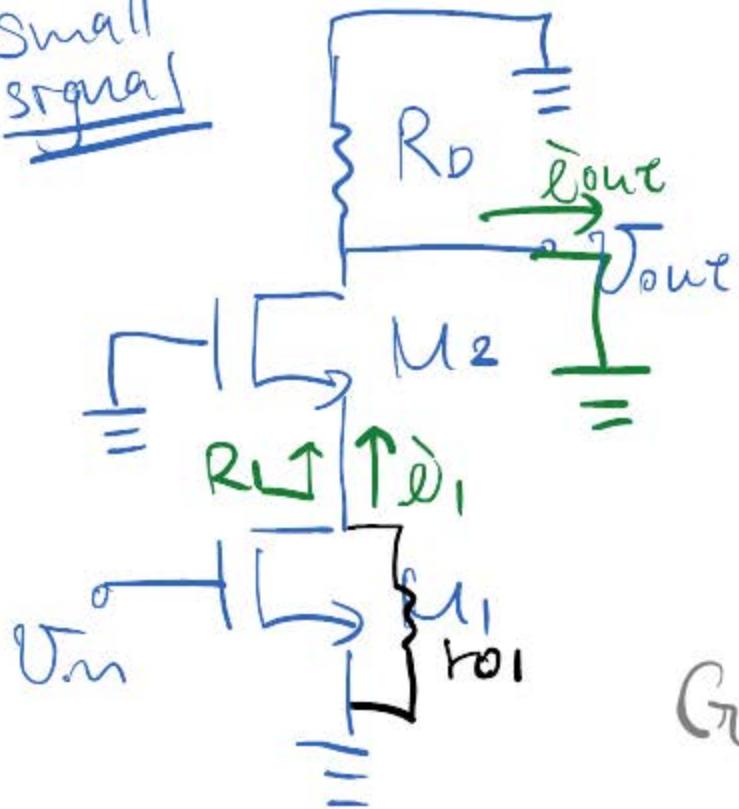


$$G_m = \dot{i}_{\text{out}} / V_m$$

$$\dot{i}_1 = \dot{i}_{\text{out}}$$


$$R_i = r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}}$$

$$\dot{i}_1 = (-g_{m1} V_m) \frac{r_{o1}}{\dot{i}_{\text{out}} + R_i}$$

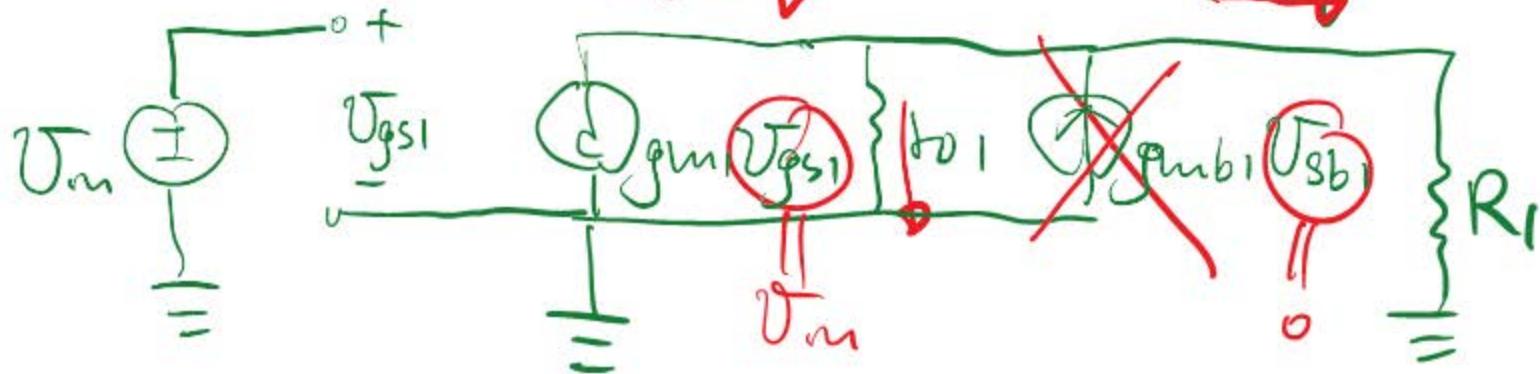
$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)}$$



Small signal


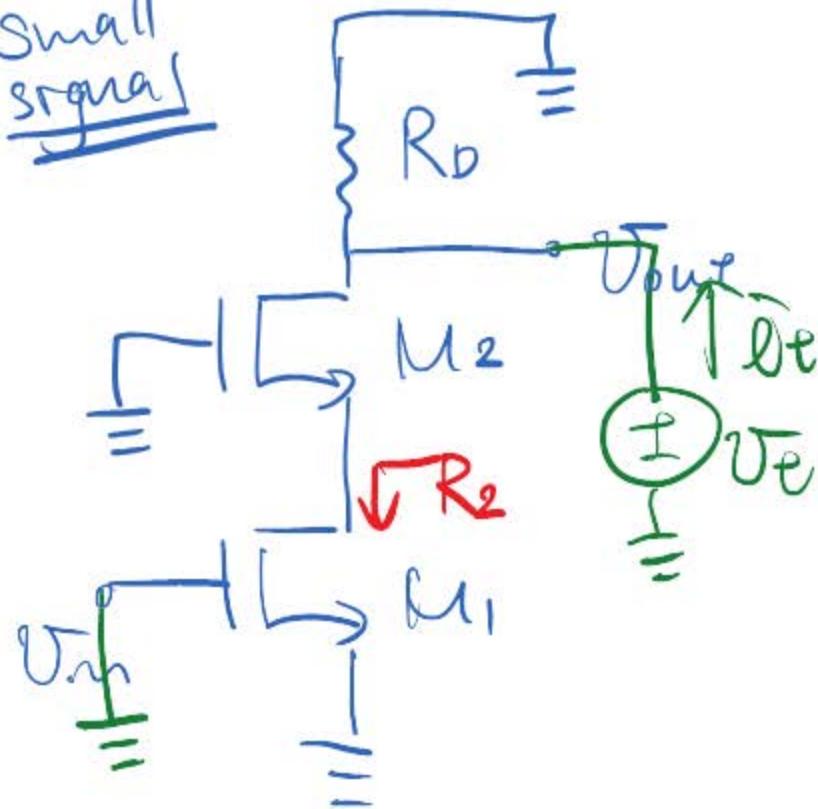


*

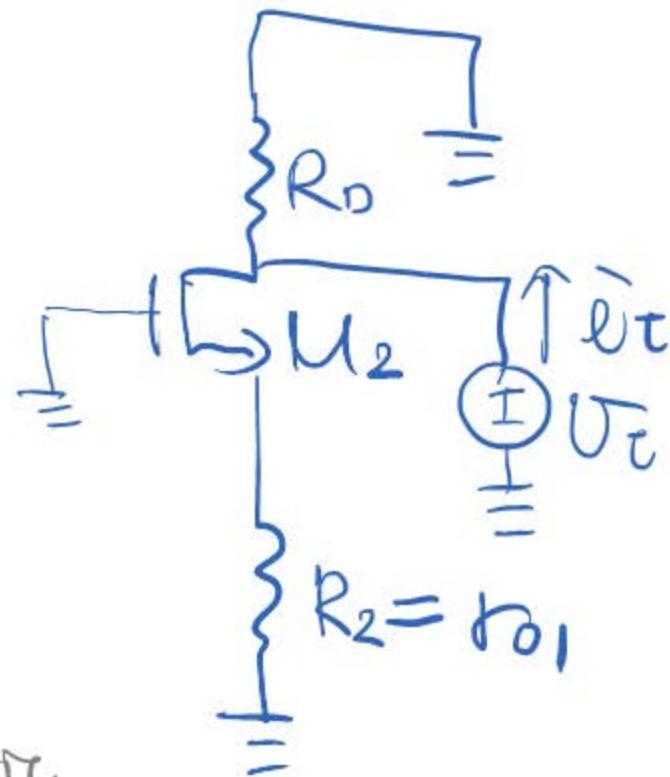

intrinsic
gain of M_2

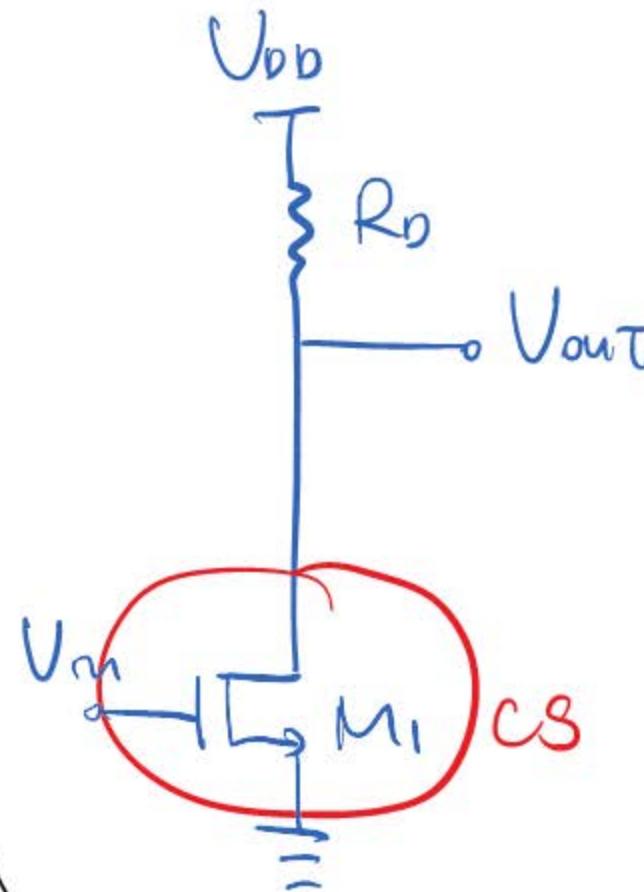
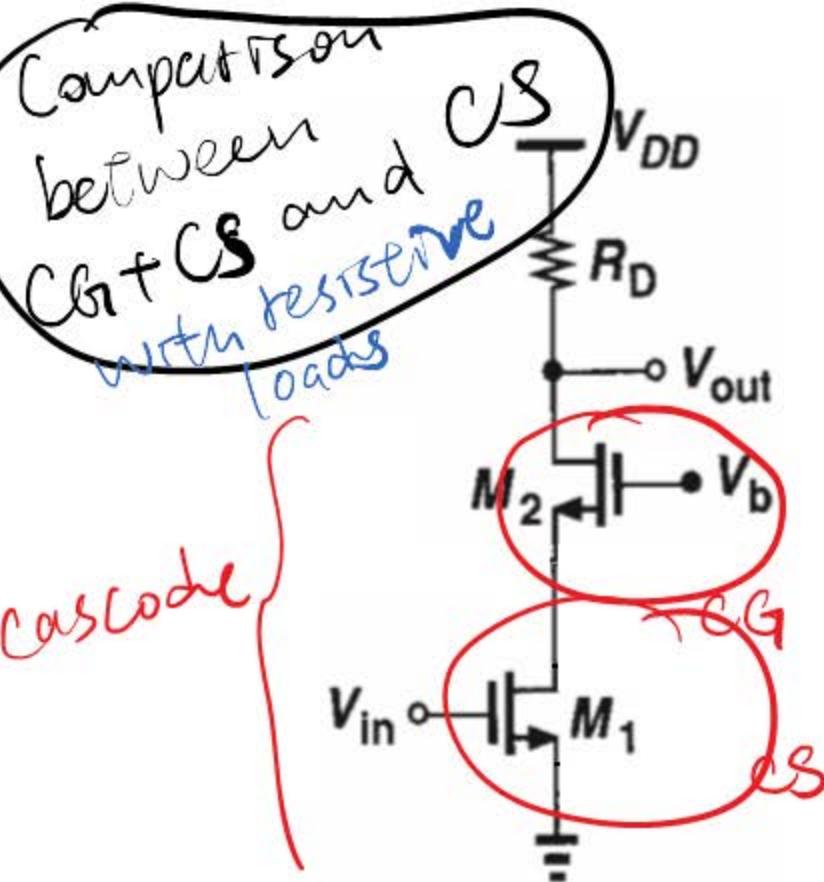
$$R_{out} = R_D / \left[r_{o2} + r_{o1} + \underbrace{(g_{m2} + g_{mb2}) r_{o2} r_{o1}}_{\text{intrinsic gain of } M_2} \right]$$





$$G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left(r_{o2} \| \frac{1}{g_{m2} + g_{ub2}} \right)}$$

$$R_{out} = R_D / \left[r_{o2} + r_{o1} + (g_{m2} + g_{ub2}) r_{o2} r_{o1} \right]$$

$$R_{out} = r_{o1} / R_D$$

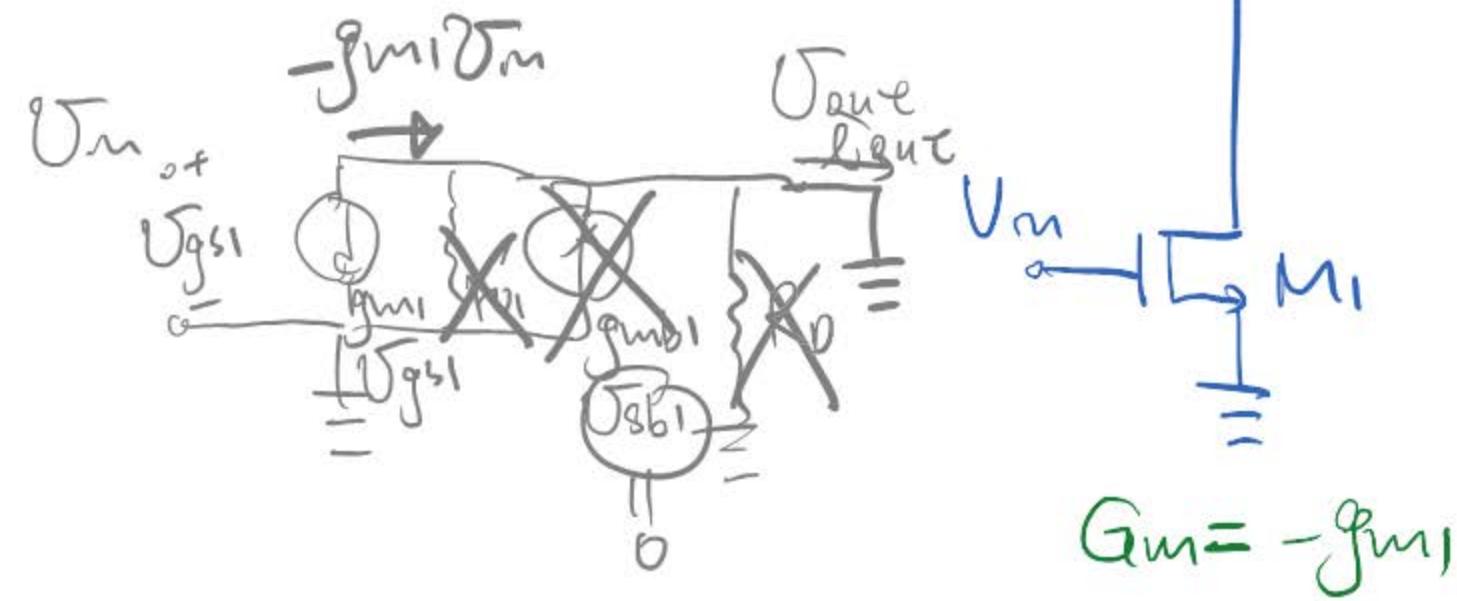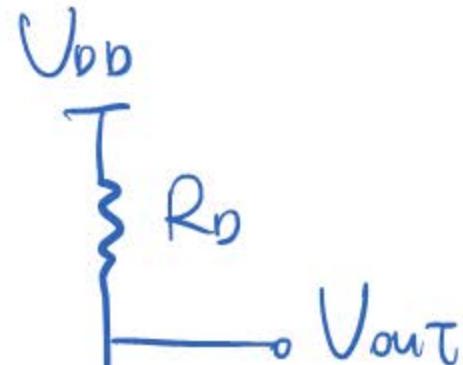

$$I_{out} = -jg_m1 U_m$$

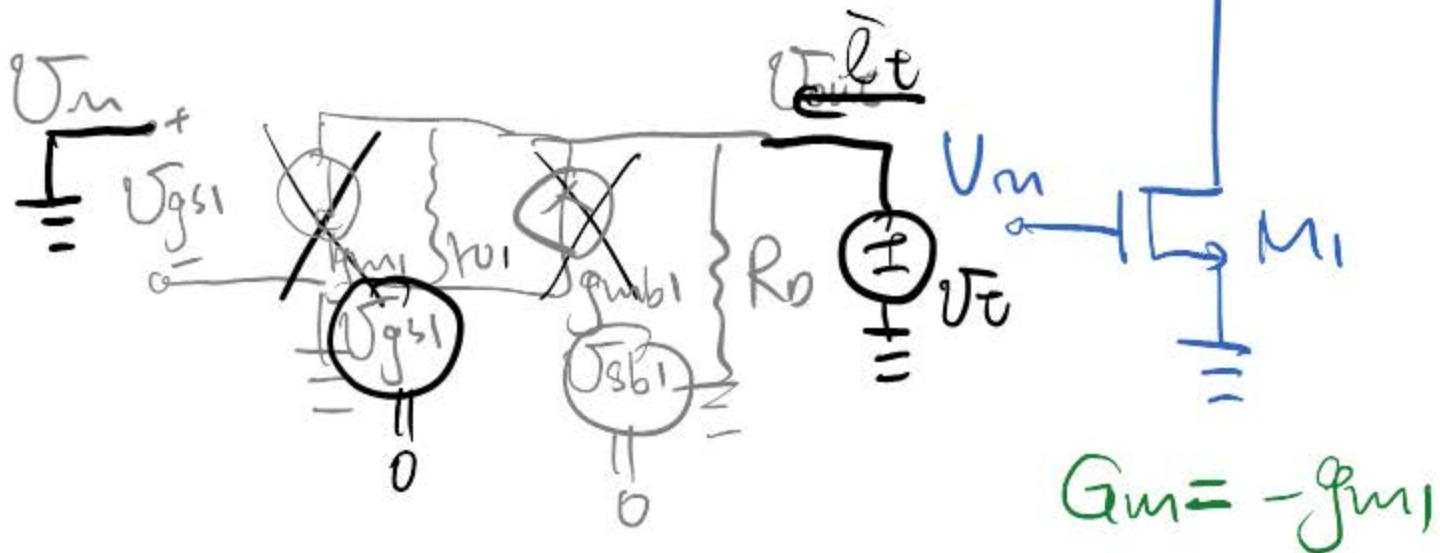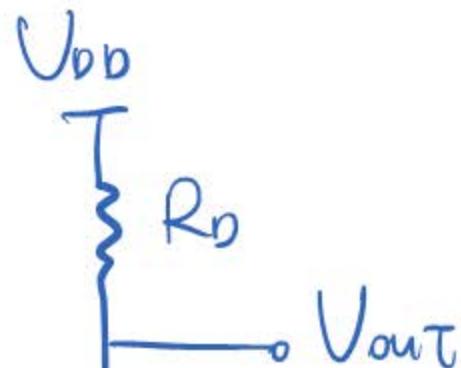


$$R_{out} = \frac{U_c}{\partial I_E} = R_D \parallel r_{D1}$$

Comparison between CS and C_{BS} + CS with current source loads via U_b

* Assume all msat.


* Assume $\lambda \neq 0, r \neq 0$

* a, b, c, d are DC

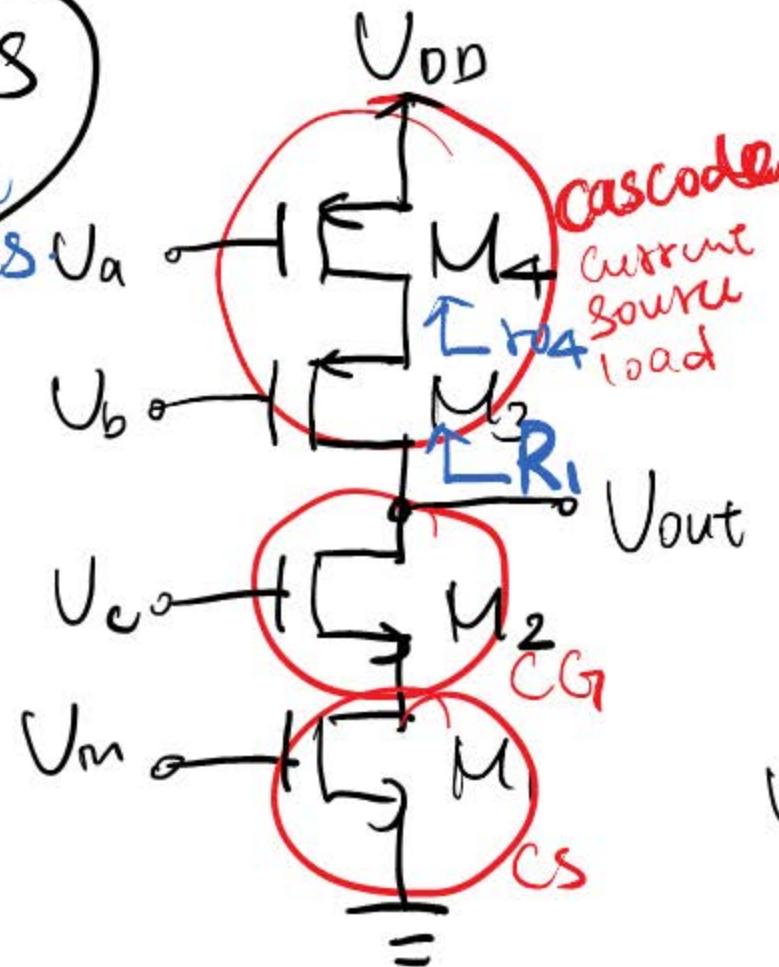



$$R_1 = R_{03} + R_{04} + \\ (g_{m3} + g_{mb3}) R_{03} R_{04}$$

Futuristic game
of M3

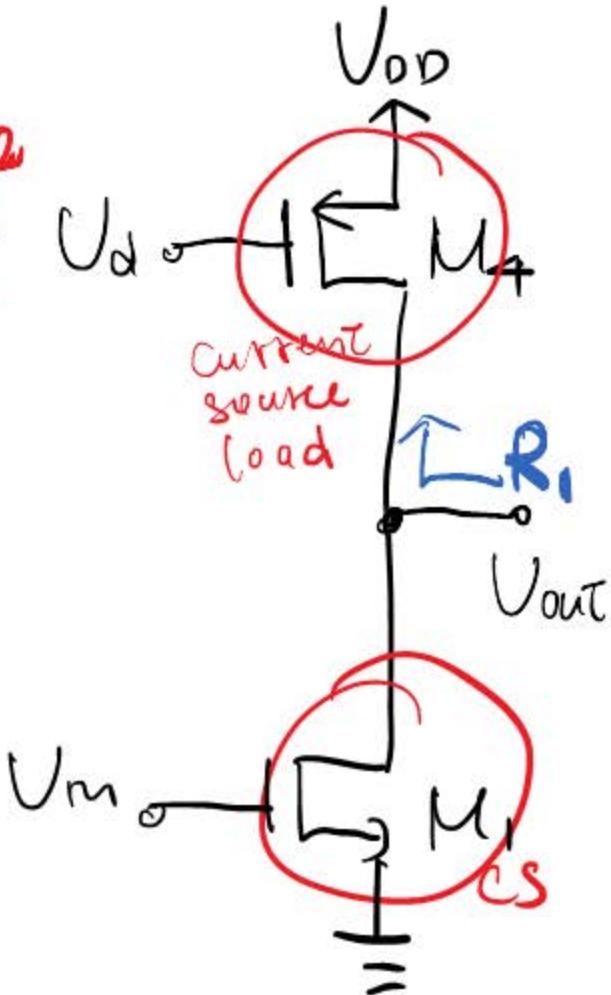

$$R_1 = 50\Omega$$

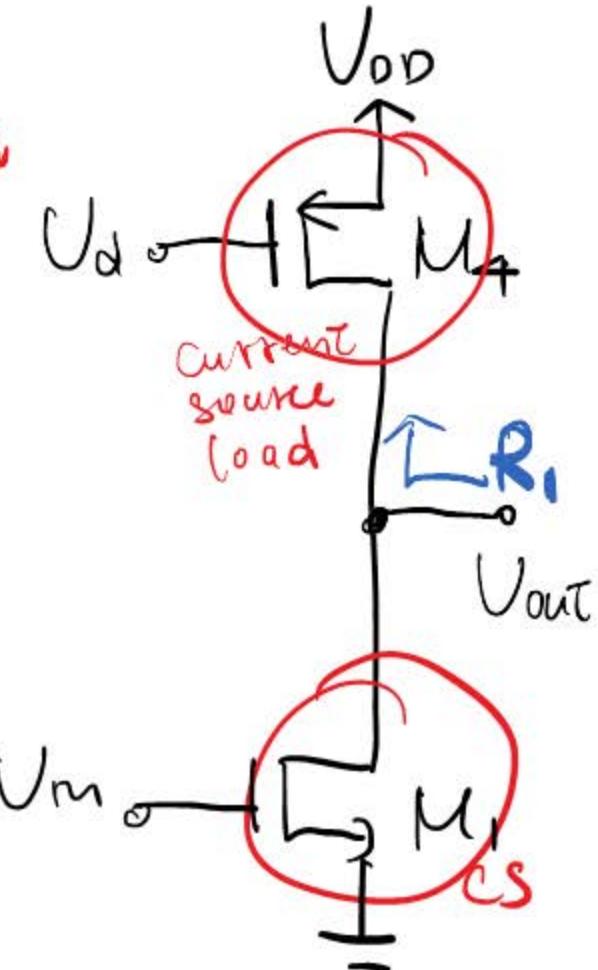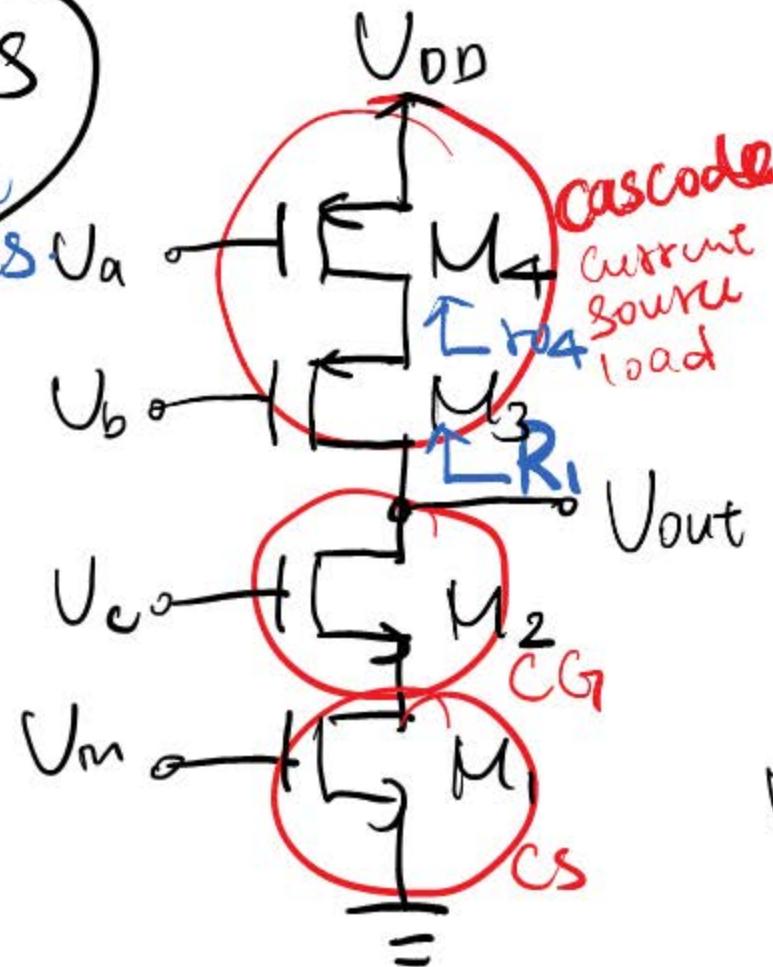Comparison
between
CBit + CS and
CS with current
source load



$$G_m = -g_{m1}$$


$$R_{out} = r_{o1} // r_{o4}$$

* Assume all msat.

* Assume $\lambda \neq 0, r \neq 0$

* V_a, b, c, d are DC

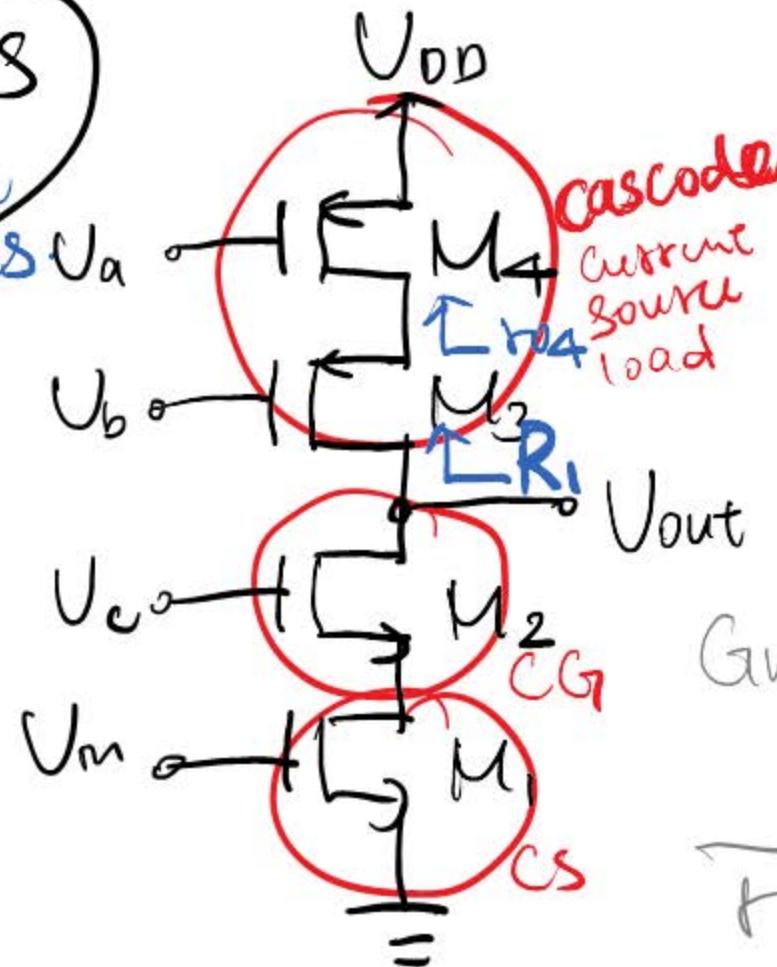Comparison
between
CBit + CS and
CS with current
source pads



$$Gm = -g_{m1} -$$

$$\frac{f_{o1}}{f_{o1} + \left(f_{o2} // \frac{1}{g_{m2} + g_{mb2}} \right)}$$

$$R_{out} = \left[r_{o3} + r_{o4} + (g_{m3} + g_{mb3})r_{o3} r_{o4} \right] //$$

$$\left[r_{o2} + r_{o1} + (g_{m2} + g_{mb2})r_{o2} r_{o1} \right]$$

* Assume all
msat.


* Assume
 $\lambda \neq 0, R \neq 0$

* V_a, b, c, d are DC

Equivalent small signal

circuit for cascode


with cascode current source.

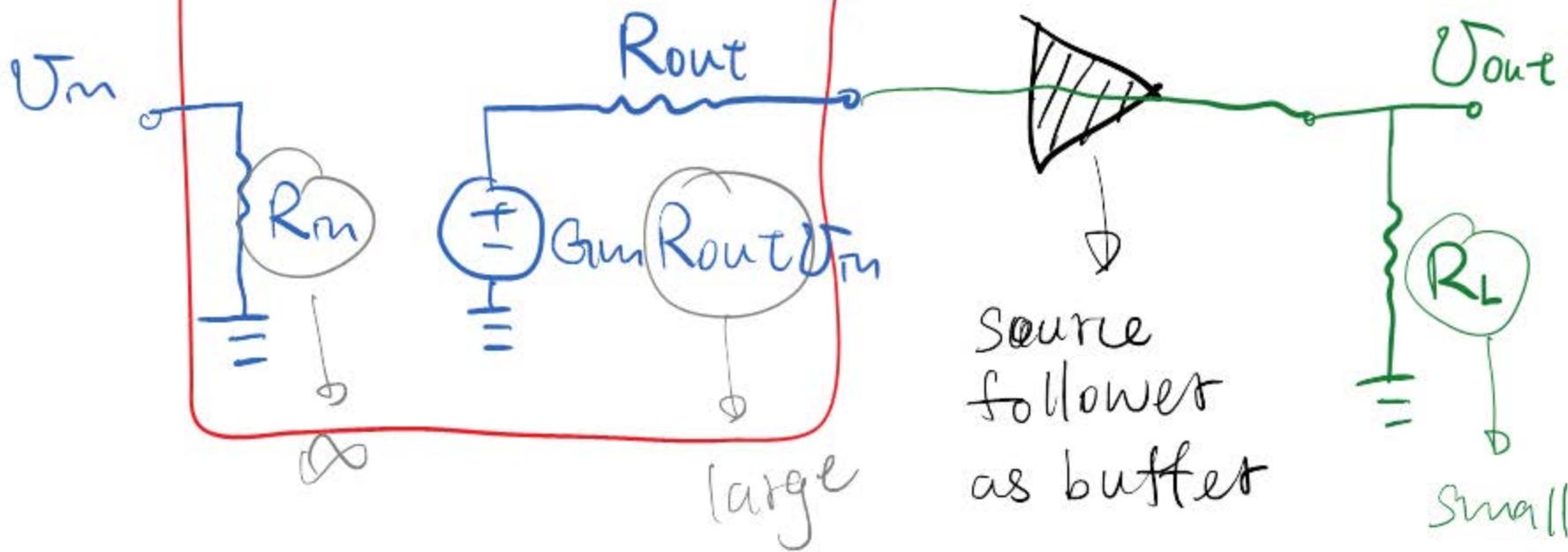


$$A_v = \frac{V_{out}}{V_m} = G_m R_{out} \frac{R_L}{R_{out} + R_L} \text{ (without buffer)}$$

Ideal Amplifier


Voltage Amp.

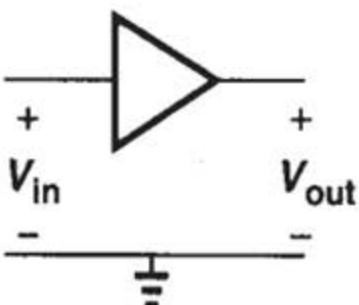






Transimpedance Amp.

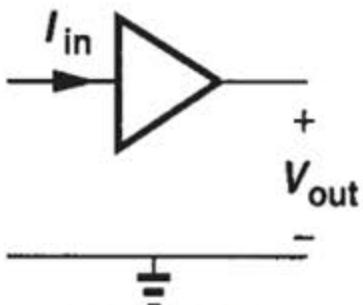

Transconductance Amp.

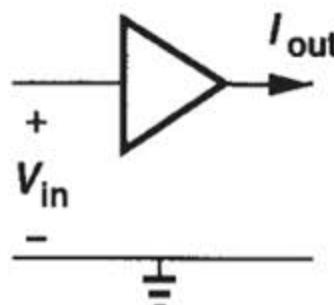



Current Amp.

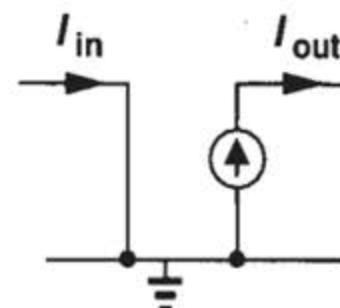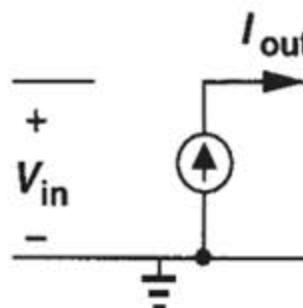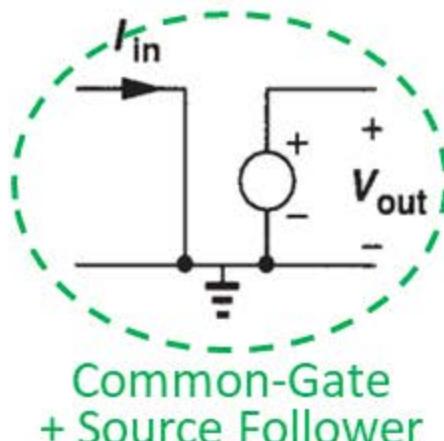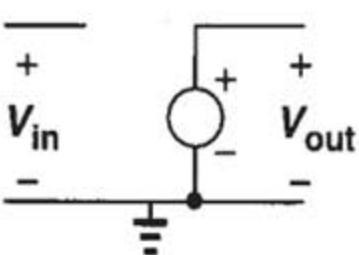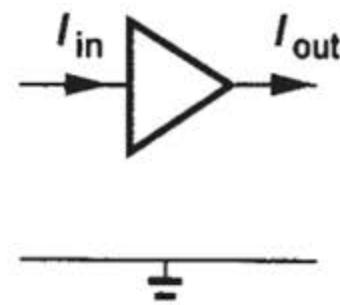

- For converting and amplifying small-signal current to voltages, common-gate provides **low input impedance** and **moderate gain**, but relatively **large output impedance**.

NOT Ideal Amplifier



Voltage Amp.

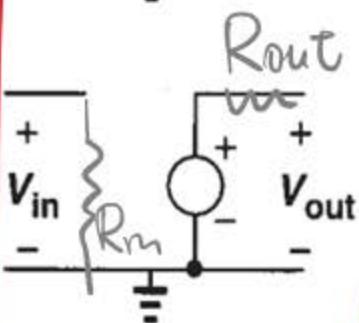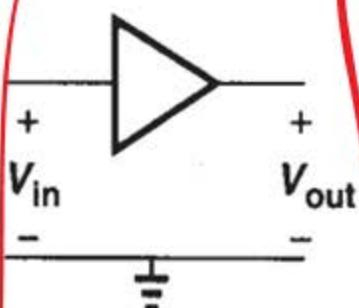

$R_m \rightarrow \infty$

$R_{out} \rightarrow 0$



Transimpedance Amp.

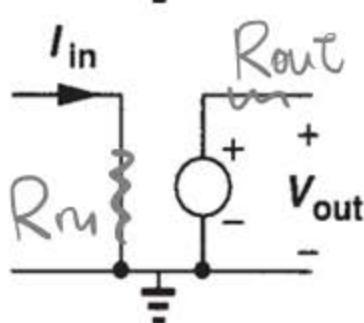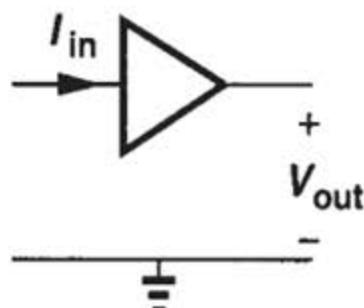

$R_m \rightarrow 0$

$R_{out} \rightarrow 0$



Transconductance Amp.

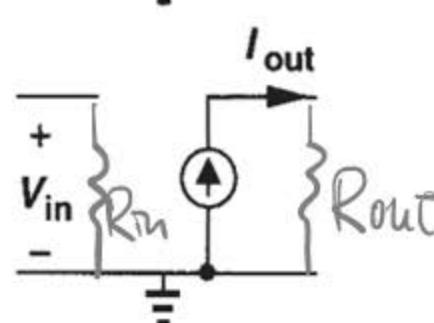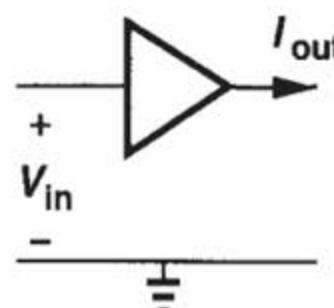

$R_m \rightarrow \infty$


$R_{out} \rightarrow \infty$

Current Amp.

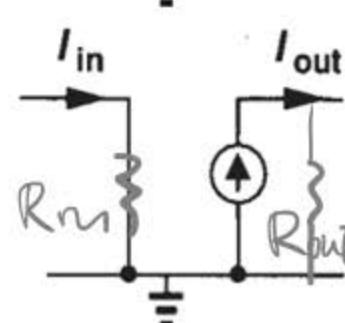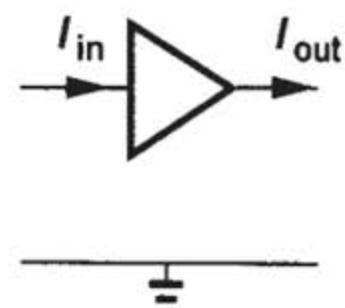


$R_m \rightarrow 0$

$R_{out} \rightarrow \infty$

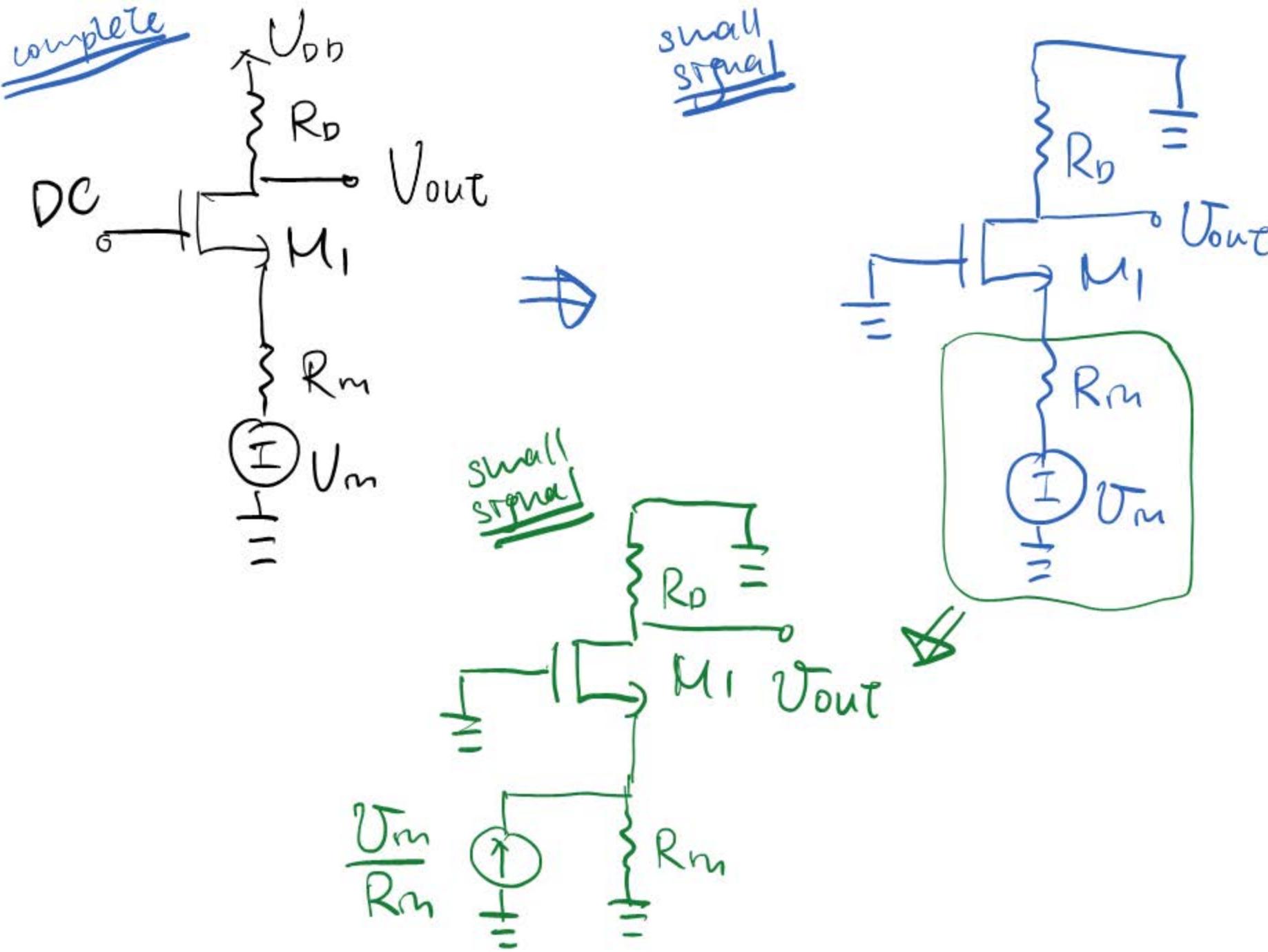

When calculating $G_m = ?$

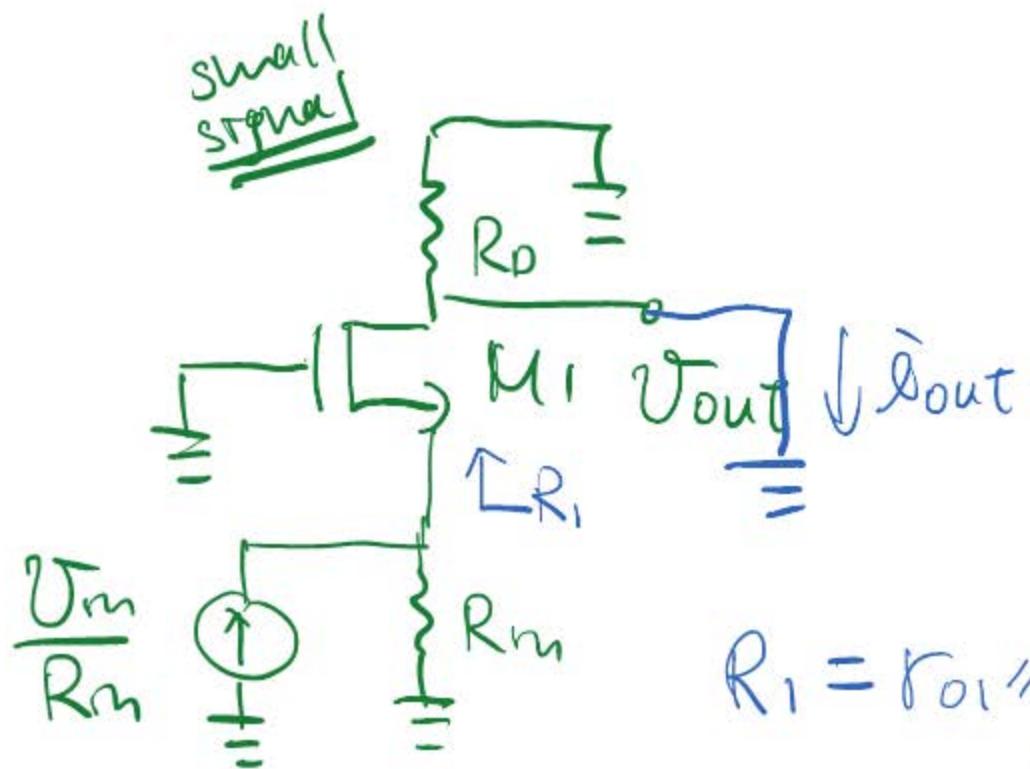
$$i_{out} = \frac{U_m}{R_m} \cdot \frac{R_m}{R_1 + R_m} = U_m \left(\frac{1}{R_1'' \frac{1}{g_m + g_{mb}} + R_m} \right)$$



$$R_1 = R_1'' \frac{1}{g_m + g_{mb}}$$

When calculating $R_{out} = ?$
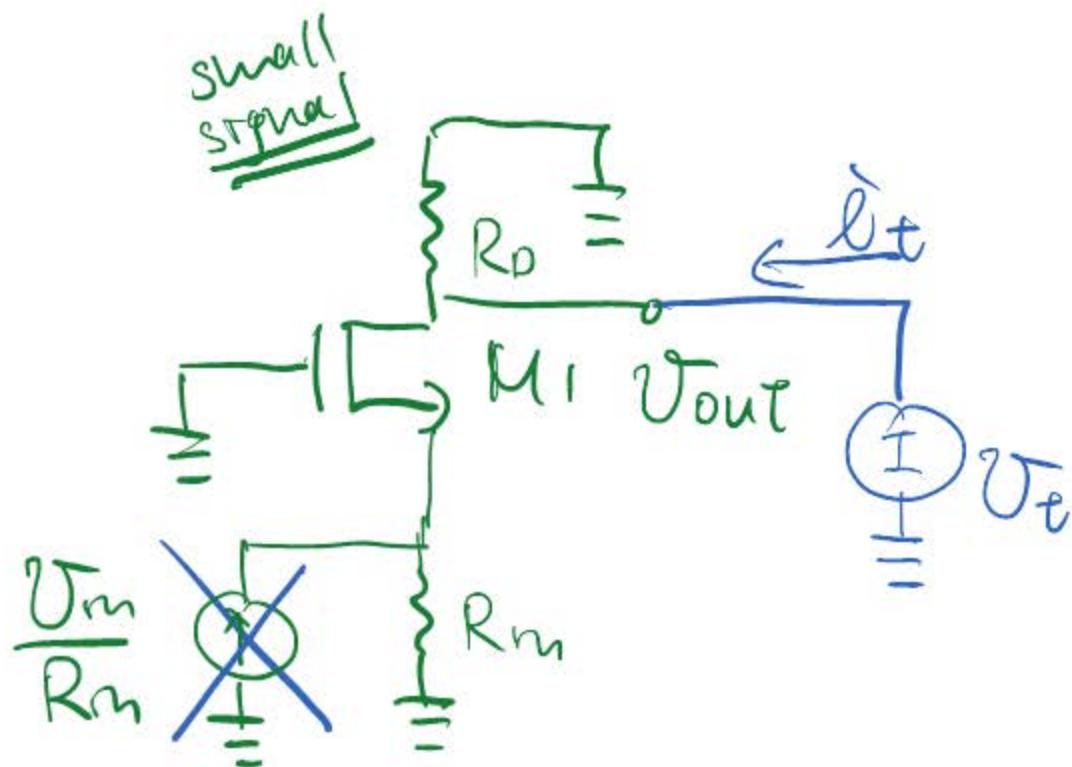
$$R_{out} = \frac{V_t}{I_t} = R_D // \left(R_{in} + (g_m + g_m b_1) R_D, R_m \right)$$





Common-Gate

DC Analysis

$$\lambda = 0 \\ \gamma \neq 0$$

$$V_{SBI} = V_{IN} \\ U_{Sb} = U_m$$

$$V_{in}$$

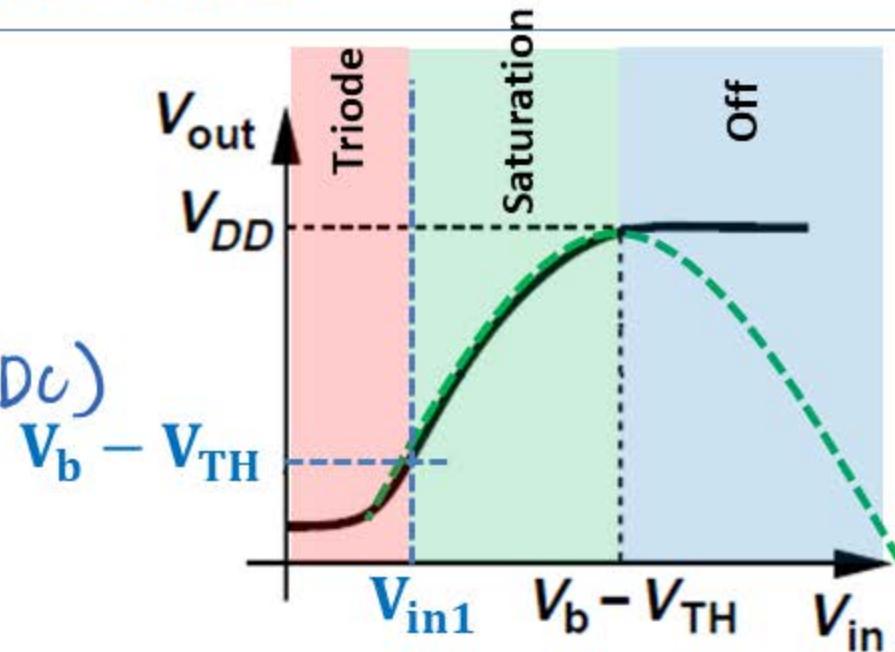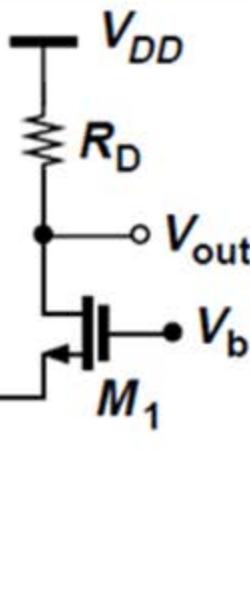

- $V_{in} > V_b - V_{TH} \rightarrow M_1 \text{ Off}$

$$V_{out} = V_{DD}$$

- $V_b - V_{TH} > V_{in} > V_{in1} \rightarrow M_1 \text{ in Saturation}$

$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2$$

- $V_{in} < V_{in1} \rightarrow M_1 \text{ in Triode}$

$$V_{out} = V_{DD} - R_D \mu_n C_{ox} \frac{W}{L} [(V_b - V_{in} - V_{TH})(V_{out} - V_{in}) - \frac{1}{2} (V_{out} - V_{in})^2]$$

$$V_{out} = V_b - V_{TH}$$

$$= V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in1} - V_{TH})^2$$

Common-Gate

DC Analysis

$\lambda = 0$

$\gamma \neq 0$

- $V_b - V_{TH} > V_{in} > V_{in1} \rightarrow M_1 \text{ in Saturation}$


$$V_{out} = V_{DD} - R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})^2$$

$$\begin{aligned} \frac{\partial V_{out}}{\partial V_{in}} &= -R_D \frac{1}{2} \mu_n C_{ox} \frac{W}{L} 2(V_b - V_{in} - V_{TH}) \left(-1 - \frac{\partial V_{TH}}{\partial V_{in}} \right) \\ &= R_D \boxed{\mu_n C_{ox} \frac{W}{L} (V_b - V_{in} - V_{TH})} \left(1 + \frac{\partial V_{TH}}{\partial V_{in}} \right) = gm \\ &\quad = \eta = \frac{\gamma}{2\sqrt{2\Phi_F + V_{SB}}} \end{aligned}$$

$$A_v = \frac{\partial V_{out}}{\partial V_{in}} = R_D gm(1 + \eta) = R_D (gm + g_{mB})$$

- gm is a function of I_D and η is a function of V_{SB} .
- A_v is not quite linear.

complete

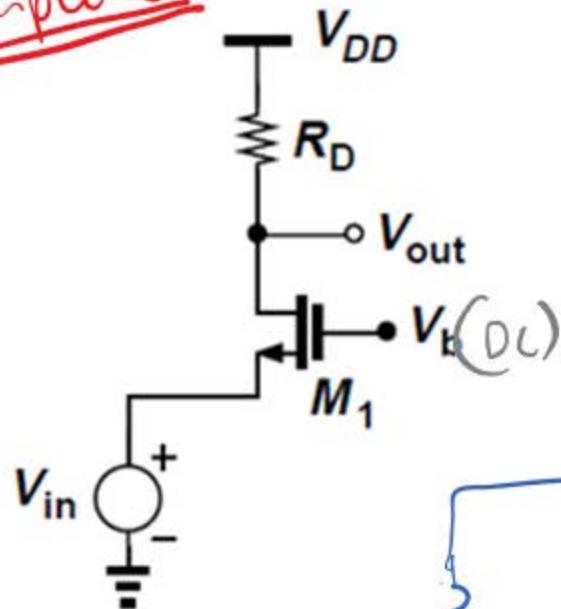

Assume $\lambda = 0, \gamma \neq 0$



Assume M_1, m sat.

$$1^\circ G_m = ?$$


$$G_m = \frac{I_{out}}{V_m}$$

$$= g_{m1} + g_{mb1}$$

small signal

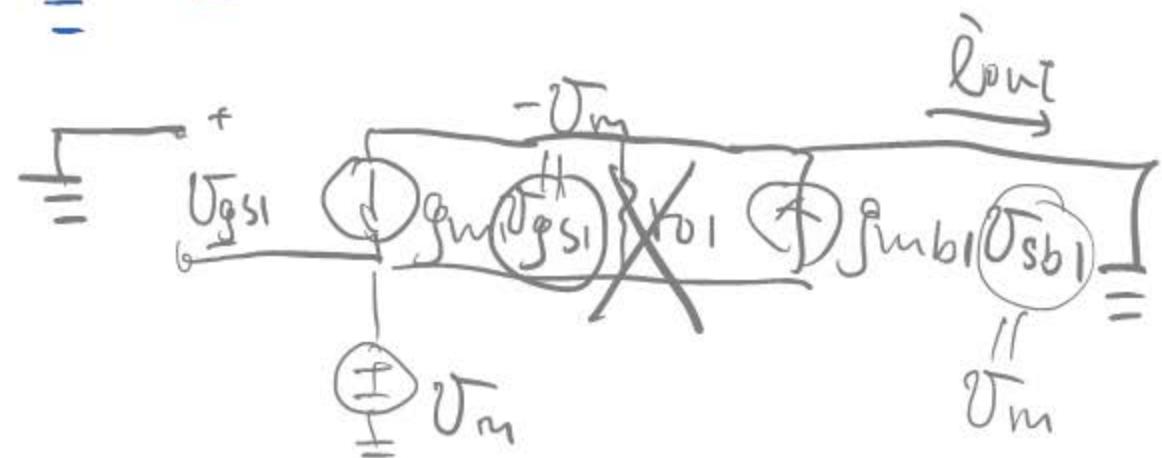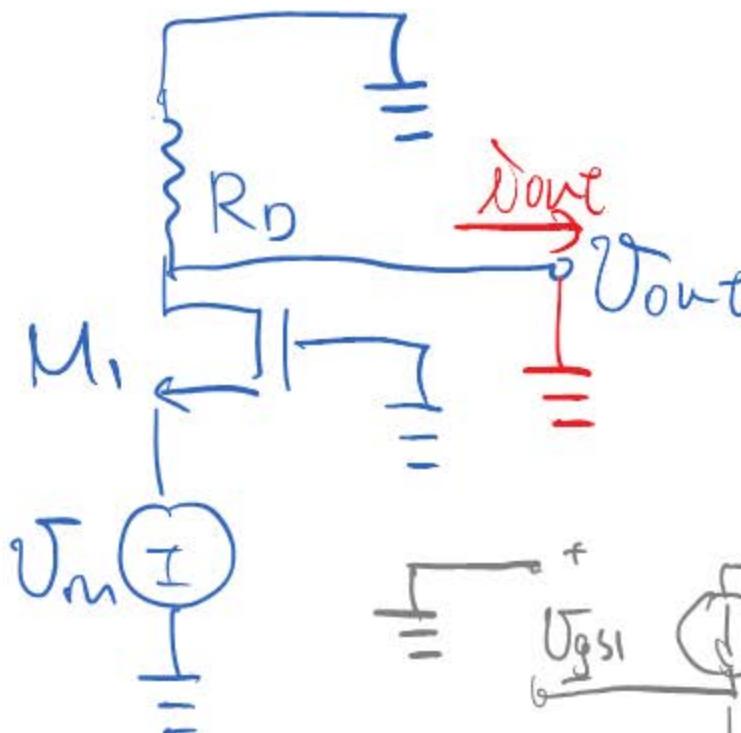

complete

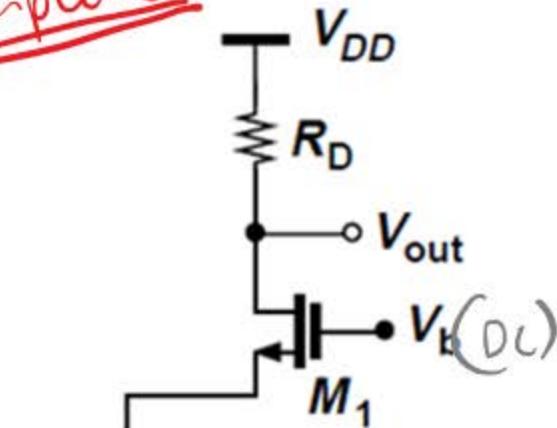


Assume $\lambda = 0$, $\gamma \neq 0$

Assume M_1 m sat.

2° $R_{out} = ?$

$$R_{out} = \frac{V_t}{I_t} = R_D$$



small signal

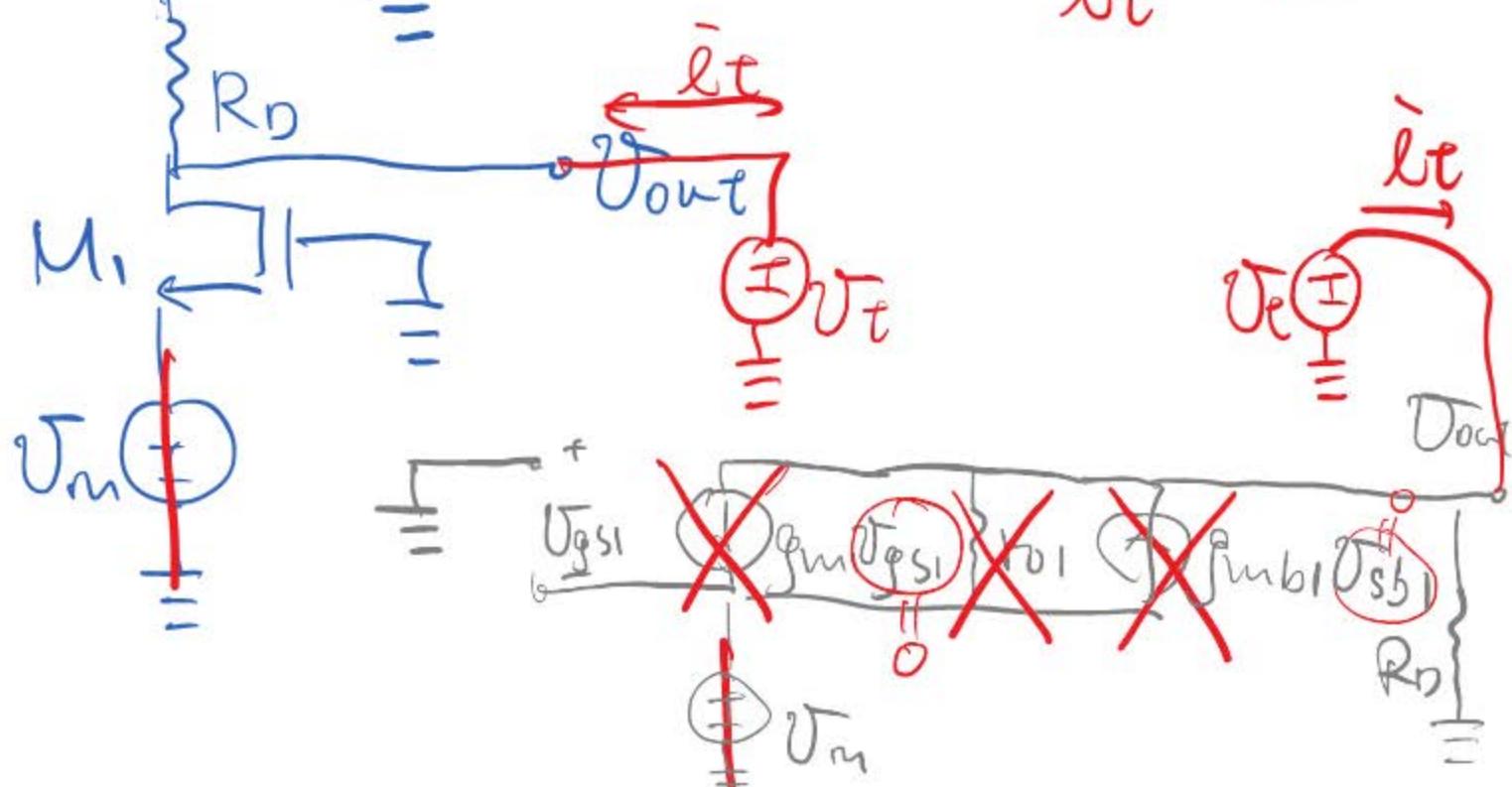

Common-Gate

Small-signal Analysis

$\lambda \neq 0$
 $\gamma \neq 0$

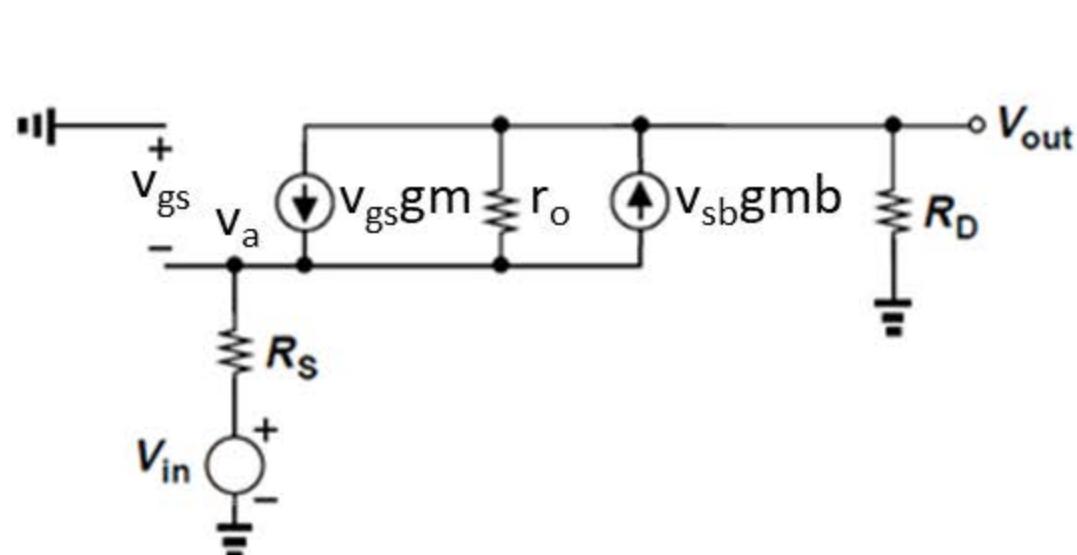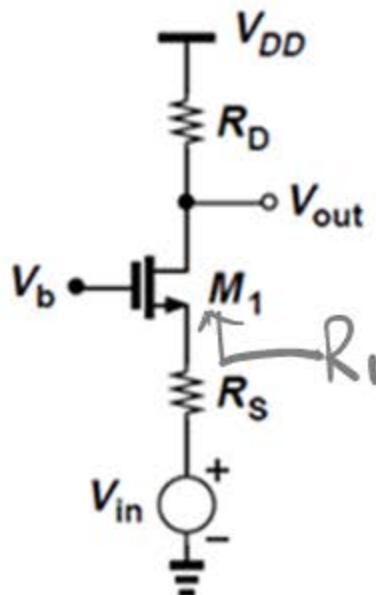

$$G_m = \frac{(gm + gmb)r_o + 1}{r_o + R_s + (gm + gmb)r_o R_s}$$

$$R_{out} = R_D \parallel [r_o + R_s + (gm + gmb)r_o R_s]$$

$$A_v = \frac{(gm + gmb)r_o + 1}{r_o + R_s + (gm + gmb)r_o R_s + R_D} R_D \approx R_D gm(1 + \eta)$$


If $R_s = 0$ and $r_o = \infty$

Common-Gate (Input Impedance)

Small-signal Analysis

$\lambda \neq 0$

$\gamma \neq 0$

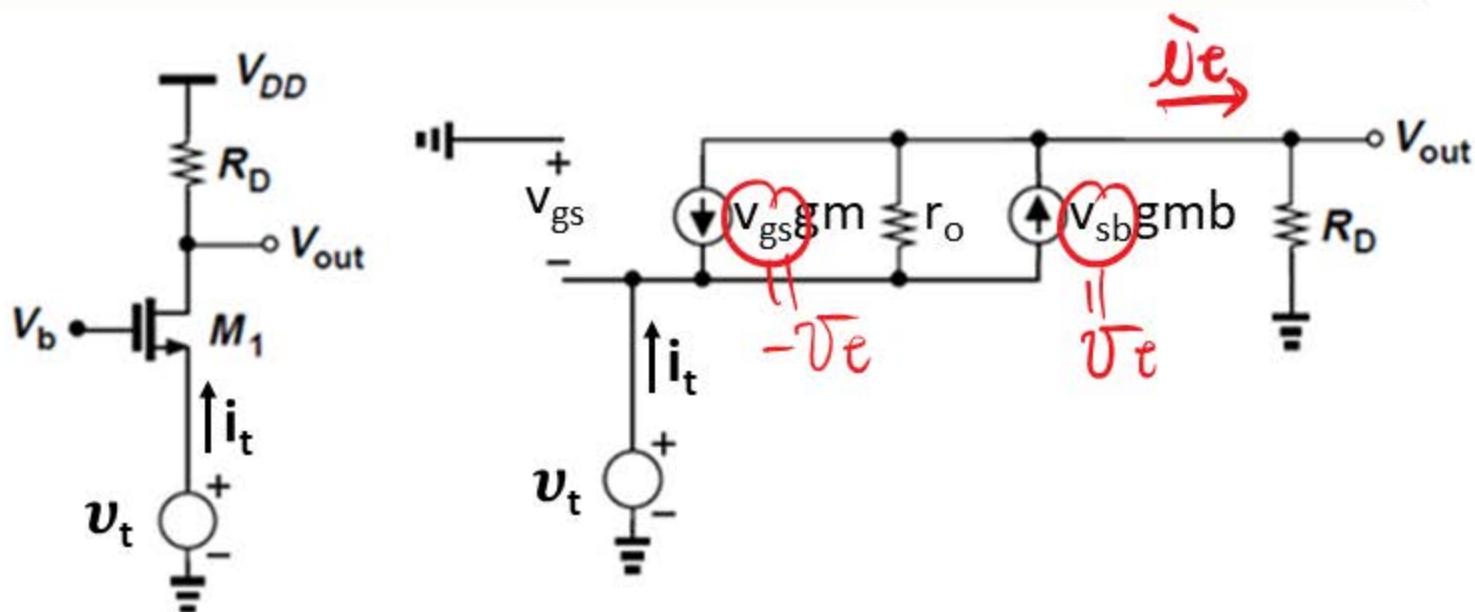


$$\begin{cases} i_t = v_t(gm + gmb) + \frac{v_t - v_{out}}{r_o} \\ v_{out} = R_D i_t \end{cases}$$


$$R_{in} = \frac{R_D + r_o}{1 + (gm + gmb)r_o}$$

If $R_D = 0$ $R_{in} = r_o \parallel \frac{1}{gm} \parallel \frac{1}{gmb}$

If $R_D = \infty$ $R_{in} = \infty$

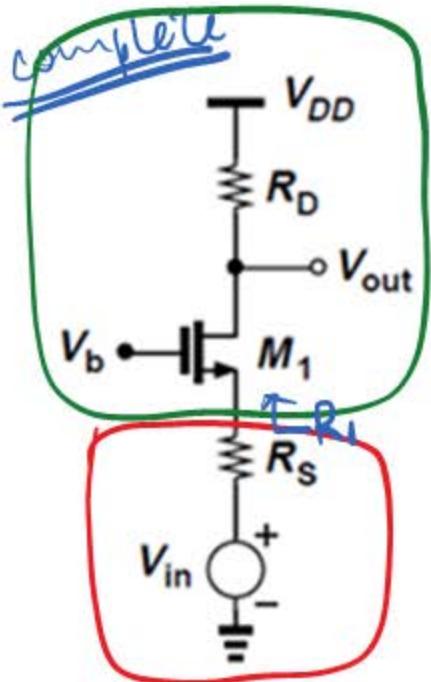

Equivalent
small-signal

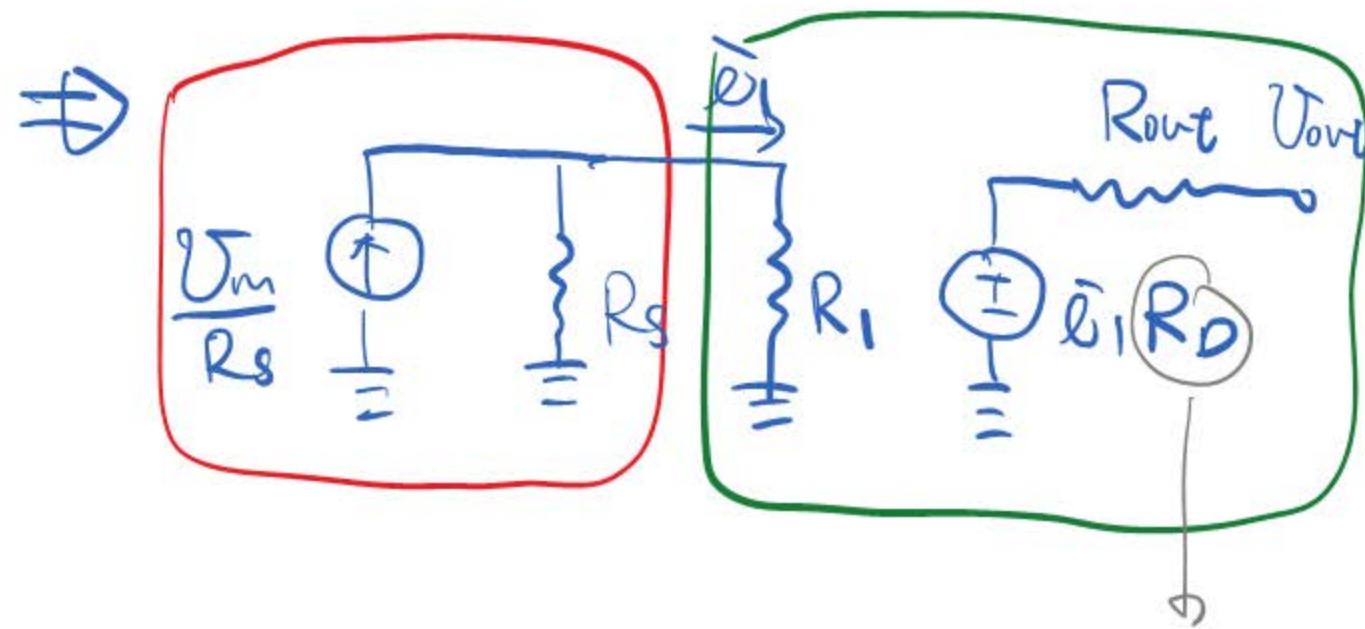

$$R_1 = \frac{R_D + r_{o1}}{1 + (g_{m1} + g_{mb})r_{o1}}$$

Trans-
impedance
gain.


$$\hat{d}_1 = \frac{R_s}{R_s + R_1}$$

Common-Gate (Output Impedance)

Small-signal Analysis

$\lambda \neq 0$

$\gamma \neq 0$

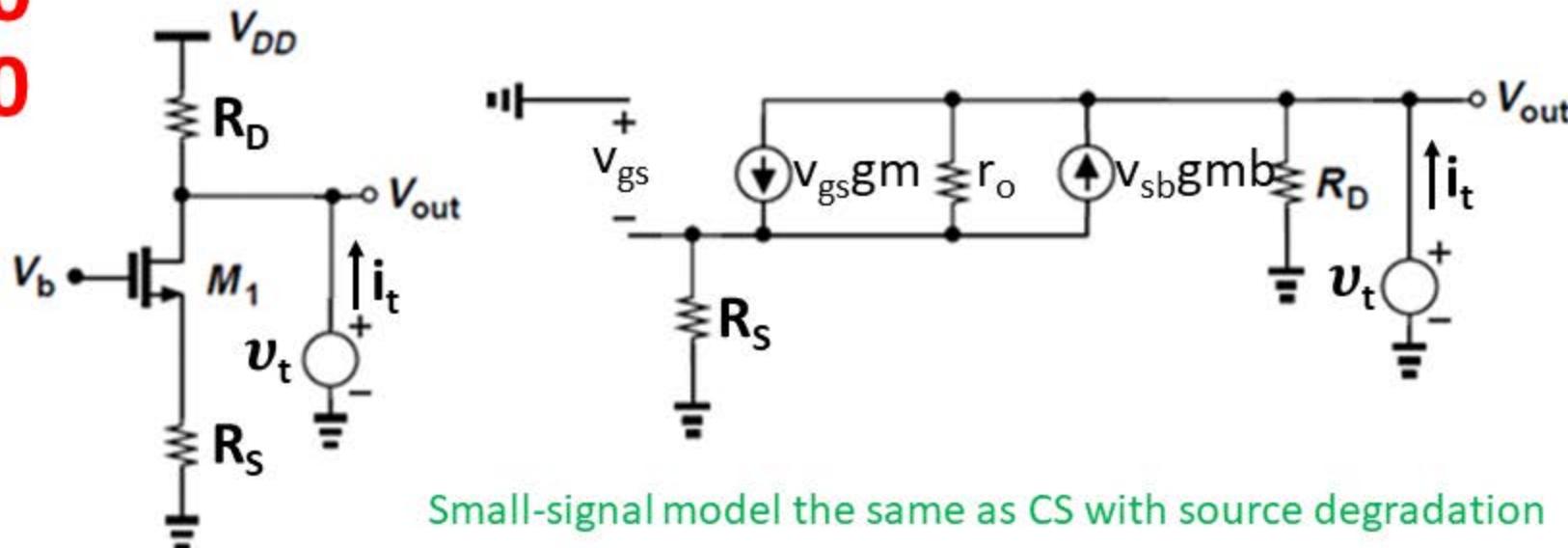


Small-signal model the same as CS with source degradation

$$R_{out} = [R_S + r_{o1} + (gm_1 + gmb_1)r_{o1}R_S] \parallel R_D$$



Example

Calculate the small-signal voltage gain at low frequencies of the circuits below. To minimize wave reflection at point X, the input impedance must be equal to 50Ω .

Assume $\lambda = 0$

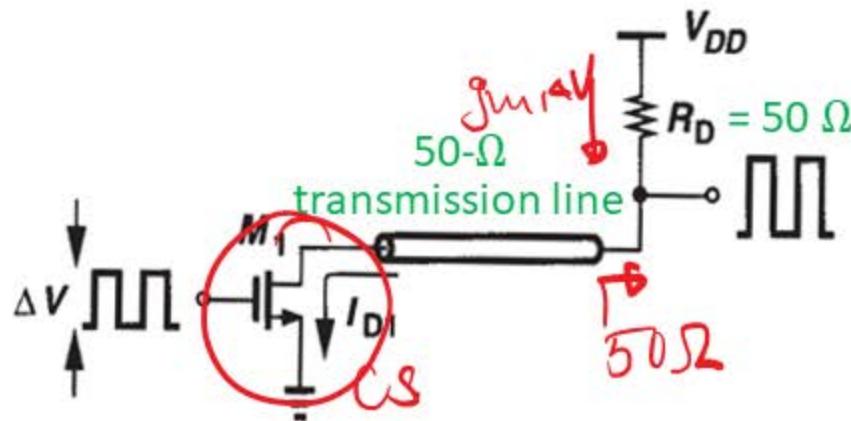

$$A_v = -g_{m1} R_D \\ = 50 \Omega$$

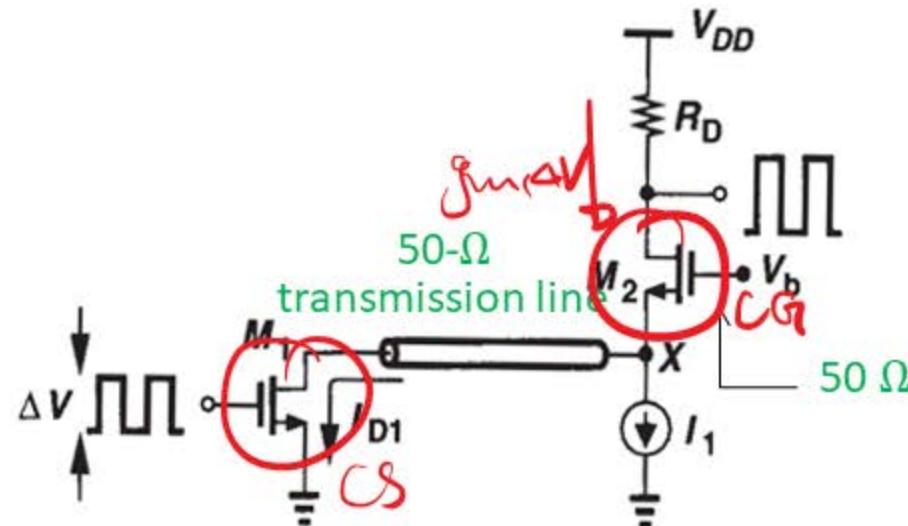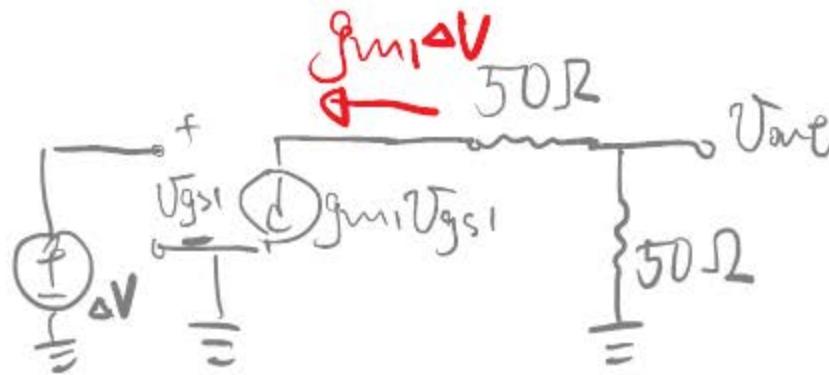


$$A_v = -g_{m1} R_D$$

can be much larger than 50Ω , so as to achieve a much higher gain.

$$R_{in} = \frac{R_D + r_{o2}}{1 + (g_{m2} + g_{mb2})r_{o2}} = 50 \Omega$$



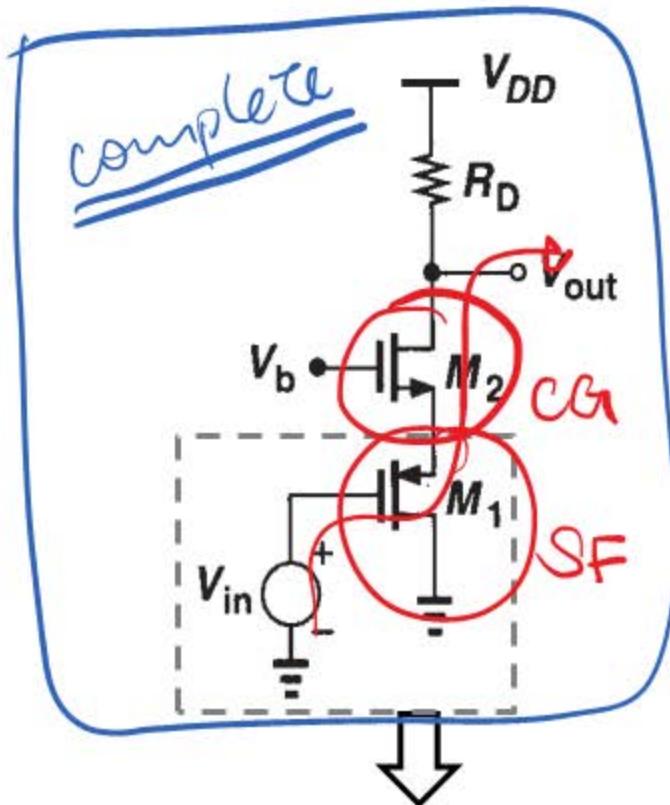
Example

Calculate the small-signal voltage gain of the circuit below. ($\lambda \neq 0, \gamma \neq 0$)



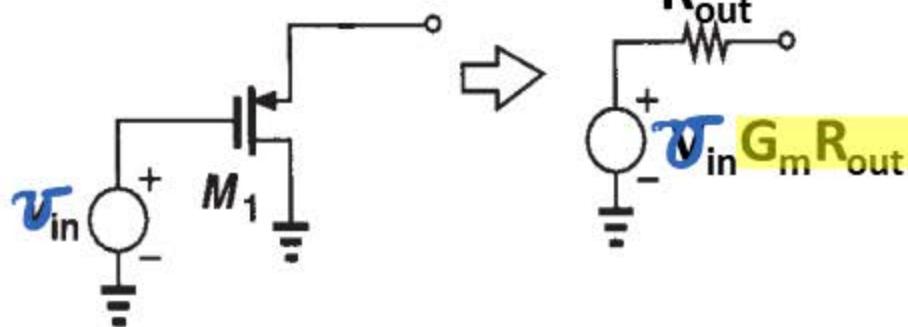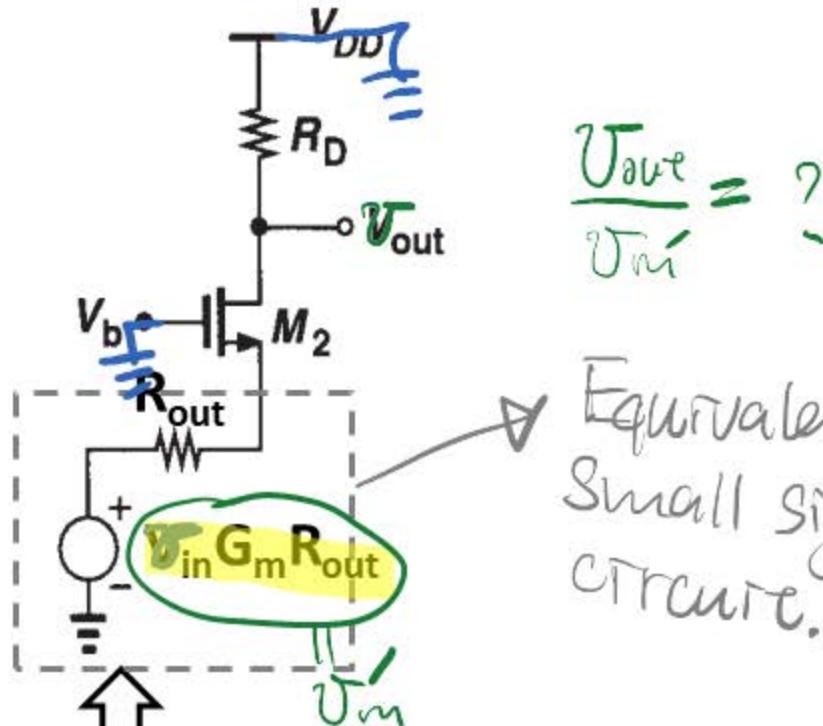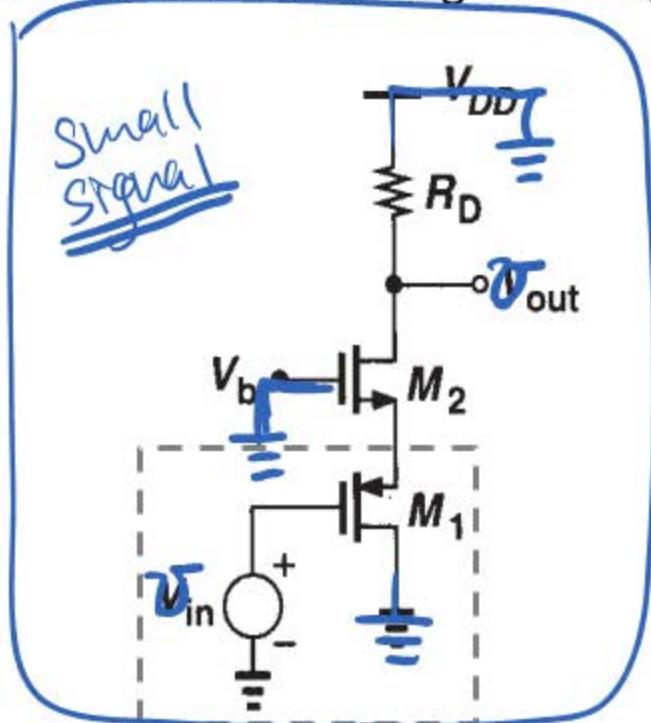Example

Calculate the small-signal voltage gain of the circuit below. ($\lambda \neq 0, \gamma \neq 0$)



$$\left\{ \begin{array}{l} G_m = g_{m1} \\ R_{out} = r_{o1} \parallel \frac{1}{g_{m1}} \parallel \frac{1}{g_{mb1}} \end{array} \right.$$


$$\frac{V_{out}}{V_m} = \frac{(gm_2 + gmb_2)r_{o2} + 1}{r_{o2} + R_{out} + (gm_2 + gmb_2)r_{o2}R_{out} + R_D} R_D$$

$$V_m \left[gm_1 \left(r_{o1} // \frac{1}{gm_1 + gmb_1} \right) \right]$$


$$r_{o1} // \frac{1}{gm_1 + gmb_1}$$

$$A_{vJ} = \frac{V_{out}}{V_m} = \left[gm_1 \left(r_{o1} // \frac{1}{gm_1 + gmb_1} \right) \right] R_D$$

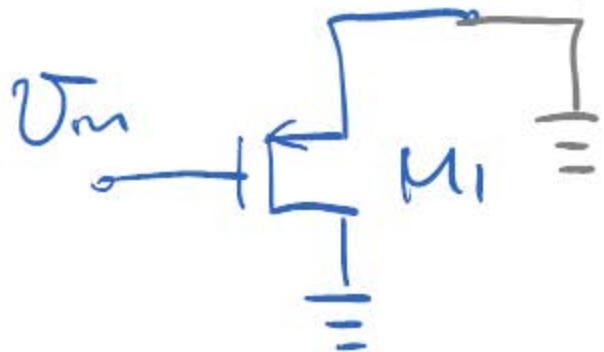
$$\overline{i_{out}} \quad 1^{\circ} G_m = ?$$



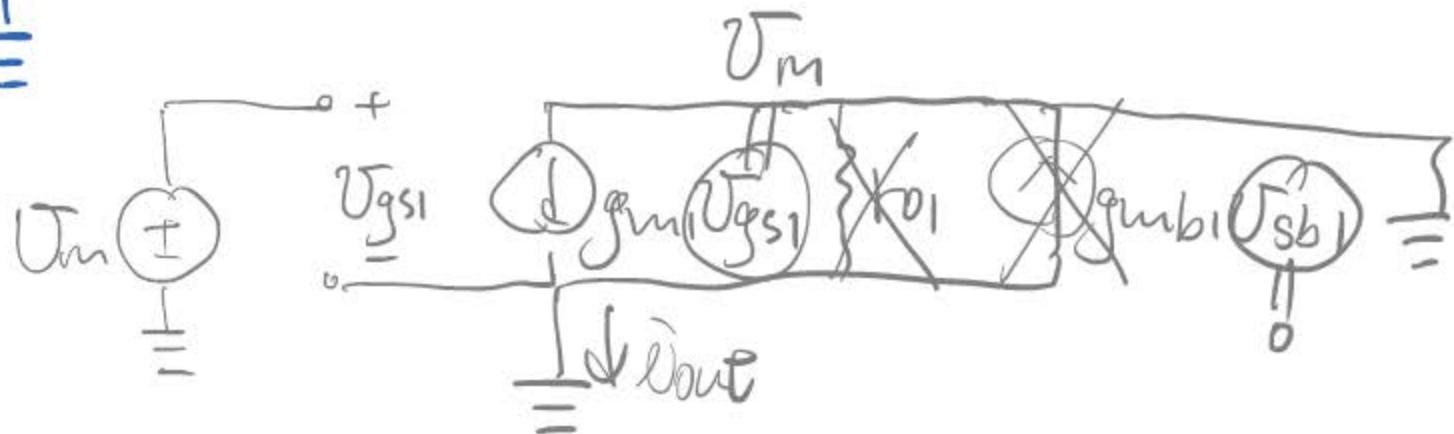
$$G_m = \overline{i_{out}} / \overline{V_m} = g_m,$$



2^o $R_{out} = ?$

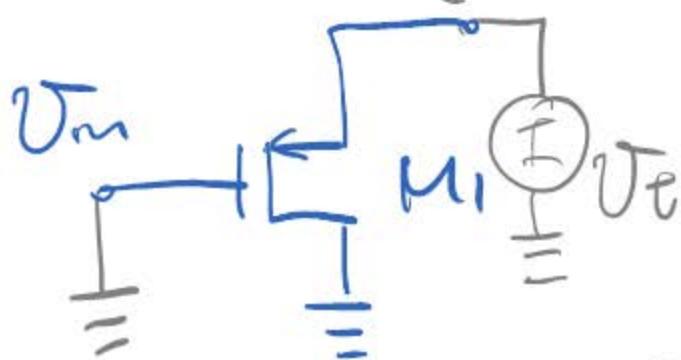
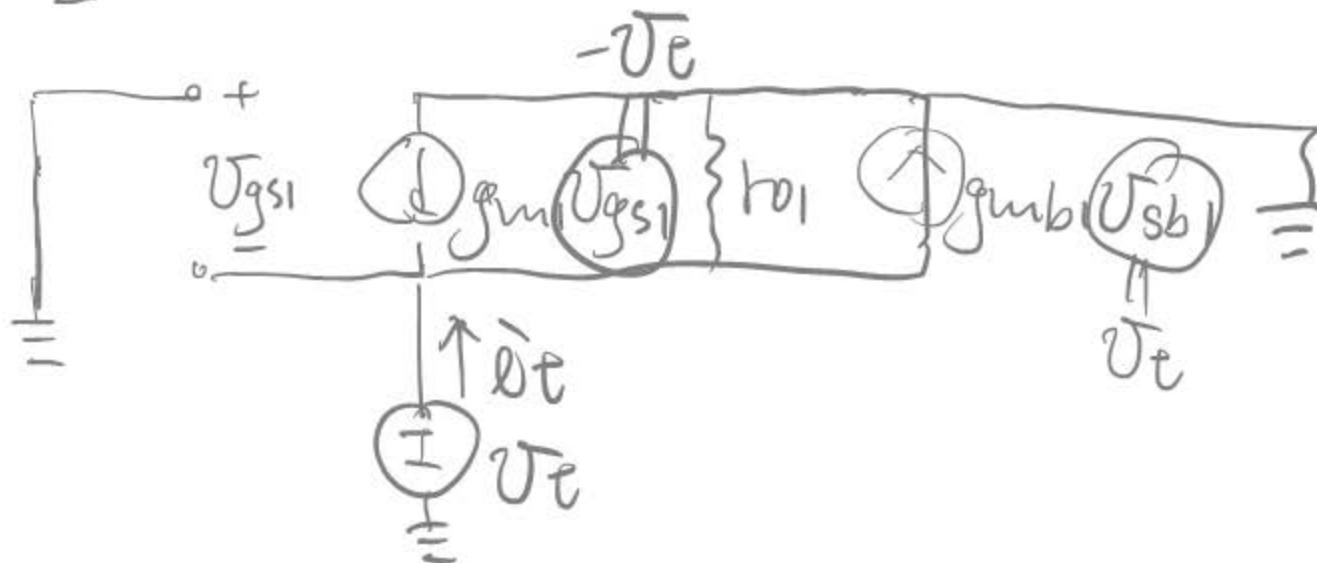
$$R_{out} = \frac{V_t}{I_e} = h_{o1} \parallel \frac{1}{g_{m1} + g_{mb1}}$$




$$3^o A_V = G_m R_{out} = g_{m1} \left(h_{o1} \parallel \frac{1}{g_{m1} + g_{mb1}} \right)$$

SF

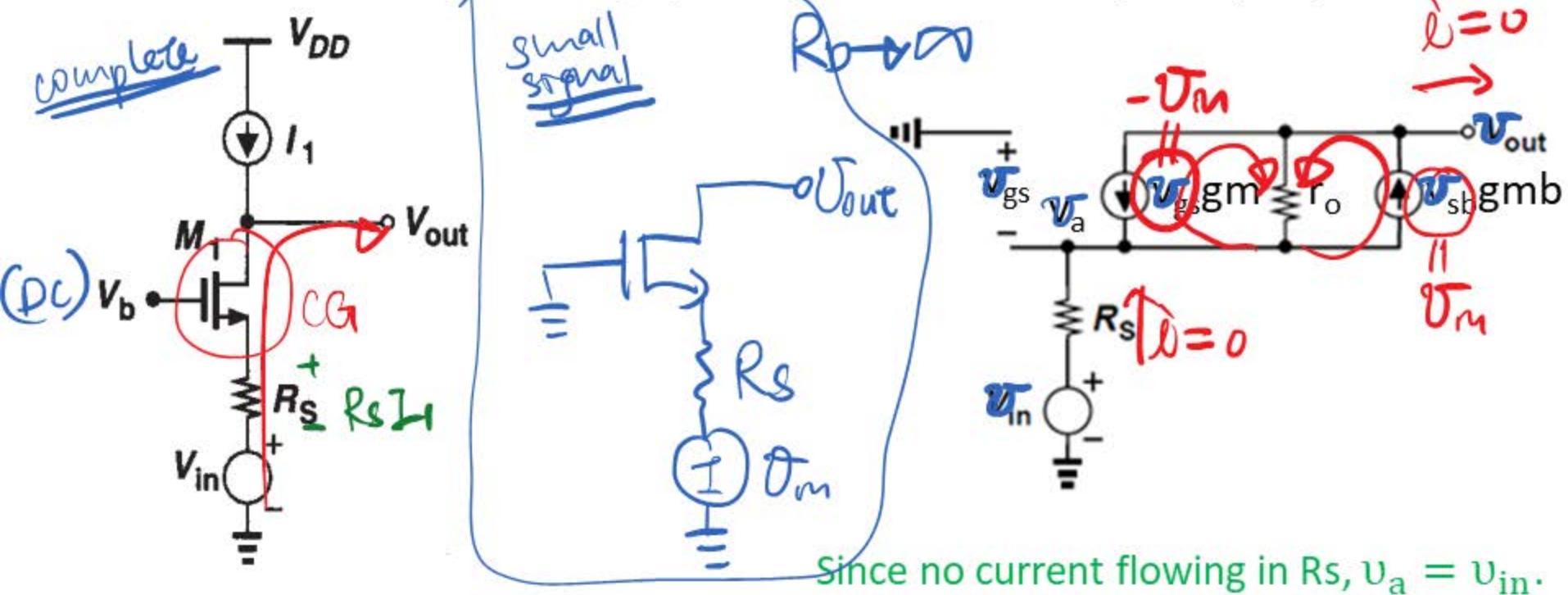Example

Calculate the small-signal voltage gain of the circuit below. ($\lambda \neq 0, \gamma \neq 0$)





$$v_{out} - v_{in}(gm + gmb)r_o = v_{in}$$

$$A_v = \frac{v_{out}}{v_{in}} = 1 + (gm + gmb)r_o$$

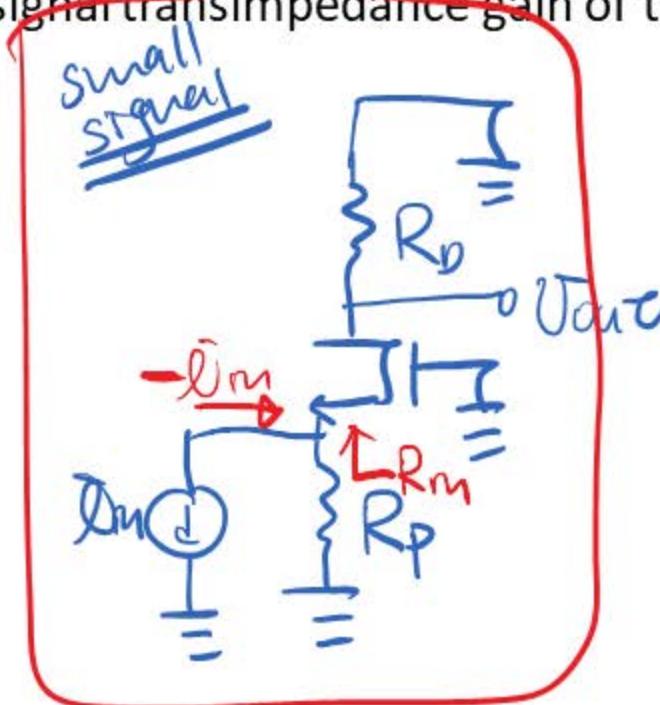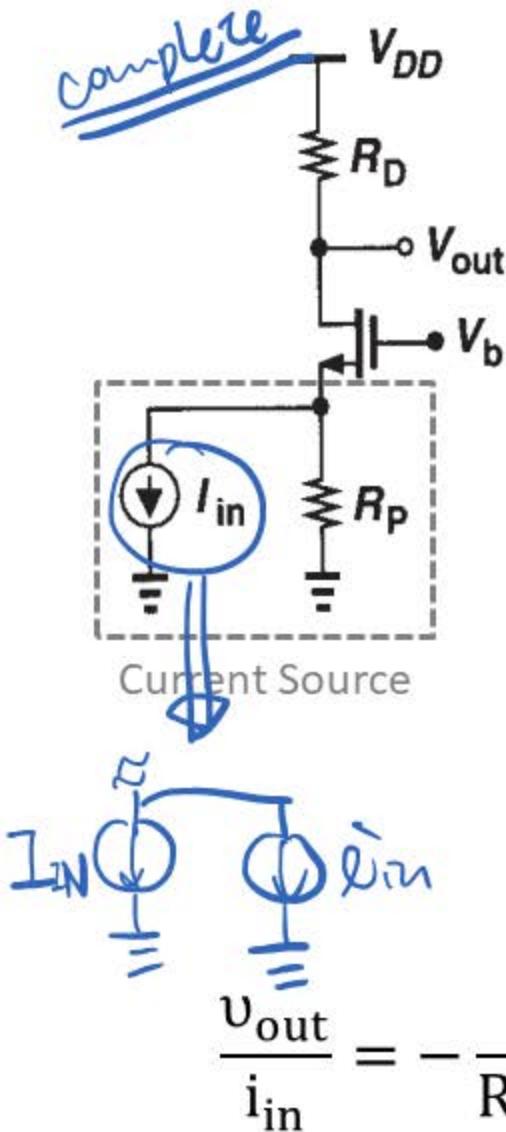Example



Calculate the small-signal transimpedance gain of the circuit below. ($\lambda \neq 0, \gamma \neq 0$)



$$R_{in} = \frac{R_D + r_o}{1 + (gm + gmb)r_o}$$

$$\left(-i_{in} \frac{R_P}{R_{in} + R_P} \right) R_D = v_{out}$$
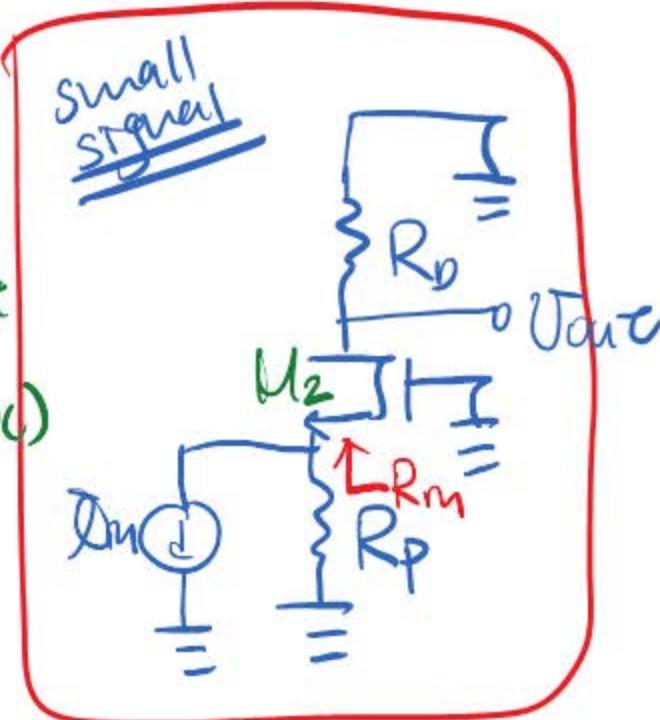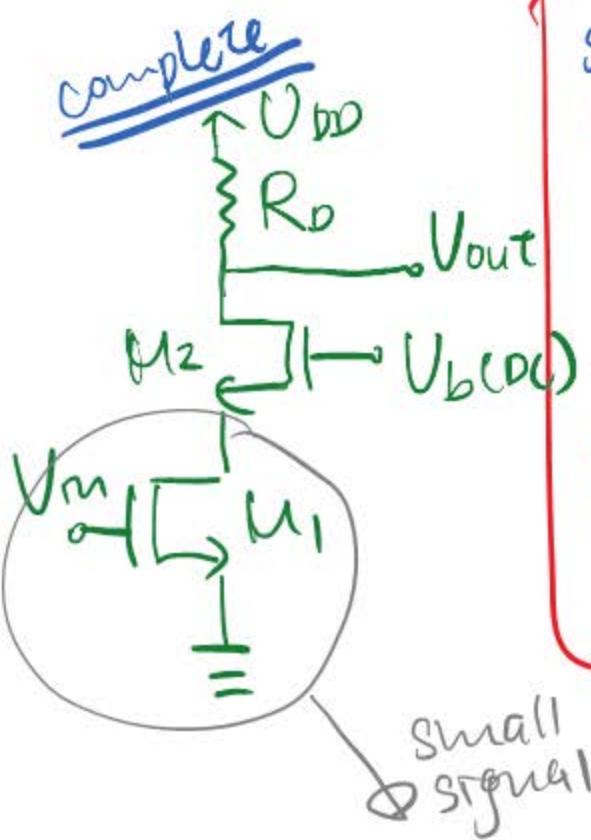
$$\frac{v_{out}}{i_{in}} = -\frac{R_P}{R_{in} + R_P} R_D = \frac{-R_P R_D [1 + (gm + gmb)r_o]}{R_D + r_o + R_P + (gm + gmb)r_o R_P} \quad (\Omega)$$




$$\delta V_m = f_m, U_m$$

$$R_P = r_o,$$



Cascode


Ideal Amplifier

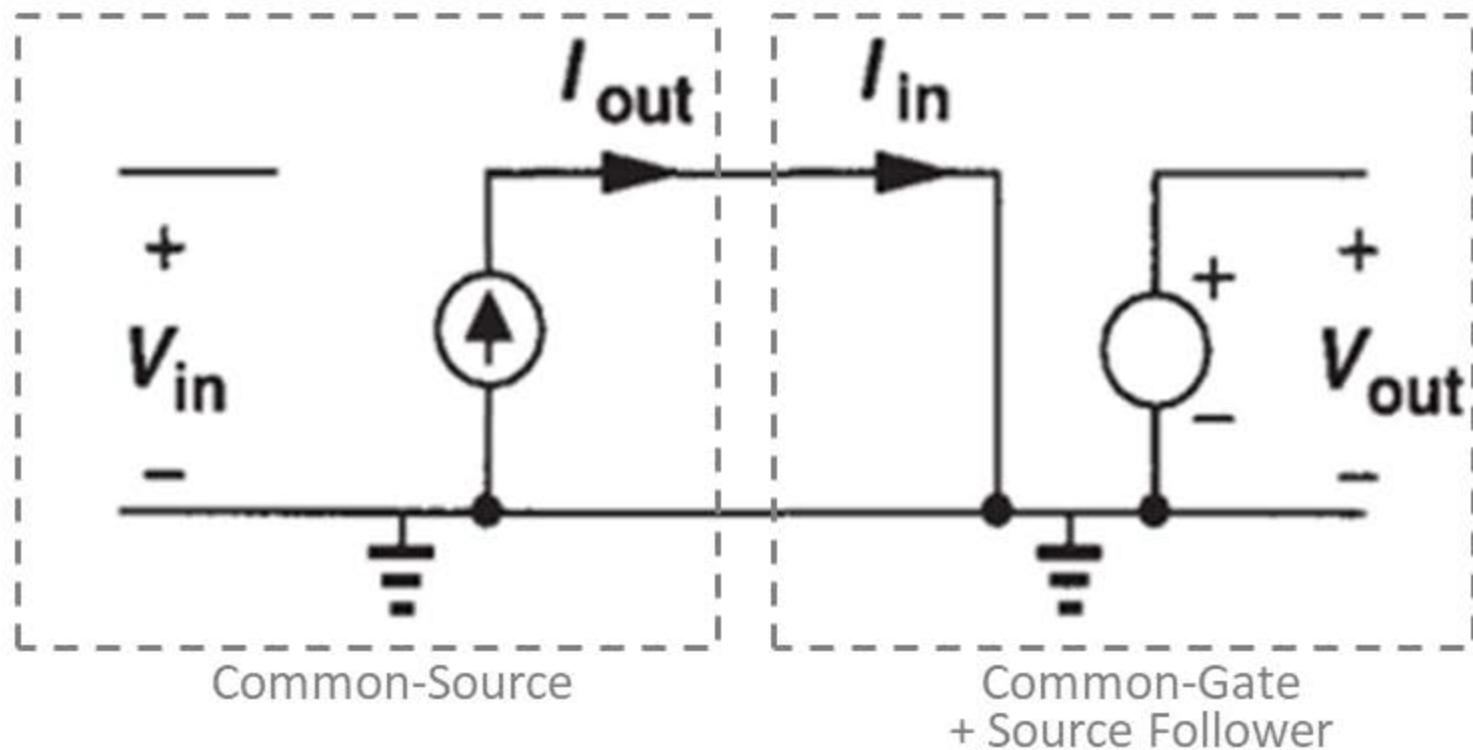

CS + CG with Resistive Load

Small-signal Analysis

$\lambda \neq 0 \quad \gamma \neq 0$

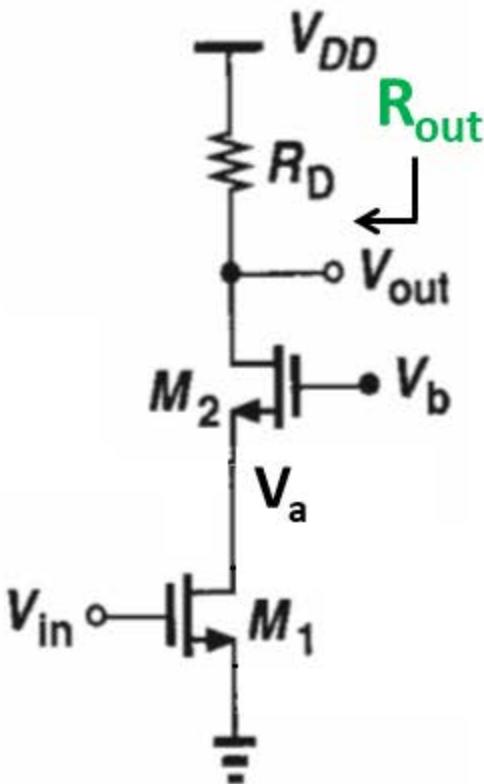

$$\left\{ \begin{array}{l} G_m = -gm_1 \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{gm_2 + gmb_2} \right)} \\ R_{out} = [r_{o1} + r_{o2} + (gm_2 + gmb_2)r_{o2}r_{o1}] \parallel R_D \end{array} \right.$$

$$A_v = G_m R_{out}$$

$$V_a \geq V_{in} - V_{TH1}$$

$$V_b - V_{GS2} \geq V_{in} - V_{TH1}$$

$$V_b \geq V_{in} - V_{TH1} + V_{GS2}$$


$$V_{out} \geq V_b - V_{TH2} \geq (V_{in} - V_{TH1}) + (V_{GS2} - V_{TH2})$$

$$V_{DD} \geq V_{out} \geq V_{ov1} + V_{ov2}$$

CS + CG with Ideal Current Source Load

Small-signal
Analysis

$$\lambda \neq 0 \quad \gamma \neq 0$$

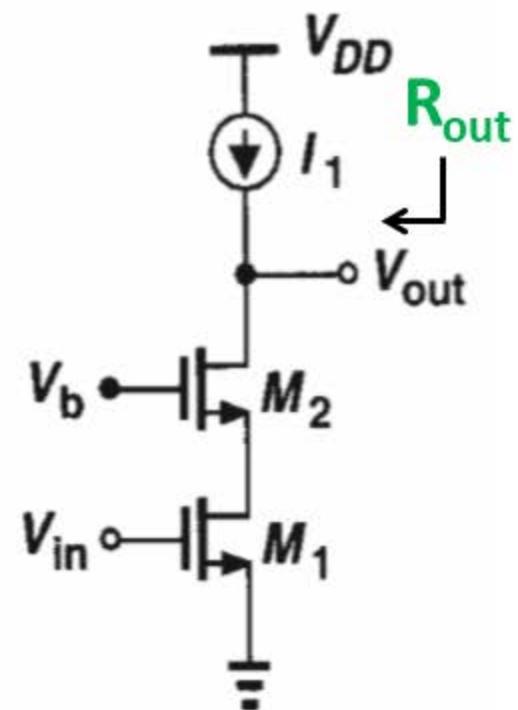

$$\left\{ \begin{array}{l} G_m = -g_{m1} \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{g_{m2} + g_{mb2}} \right)} \\ R_{out} = r_{o1} + r_{o2} + (g_{m2} + g_{mb2})r_{o2}r_{o1} \end{array} \right.$$


$$A_v = G_m R_{out}$$

CS + CG with Cascode Current Source Load

Small-signal Analysis

Assume $\lambda \neq 0 \ \gamma \neq 0$

Assume all m sat.

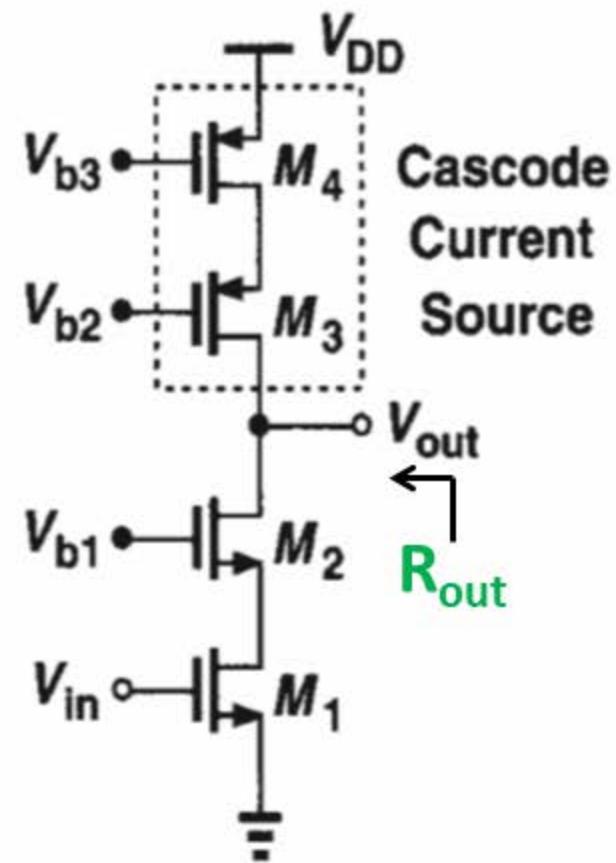

$$\left\{ \begin{array}{l} G_m = -gm_1 \frac{r_{o1}}{r_{o1} + \left(r_{o2} \parallel \frac{1}{gm_2 + gmb_2} \right)} \\ R_{out} = [r_{o1} + r_{o2} + (gm_2 + gmb_2)r_{o2}r_{o1}] \\ \parallel [r_{o3} + r_{o4} + (gm_3 + gmb_3)r_{o3}r_{o4}] \end{array} \right.$$

$$A_v = G_m R_{out}$$


$$V_{DD} - V_{ov3} - V_{ov4} \geq V_{out} \geq V_{ov1} + V_{ov2}$$

Vout headroom

Folded Cascode


Small-signal
Analysis

$\lambda \neq 0$ $\gamma \neq 0$

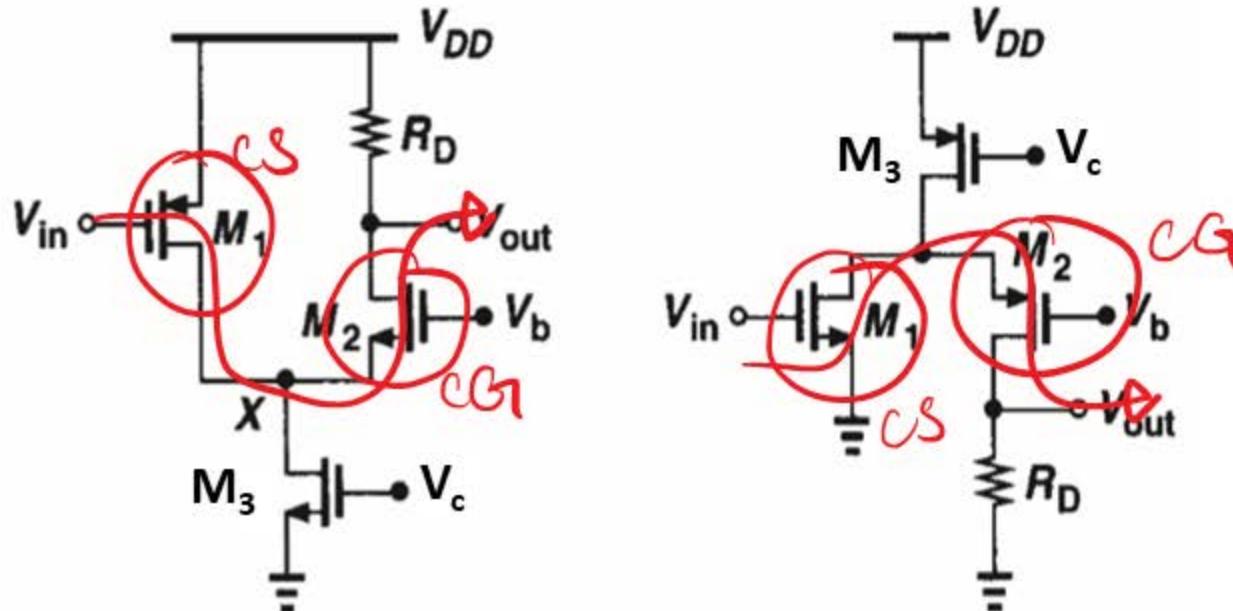



$$\left\{ \begin{array}{l} G_m = -gm_1 \frac{(r_{o1} \parallel r_{o3})}{(r_{o1} \parallel r_{o3}) + \left(r_{o2} \parallel \frac{1}{gm_2 + gmb_2} \right)} \\ R_{out} = [(r_{o1} \parallel r_{o3}) + r_{o2} + (gm_2 + gmb_2)r_{o2}(r_{o1} \parallel r_{o3})] \parallel R_D \end{array} \right.$$

$$A_v = G_m R_{out}$$

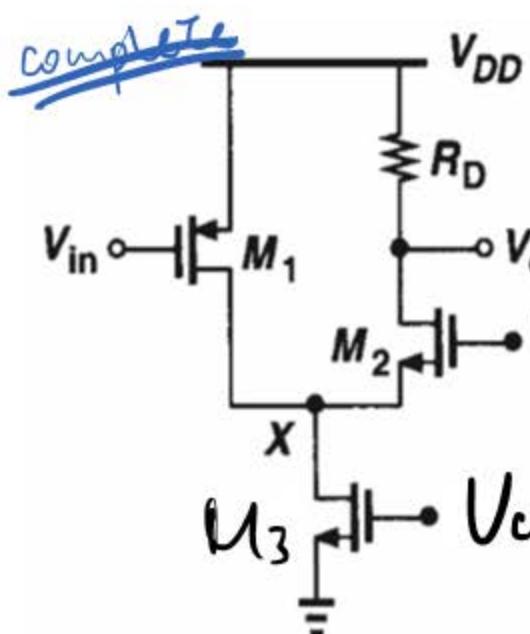


$$\lambda \neq 0, \delta \neq 0$$

small signal

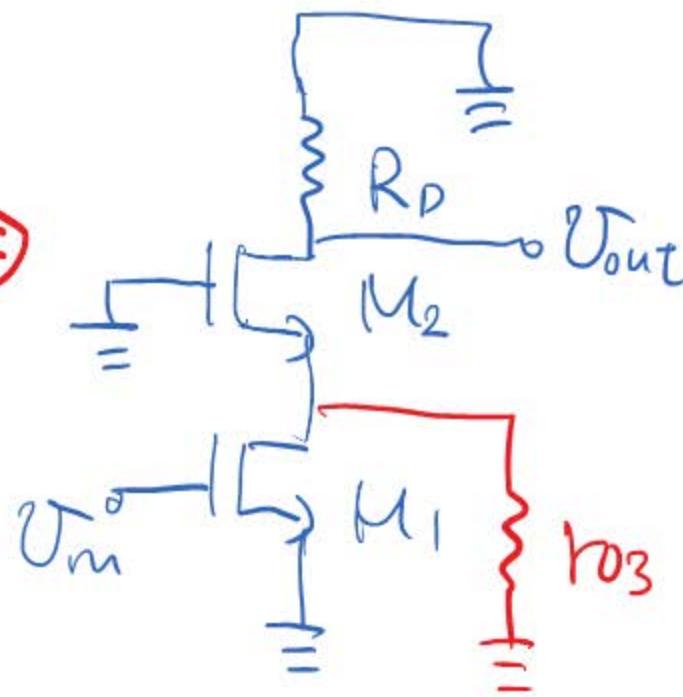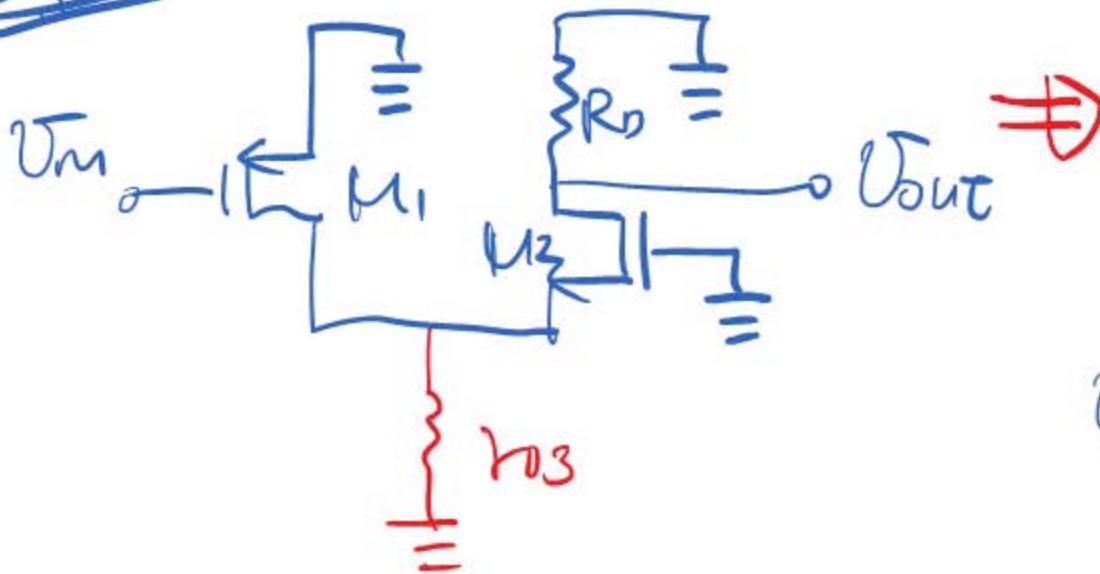

~~complete~~

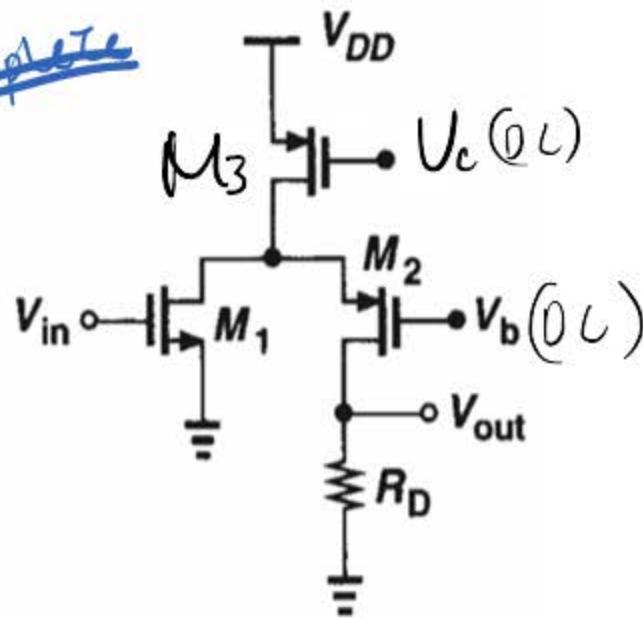

$$\lambda \neq 0, \delta \neq 0$$

~~small signal~~

