

1. (a). NMOS

(1). When $V_{DD} > V_x$,we have $V_D = 5V$, $V_S = V_x$.

$$V_{GS} = 5 - V_x, \quad V_{DS} = 5 - V_x,$$

① When $V_{GS} = 5 - V_x < V_{TH} = 0.7 \Rightarrow V_x > 4.3V$,
we know $I_x = 0$.

② When $V_{GS} = 5 - V_x > V_{TH} = 0.7 \Rightarrow V_x < 4.3V$,
we know $V_{DS} = 5 - V_x > V_{GS} - V_{TH} = 5 - V_x - 0.7$.


Therefore, it is in saturation region.

$$I_x = I_D = \frac{1}{2} \times 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20 \times 10^{-6}}{2 \times 10^{-6} - 2 \times 0.08 \times 10^{-6}} (5 - V_x - 0.7)^2$$

$$= 7.29 \times 10^{-4} (V_x - 4.3)^2$$

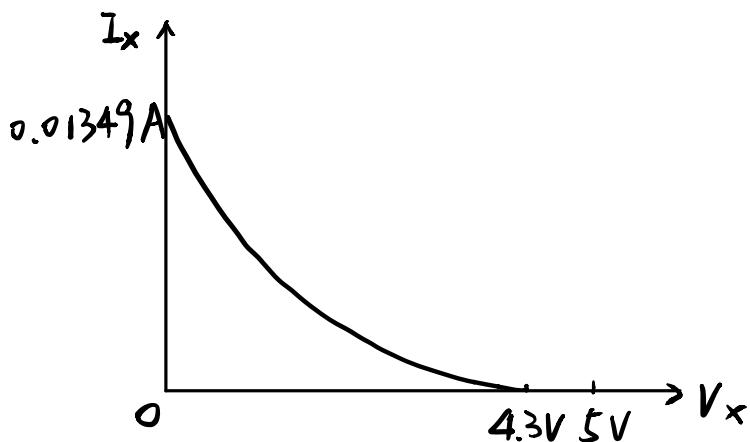(2). When $V_{DD} < V_x$, we have $V_x > 5V$.

According to the directions, we do not need to consider this case.



(b). NMOS

(1) When $V_x < 1V$, we have $V_D = 1V$, $V_S = V_x$

$$V_{GS} = 1.9 - V_x, \quad V_{DS} = 1 - V_x$$

Since $V_x < 1V$, we know $V_{GS} = 1.9 - V_x > 0.9 > V_{TH}$.

Since $V_{DS} = 1 - V_x < V_{GS} - V_{TH} = 1.9 - V_x - 0.7$,

We know it is in triode region.

$$I_x = -I_D = -350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20 \times 10^{-6}}{2 \times 10^{-6} - 2 \times 0.08 \times 10^{-6}} \left[(1.2 - V_x)(1 - V_x) - \frac{1}{2}(1 - V_x)^2 \right]$$

$$= -1.46 \times 10^{-3} (-0.5V_x^2 + 1.2V_x + 0.7)$$

(2) When $V_x > 1V$, we have $V_D = V_x$, $V_S = 1V$

$$V_{GS} = 0.9V, \quad V_{DS} = V_x - 1$$

Since $V_{GS} = 0.9V > 0.7V$, it is turned on

① When $V_{DS} = V_x - 1 < V_{GS} - V_{TH} = 0.2 \Rightarrow 1 < V_x < 1.2$,

We know it is in triode region


$$I_x = I_D = 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20 \times 10^{-6}}{2 \times 10^{-6} - 2 \times 0.08 \times 10^{-6}} \left[(0.9 - 0.7)(V_x - 1) - \frac{1}{2}(V_x - 1)^2 \right]$$

$$= 1.46 \times 10^{-3} (-0.5V_x^2 + 1.2V_x - 0.7)$$

② When $V_{DS} = V_x - 1 \geq V_{GS} - V_{TH} = 0.2 \Rightarrow V_x > 1.2$, in saturation.

$$I_x = I_D = \frac{1}{2} \times 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20 \times 10^{-6}}{2 \times 10^{-6} - 2 \times 0.08 \times 10^{-6}} [0.2]^2$$

$$= 2.92 \times 10^{-5}$$

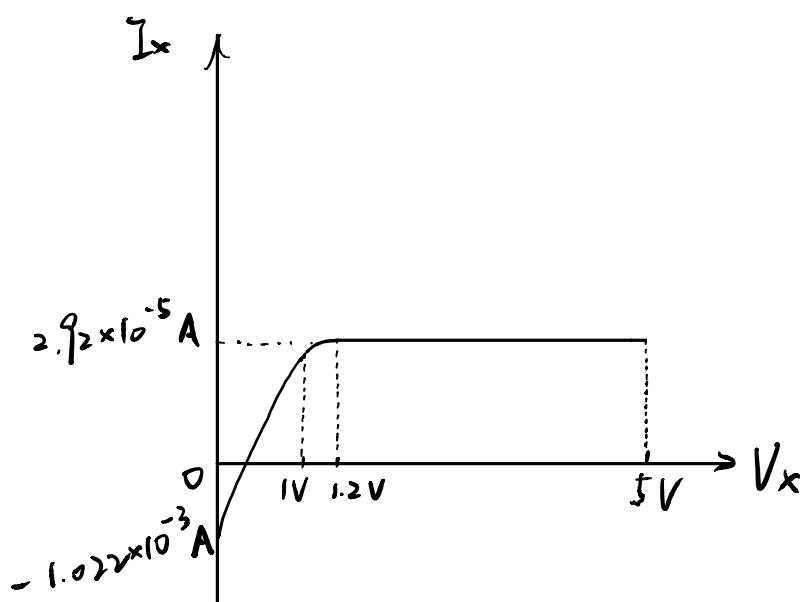

(c). NMOS

(1). When $V_x < 1.9V$, we have $V_D = 1.9V$, $V_S = V_x$

$$V_{GS} = 1 - V_x, \quad V_{DS} = 1.9 - V_x$$

① When $V_{GS} = 1 - V_x < 0.7V \Rightarrow V_x > 0.3V$,
we have $I_x = 0$

② When $V_{GS} = 1 - V_x > 0.7V \Rightarrow V_x < 0.3V$.


we know $V_{DS} = 1.9 - V_x > V_{GS} - V_{TH} = 0.3 - V_x$, in saturation

$$I_x = -I_D = \frac{1}{2} \times 350 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20 \times 10^{-6}}{2 \times 10^{-6} - 2 \times 0.08 \times 10^{-6}} [0.3 - V_x]^2 \\ = -7.29 \times 10^{-4} (V_x - 0.3)^2$$

(2). When $V_x > 1.9V$, we have $V_D = V_x$, $V_S = 1.9V$,

$$V_{GS} = 1 - 1.9 = -0.9V < V_{TH} = 0.7V.$$

Therefore, $I_x = 0$.

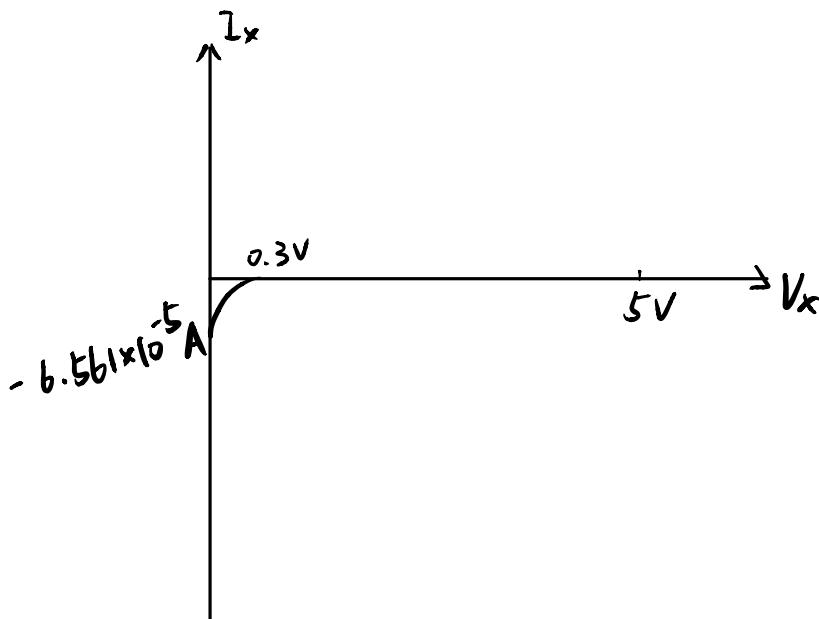

(d). PMOS

(1). When $V_x > 1.9V$, $V_S = V_x$, $V_D = 1.9V$.

$$V_{SG} = V_x - 1, \quad V_{SD} = V_x - 1.9$$

Since $V_{SG} = V_x - 1 > 0.9 \Rightarrow 0.8 = |V_{TH}|$. it is turned on.

Since $V_{SD} = V_x - 1.9 < V_{SG} - |V_{TH}| = V_x - 0.2$, in triode region.

$$I_x = I_D = 100 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20 \times 10^{-6}}{2 \times 10^{-6} - 2 \times 0.09 \times 10^{-6}} [(V_x - 1 - 0.8)(V_x - 1.9) - \frac{1}{2}(V_x - 1.9)^2]$$

$$= 4.21 \times 10^{-4} (0.5V_x^2 - 1.8V_x + 1.615)$$

(2). When $V_x < 1.9V$, $V_S = 1.9V$, $V_D = V_x$

$$V_{SG} = 1.9 - 1 = 0.9V, \quad V_{SD} = 1.9 - V_x$$

① When $V_{SD} = 1.9 - V_x < V_{SG} - |V_{TH}| = 0.1 \Rightarrow V_x > 1.8$, in triode region.


$$I_x = -I_D = -100 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20 \times 10^{-6}}{2 \times 10^{-6} - 2 \times 0.09 \times 10^{-6}} [(0.9 - 0.8)(1.9 - V_x) - \frac{1}{2}(1.9 - V_x)^2]$$


$$= 4.21 \times 10^{-4} (-0.5V_x^2 + 1.8V_x + 1.615)$$

② When $V_{SD} = 1.9 - V_x > V_{SG} - |V_{TH}| = 0.1 \Rightarrow V_x < 1.8$, in saturation region.

$$I_x = -I_D = \frac{1}{2} \times 100 \times 10^{-4} \times 3.835 \times 10^{-3} \times \frac{20 \times 10^{-6}}{2 \times 10^{-6} - 2 \times 0.09 \times 10^{-6}} (0.9 - 0.8)^2$$

$$= -2.11 \times 10^{-6} A$$

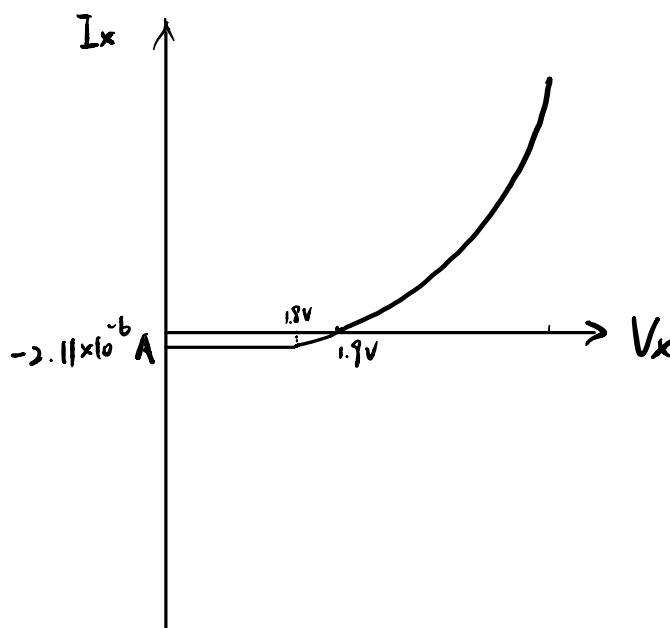

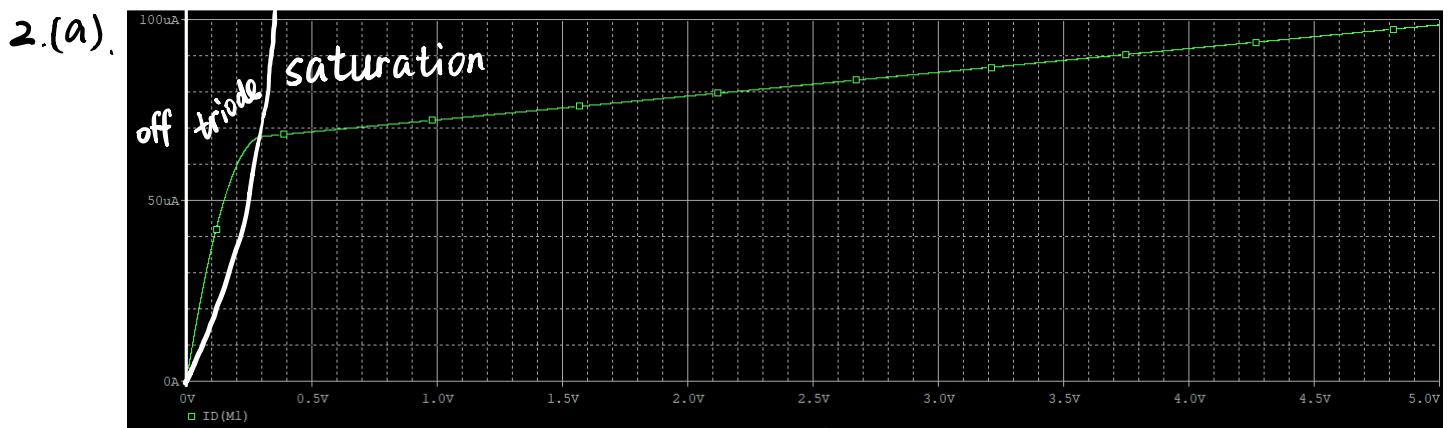


$$V_{GS} = 1V$$

From the plot, we have $(3, 85.39 \times 10^{-6}), (3.1, 86.038 \times 10^{-6})$, then
 $r_o = \frac{1}{\text{slope}} = \frac{3.1 - 3}{(86.038 - 85.39) \times 10^{-6}} = 1.54 \times 10^5$.

$$\text{Theoretically, } r_o = \frac{1}{\frac{1}{2} \mu_n C_0 \times \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda} = 1.52 \times 10^5$$

They are close to each other.

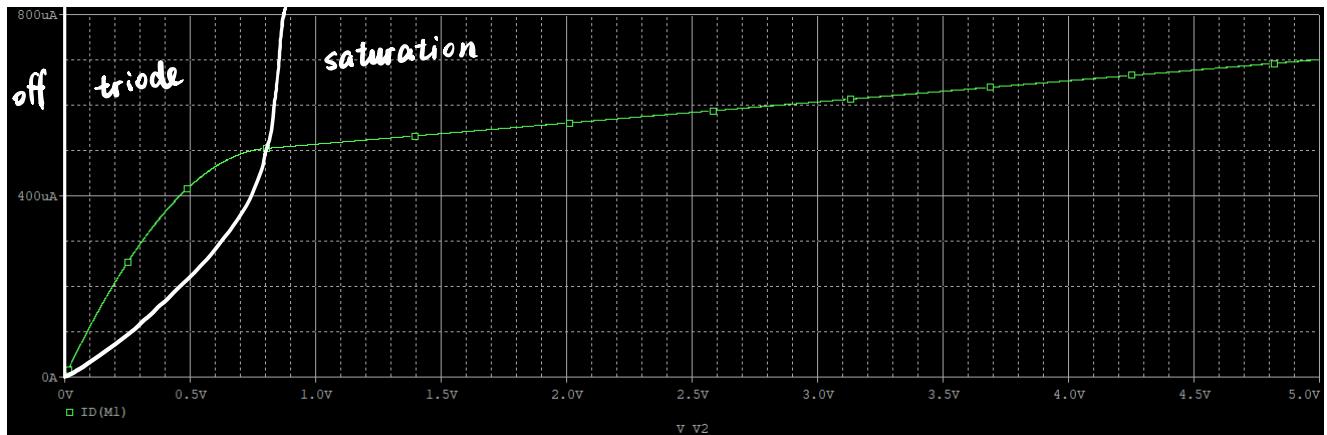


$$V_{GS} = 1.5V$$

From the plot, we have $(3, 607.22 \times 10^{-6}), (3.1, 611.83 \times 10^{-6})$, then
 $r_o = \frac{1}{\text{slope}} = \frac{3.1 - 3}{(611.83 - 607.22) \times 10^{-6}} = 2.17 \times 10^4$

$$\text{Theoretically, } r_o = \frac{1}{\frac{1}{2} \mu_n C_0 \times \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda} = 2.14 \times 10^4$$

They are close to each other.

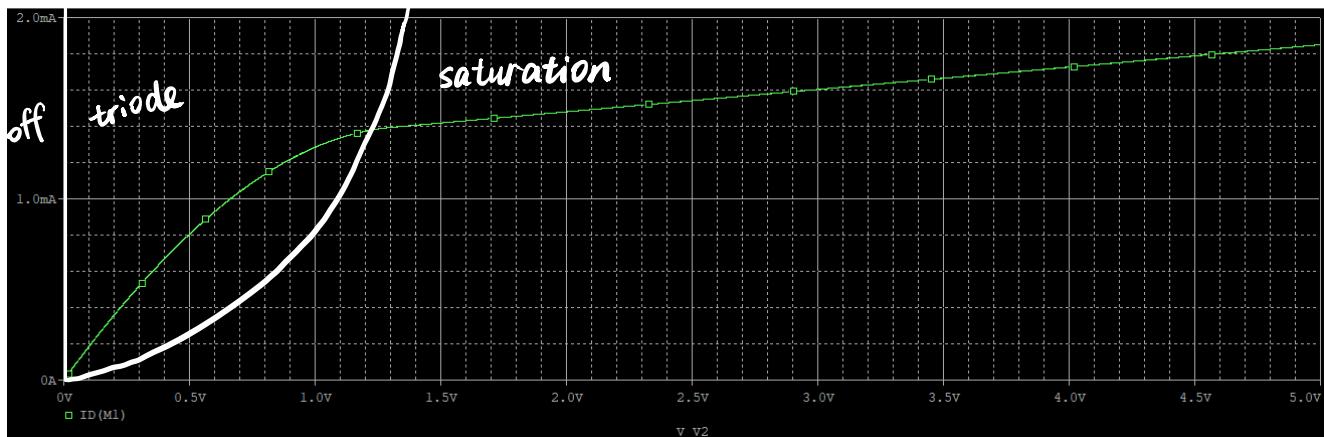


$$V_{GS} = 2V$$

From the plot, we have $(3, 1.6034 \times 10^{-3})$, $(3.1, 1.6158 \times 10^{-3})$, then
 $r_o = \frac{1}{\text{slope}} = \frac{3.1 - 3}{(1.6158 - 1.6034) \times 10^{-3}} = 7.81 \times 10^3$

$$\text{Theoretically, } r_o = \frac{1}{\frac{1}{2} \mu_n C_0 \times \frac{W}{L} (V_{GS} - V_{TH})^2 \lambda} = 8.11 \times 10^3$$

They are close to each other.

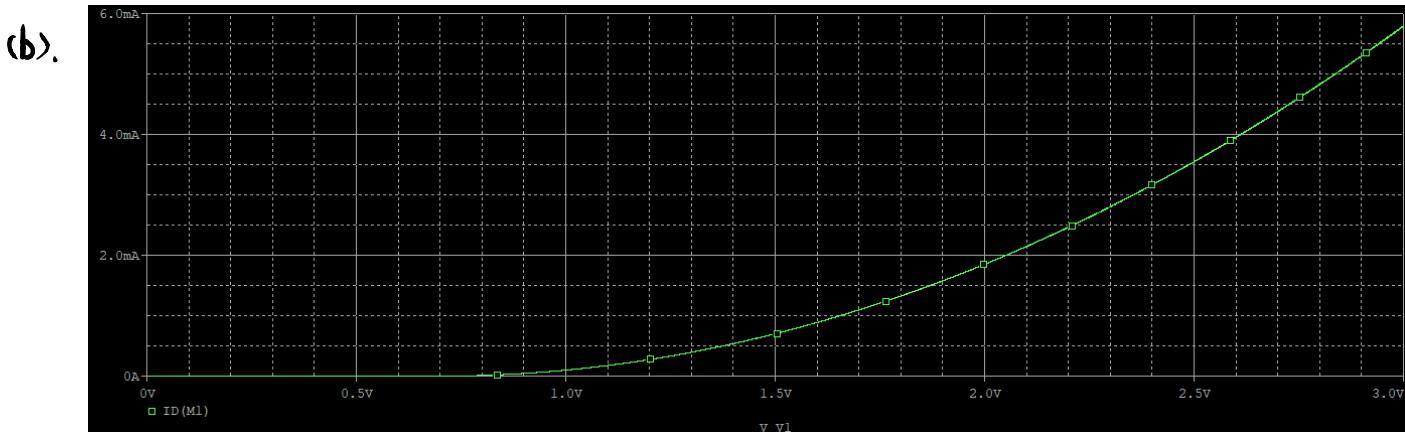

From the plot, we have $(1.95, 1.7105 \times 10^{-3})$, $(2.05, 1.9936 \times 10^{-3})$. Then
 $g_m = \text{slope} = \frac{(1.9936 - 1.7105) \times 10^{-3}}{2.05 - 1.95} = 2.831 \times 10^{-3}$

$$\begin{aligned} \text{Theoretically, we have } g_m &= \mu_n C_0 \times \frac{W}{L_{eff}} (V_{GS} - V_{TH}) (1 + \lambda V_{DS}) \\ &= 2.845 \times 10^{-3} \end{aligned}$$

They are close to each other